

# **Pre-Lab 8:**

## **BJT Amplifier Configuration**

Name: Wan-Yu Liao

ECEN 325 Section 514

TA: Mandela

Date: October 25, 2019

## Calculation

Choose  $V_{RE} = 1.1V$ ,  $V_{CE,sat} \approx 0.35V$ ,  $V_o = 1.2V$

$$V_{CC} - V_o - V_{RE} - 0.35 \geq V_{RC} \geq V_o$$

$$5 - 1.2 - 1.1 - 0.35 \geq V_{RC} \geq 1.2 \Rightarrow 2.35V \geq V_{RC} \geq 1.2V$$

$$\Rightarrow \underline{V_{RC} = 2V}$$

Choose  $\beta = 150$ ,  $N = 20$ ,  $R_i = 2.2k\Omega$

$$I_C \leq \frac{150}{2.2k} \frac{1}{\frac{20}{1.1+0.7} + \frac{20}{5-1.1-0.7} + \frac{25}{2}} = 2.28mA$$

$$\underline{I_C = 1.3mA}$$

$$R_C = \frac{2V}{1.3mA} = 1.5k\Omega$$

$$R_E = \frac{1.1V}{1.3mA} = 846\Omega$$

$$R_{B1} = \frac{150(5-1.1-0.7)}{20 \cdot 1.3mA} = 18.46k\Omega$$

$$R_{B2} = \frac{150(1.1+0.7)}{20 \cdot 1.3mA} = 10.38k\Omega$$

$$R_i = 18.46k \parallel 10.38k \parallel (150+1)(r_e + (846 \parallel R_a)) \quad R_g = \frac{1.5k}{25} - r_e$$

Choose  $R_i = 2.2k\Omega$

$$2200 = \frac{6644.06(151)(r_e + \frac{846(60-r_e)}{846+60-r_e})}{6644.06 + 151(r_e + \frac{846(60-r_e)}{846+60-r_e})} = 1.003 \times 10^6 (x +$$

$$r_e = -139.933, 221.716$$

$$R_g = 199.933, -161.716$$

②

$$R_{B1} = 18.46k\Omega$$

$$R_E = 846$$

$$R_{B2} = 10.38k\Omega$$

Find  $A_v$ ,  $R_i$ ,  $R_o$

$$V_{RB2} = \frac{10.38k}{18.46k + 10.38k} \cdot 5 = 1.8V$$

$$V_{RE} = 1.8V - 0.7V = 1.1V$$

$$I_E = \frac{1.1V}{846} = 1.3mA$$

$$r_e = \frac{V_T}{I_E} = \frac{25mA}{1.3mA} = 19.2\Omega$$

$$R_o = \frac{846 \cdot 19.2}{846 + 19.2} = \boxed{18.77\Omega}$$

$$A_v = \frac{846}{19.2 + 846} = \boxed{0.978}$$

$$R_i = 18.46k \parallel 10.38k \parallel 151(19.2 + 846) = \boxed{6322.52\Omega}$$

③

Find  $A_v$ ,  $R_i$ ,  $R_o$

$$R_o = \boxed{1.5k\Omega} = R_c$$

$$R_i = \frac{846 \cdot 19.2}{846 + 19.2} = \boxed{18.77\Omega}$$

$$A_v = \frac{1.5k}{19.2} = \boxed{78.125}$$



## Simulation

(1)

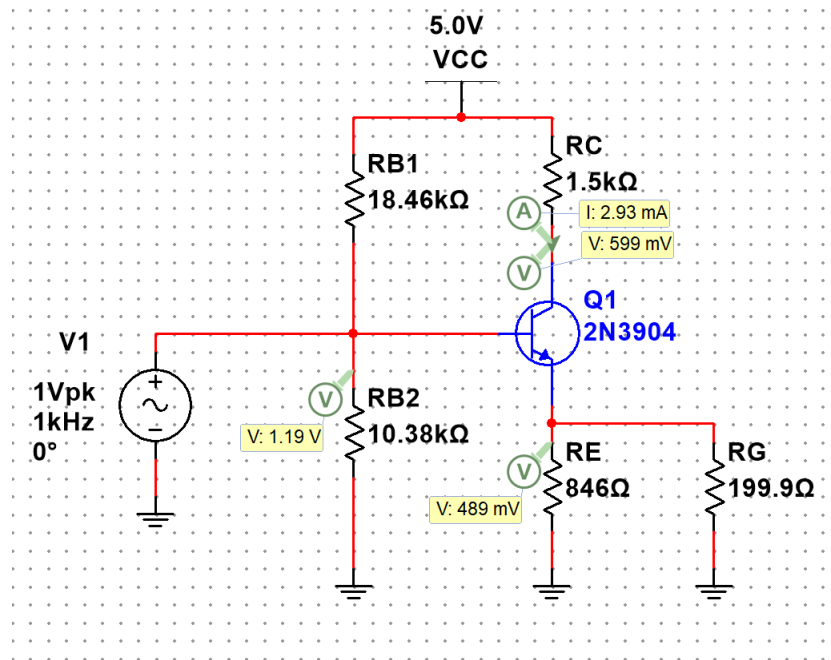


Figure 1: DC solution for Fig. 4(a)

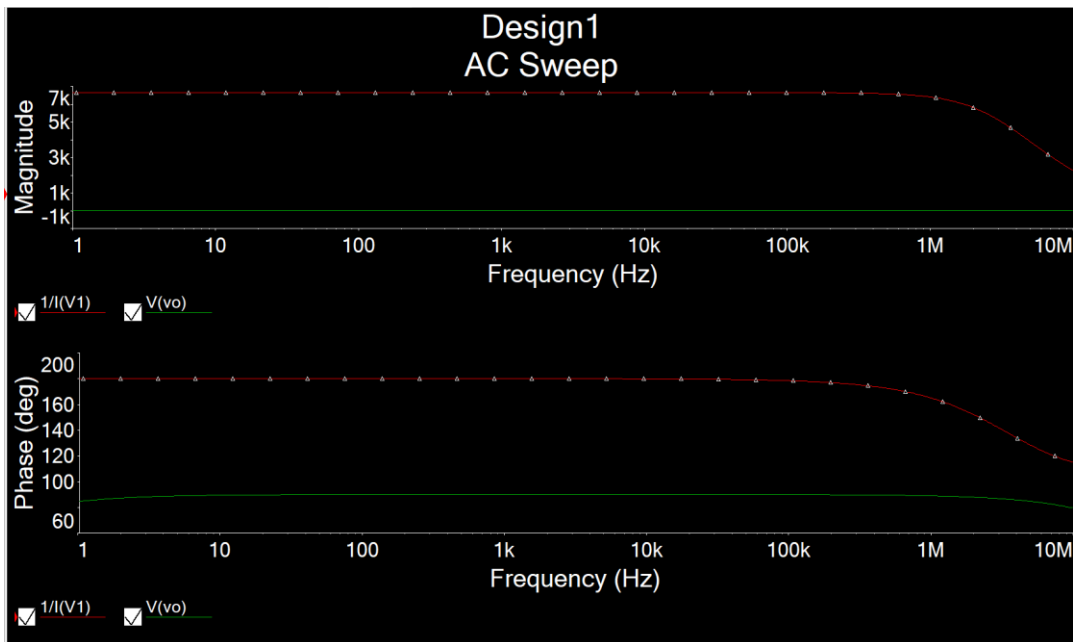


Figure 2: AC Simulation for  $A_v$ ,  $R_i$  and  $R_o$  for Fig. 4(a)

(Tried to find  $A_v$  but couldn't appear on the graph)

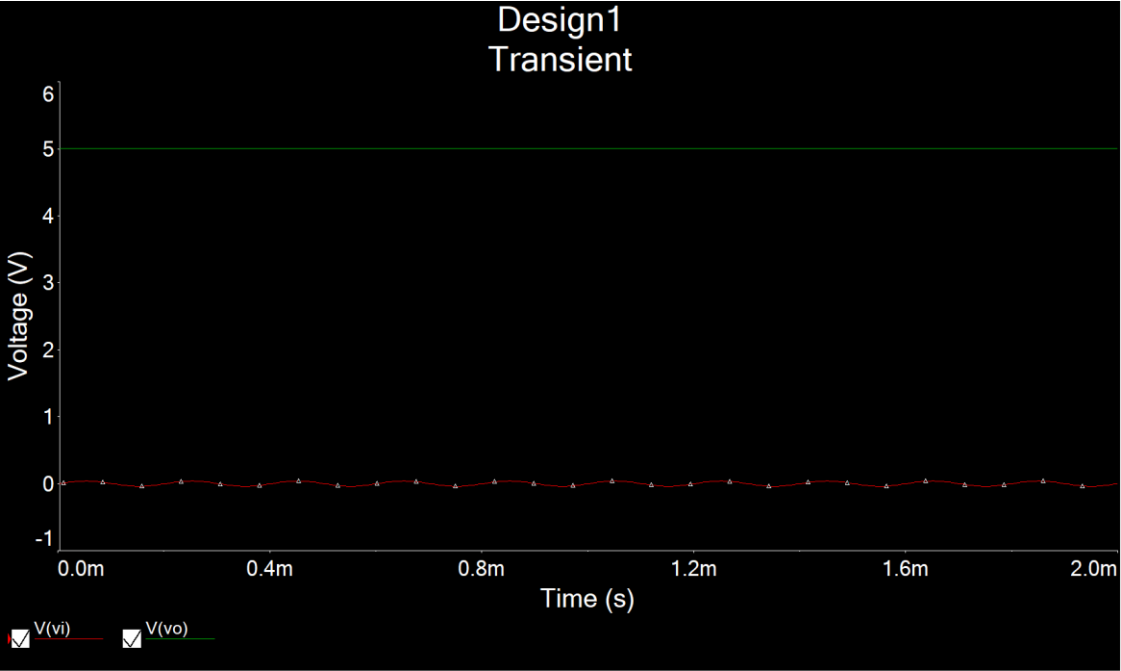


Figure 3: Time-domain Waveform for Fig. 4(a)

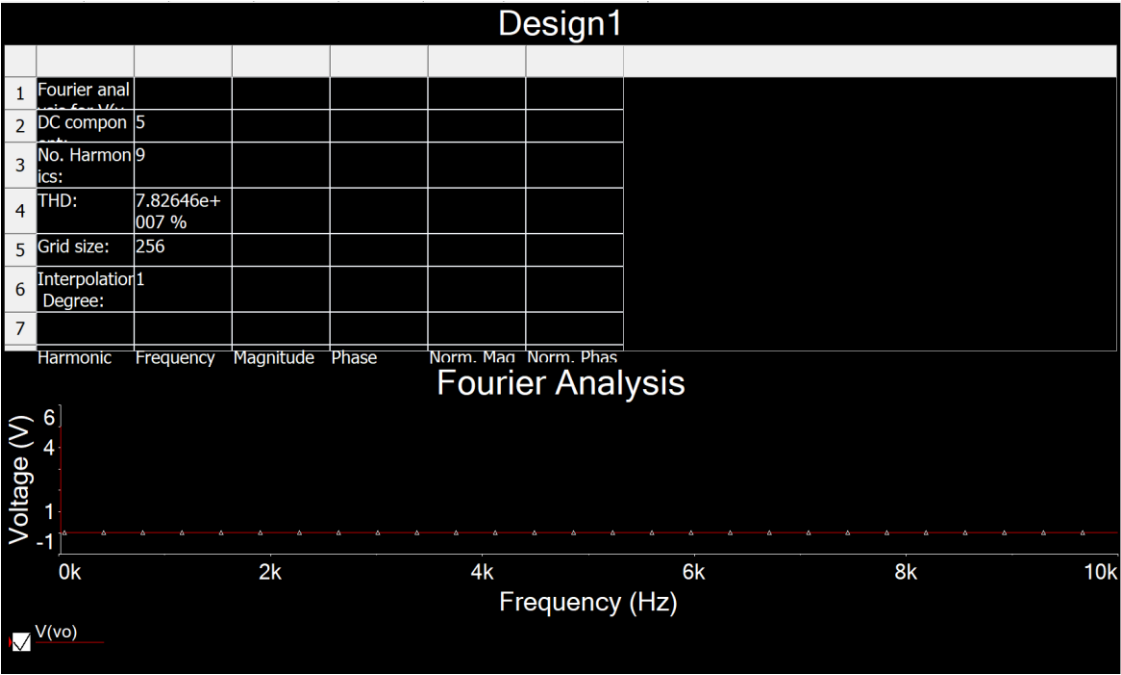


Figure 4: THD Waveform for Fig. 4(a)

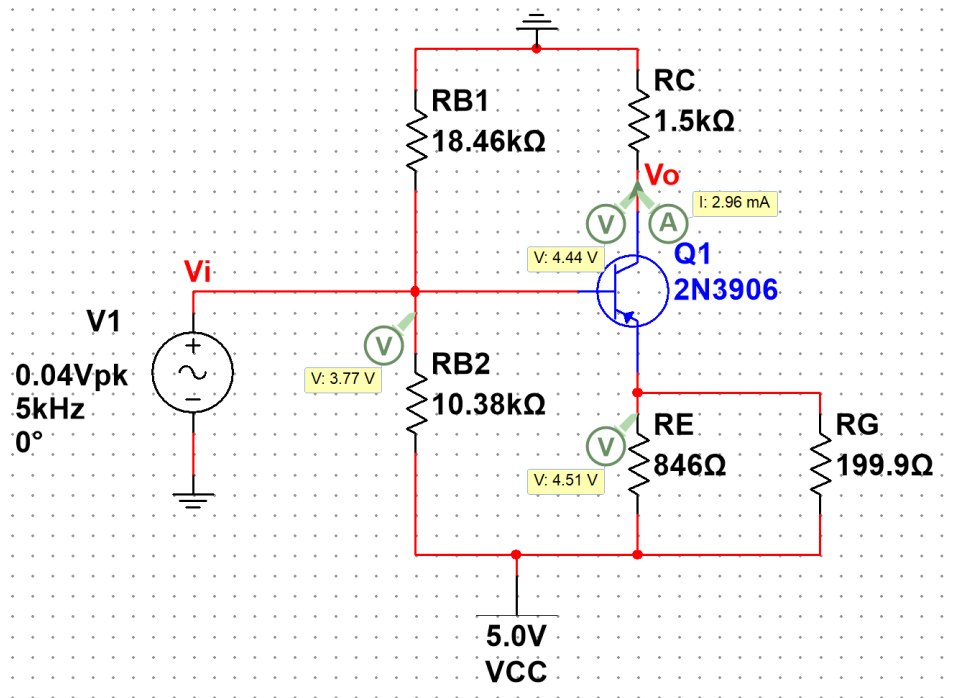


Figure 5: DC solution for Fig. 5(a)

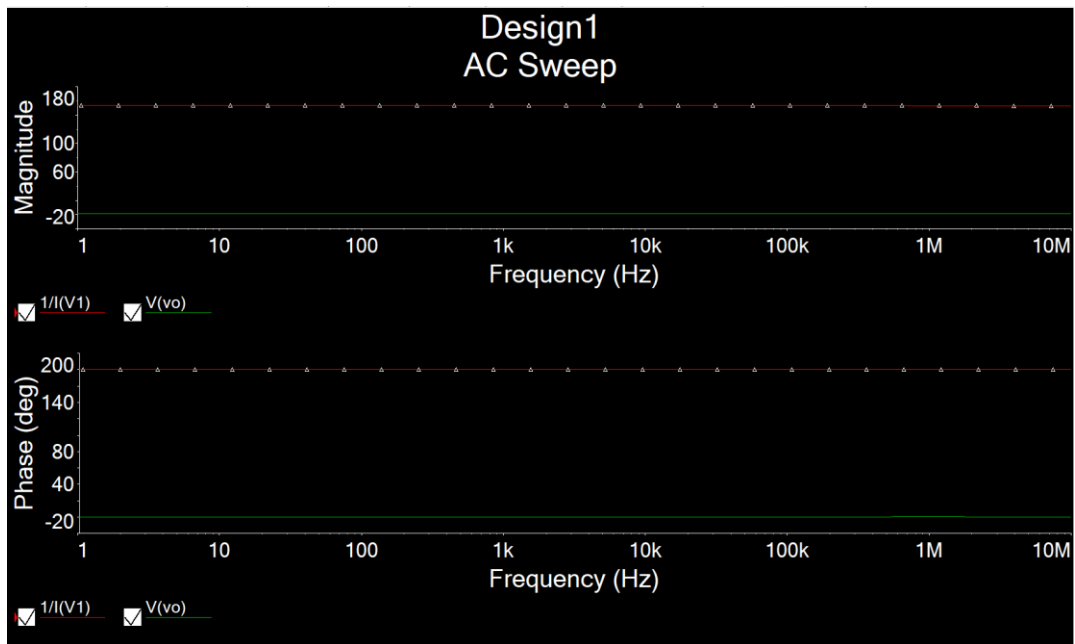


Figure 6: AC Simulation for  $A_v$ ,  $R_i$  and  $R_o$  for Fig. 5(a)

(Tried to find  $A_v$  but couldn't appear on the graph)

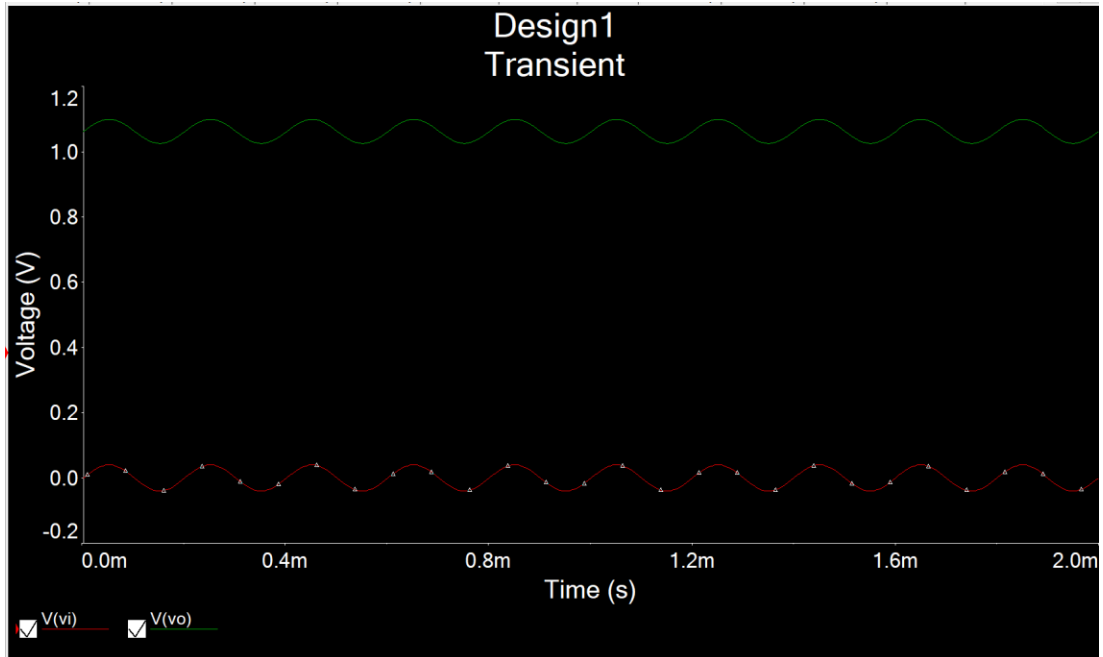


Figure 7: Time-domain Waveform for Fig. 5(a)



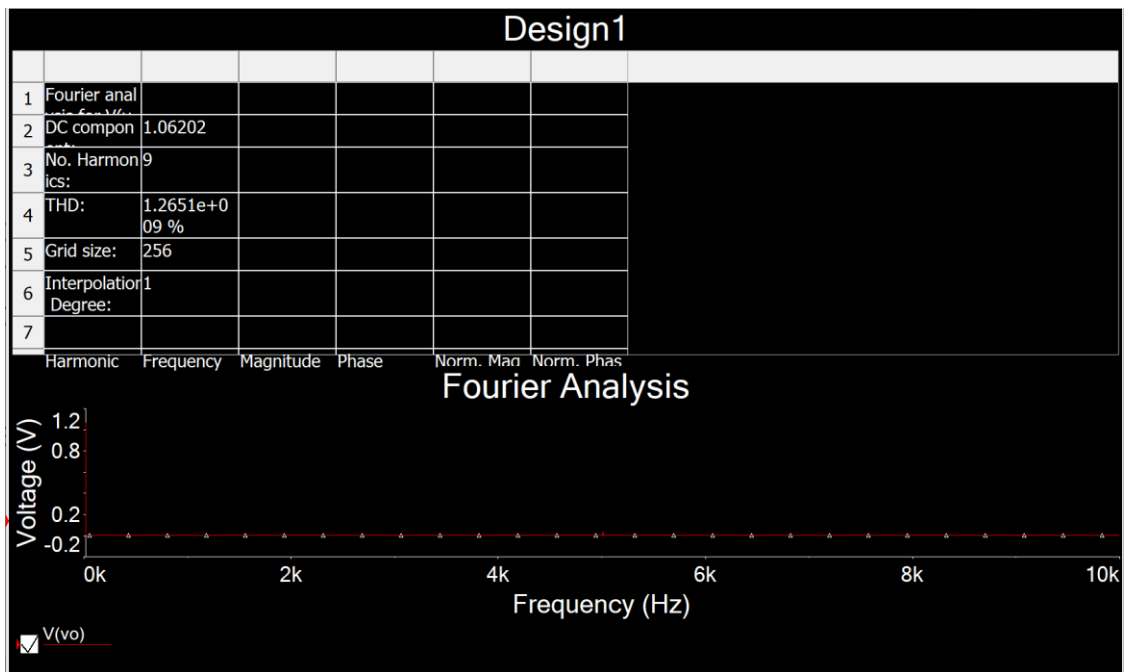


Figure 8: THD Waveform for Fig. 5(a)

(2)

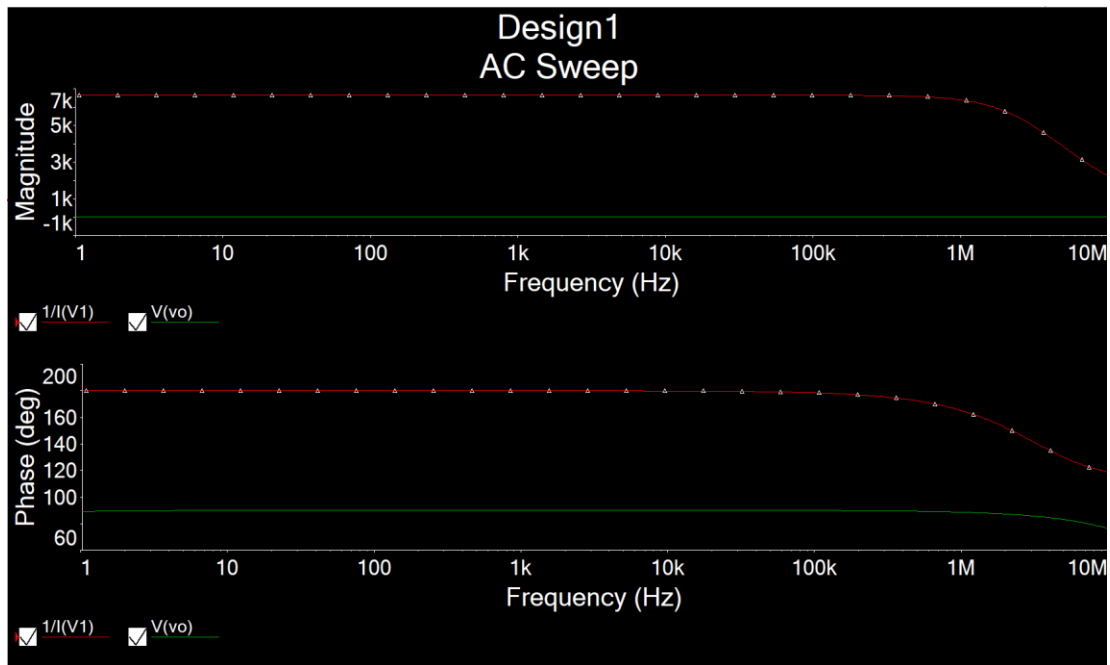

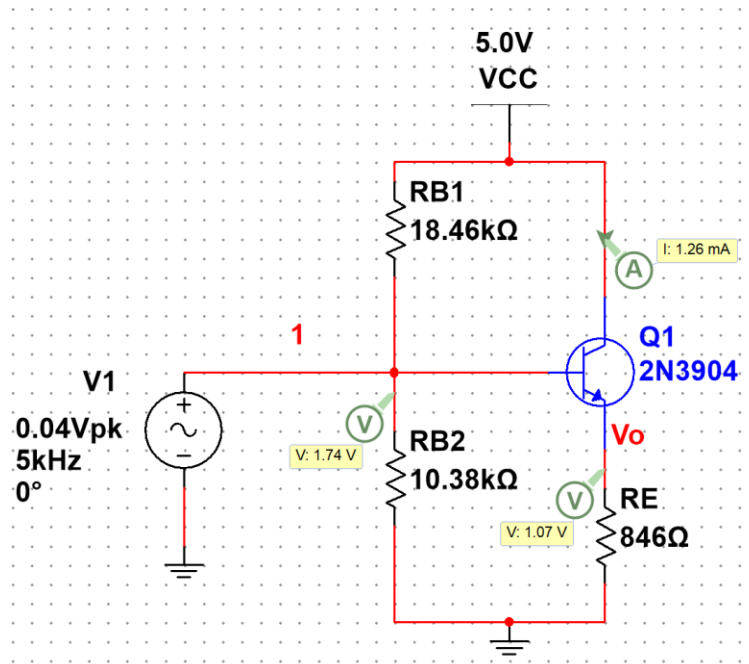

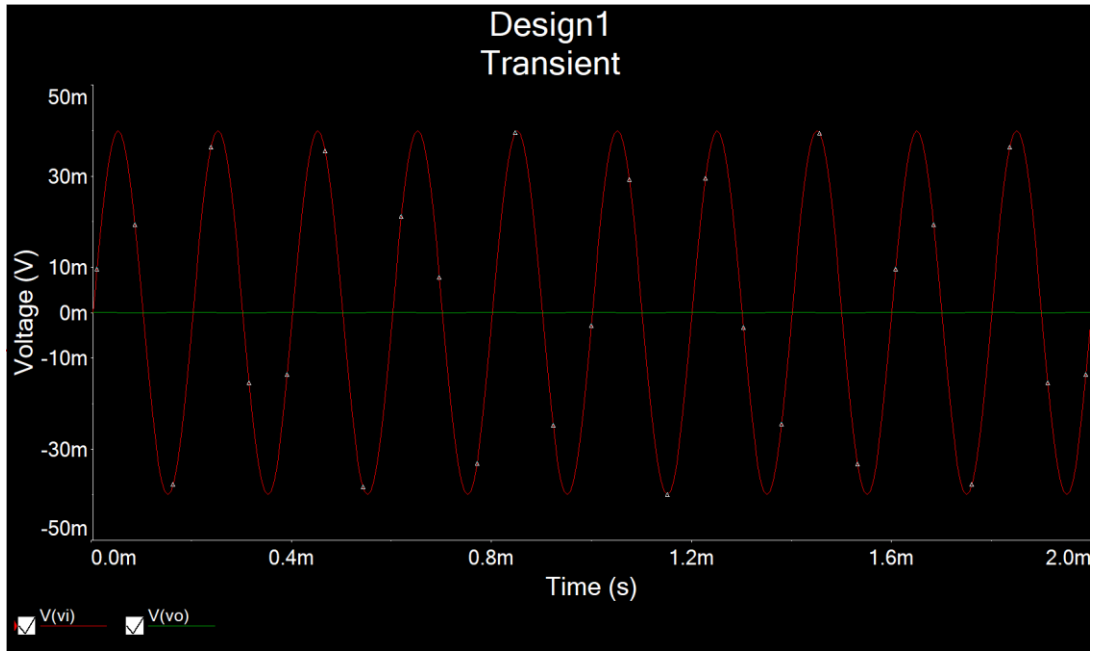


Figure 11: Time-domain Waveform for Fig. 6(a)

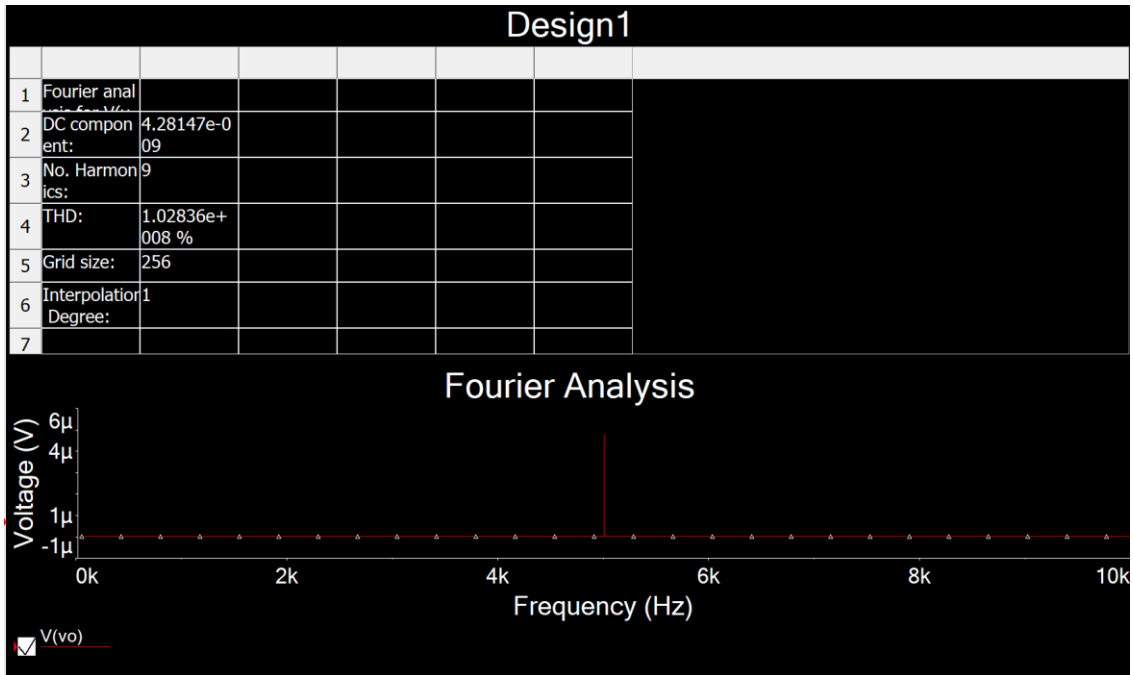


Figure 12: THD Waveform for Fig. 6(a)

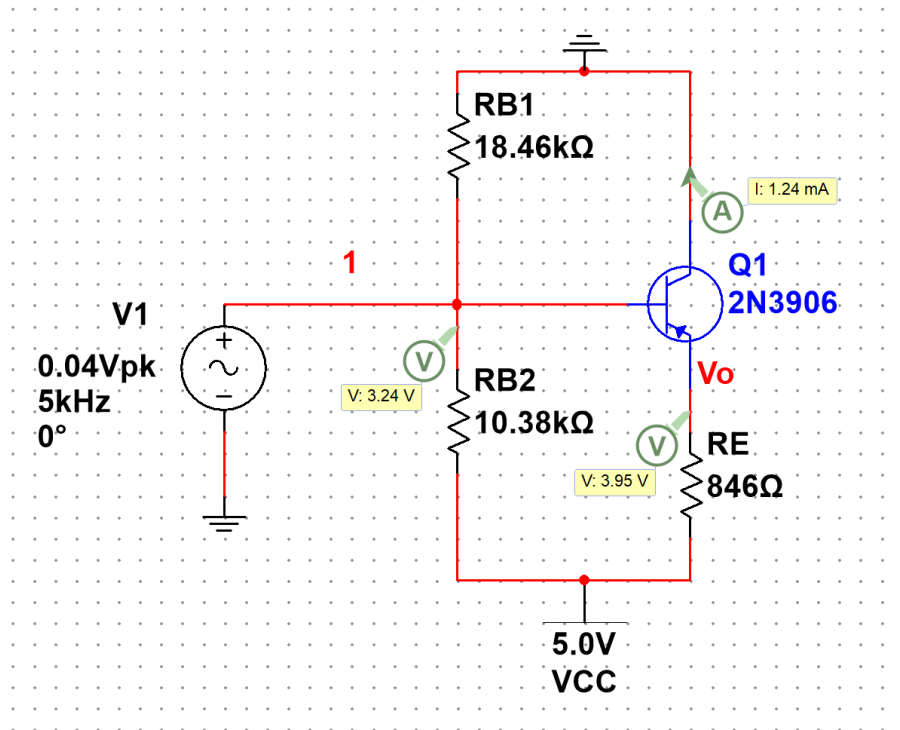


Figure 13: DC solution for Fig. 7(a)

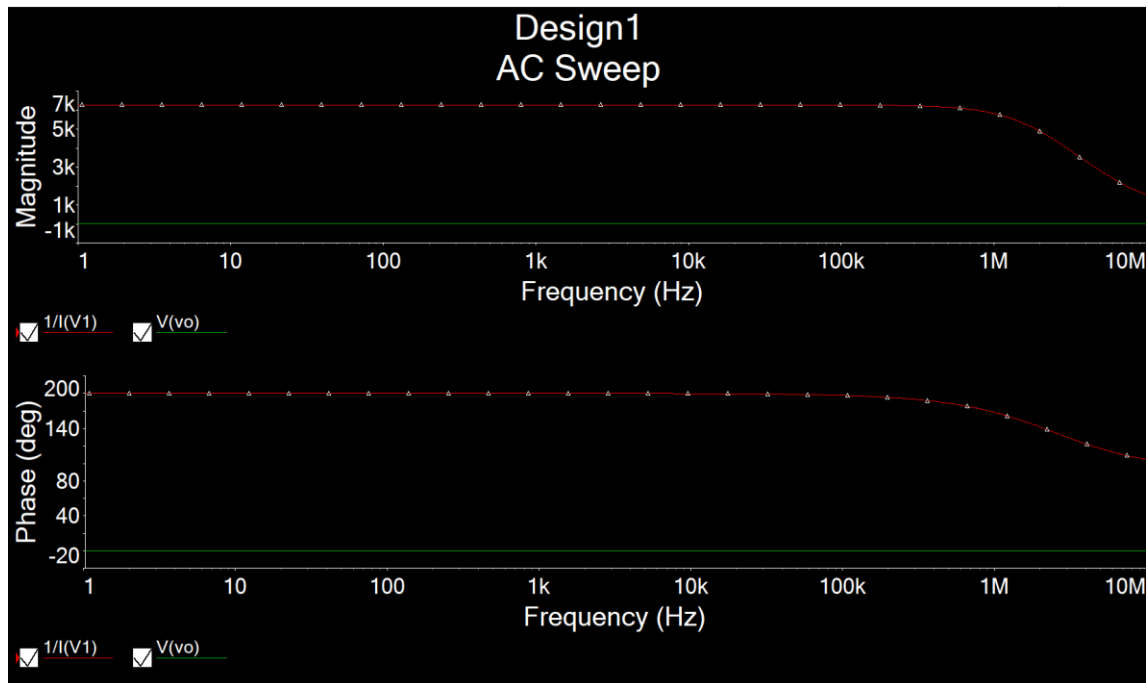


Figure 14: AC Simulation for  $A_v$ ,  $R_i$  and  $R_o$  for Fig. 7(a)

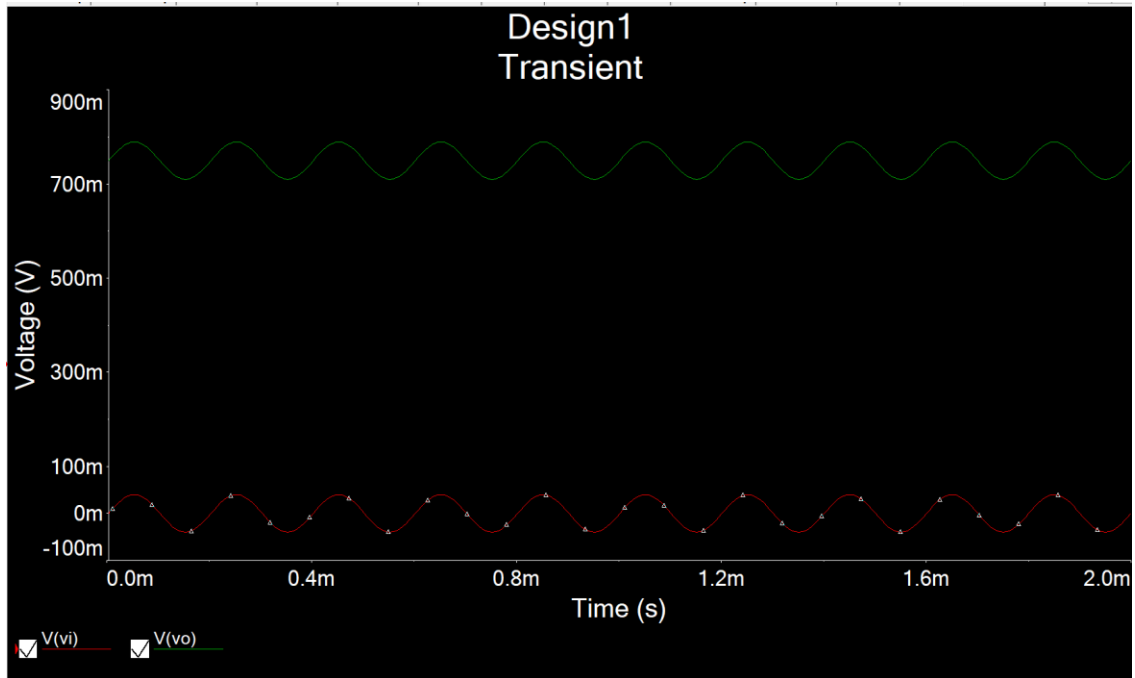


Figure 15: Time-domain Waveform for Fig. 7(a)

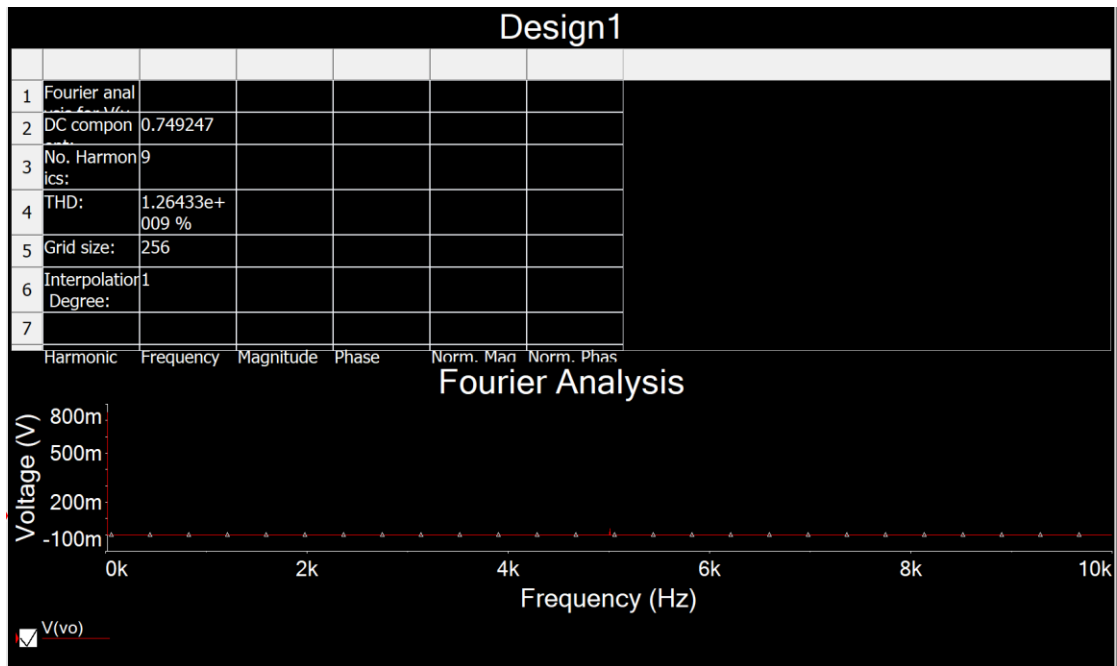


Figure 16: THD Waveform for Fig. 7(a)

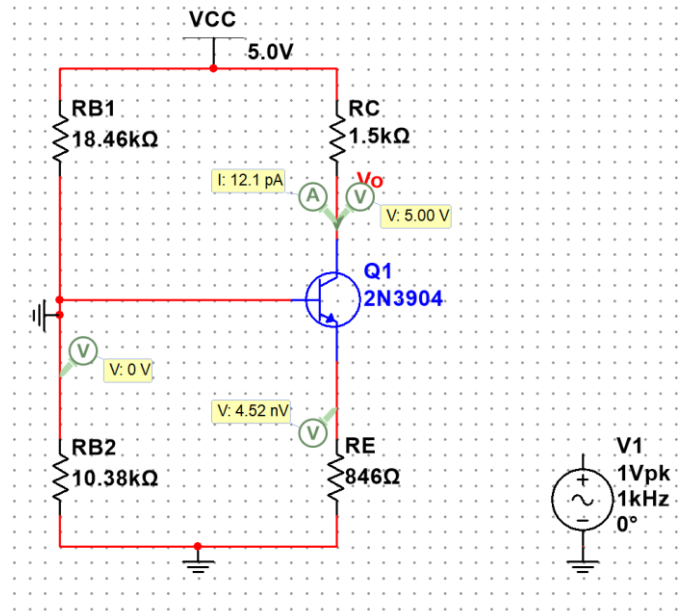


Figure 17: DC solution for Fig. 8(a)

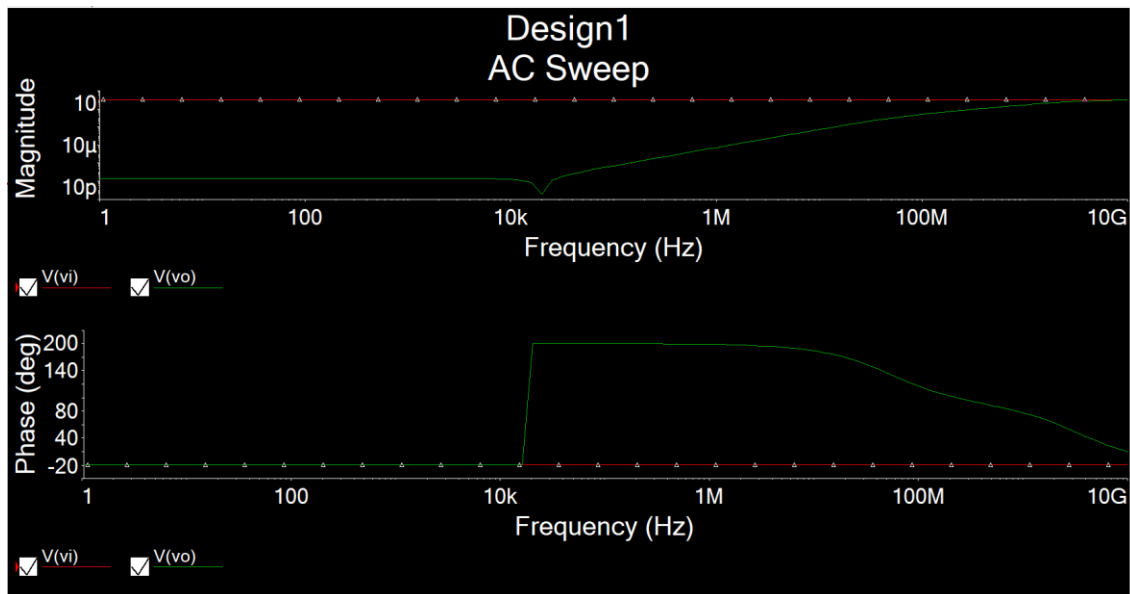


Figure 18: AC Simulation for  $A_v$ ,  $R_i$  and  $R_o$  for Fig. 8(a)

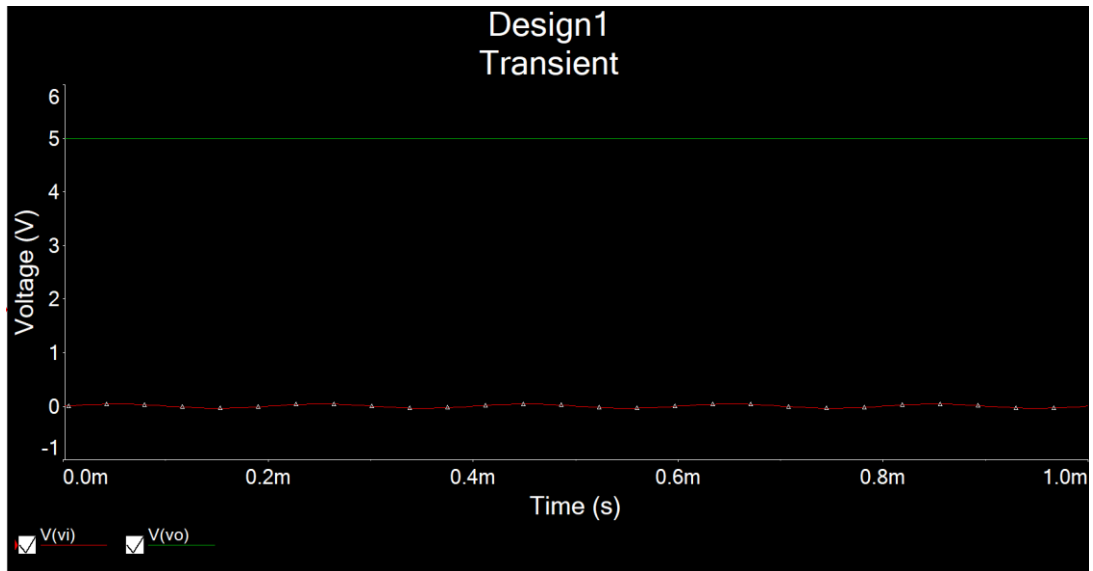


Figure 19: Time-domain Waveform for Fig. 8(a)

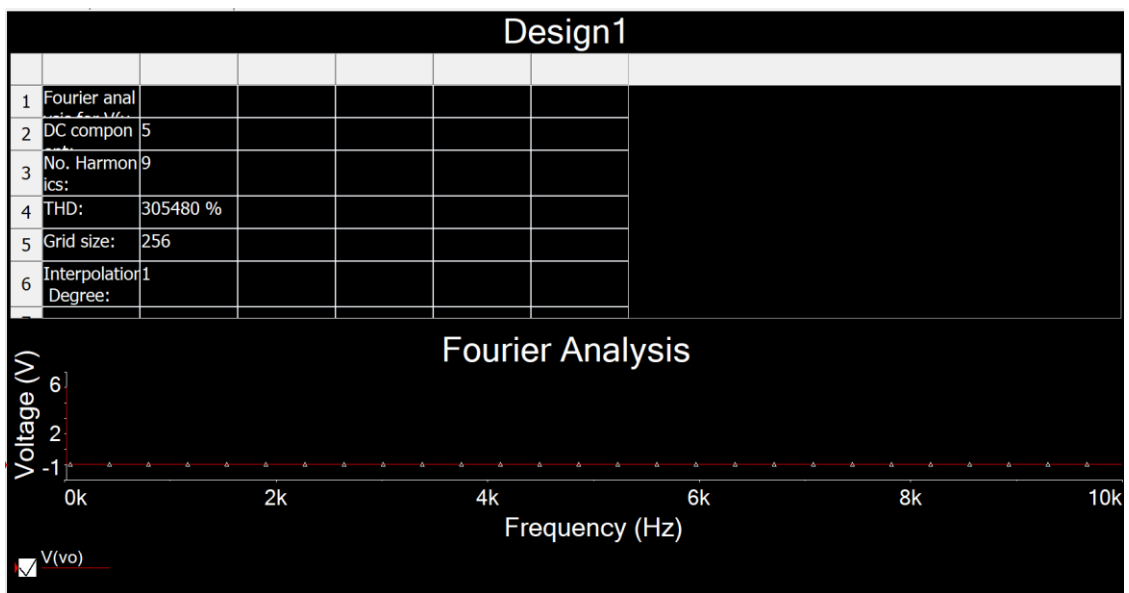


Figure 20: THD Waveform for Fig. 8(a)

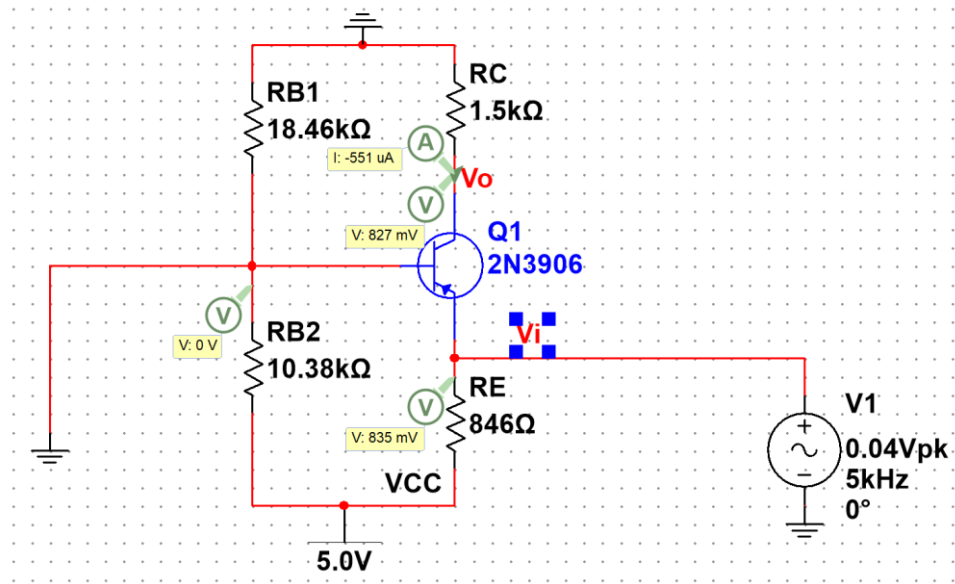


Figure 21: DC solution for Fig. 9(a)

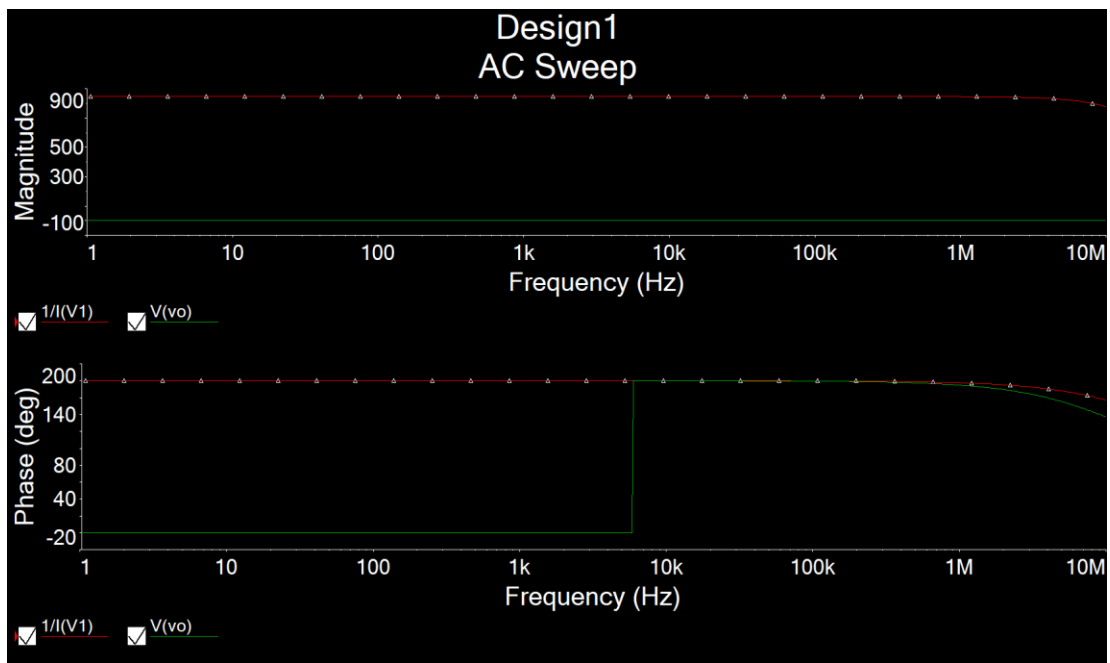


Figure 22: AC Simulation for  $A_v$ ,  $R_i$  and  $R_o$  for Fig. 9(a)

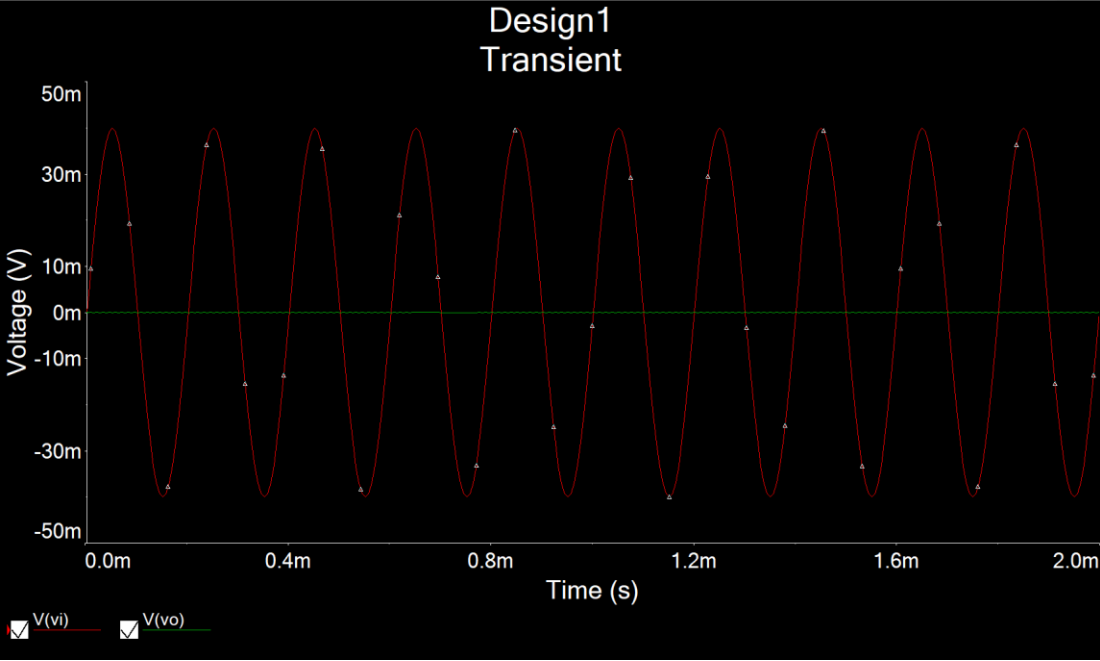


Figure 23: Time-domain Waveform for Fig. 9(a)

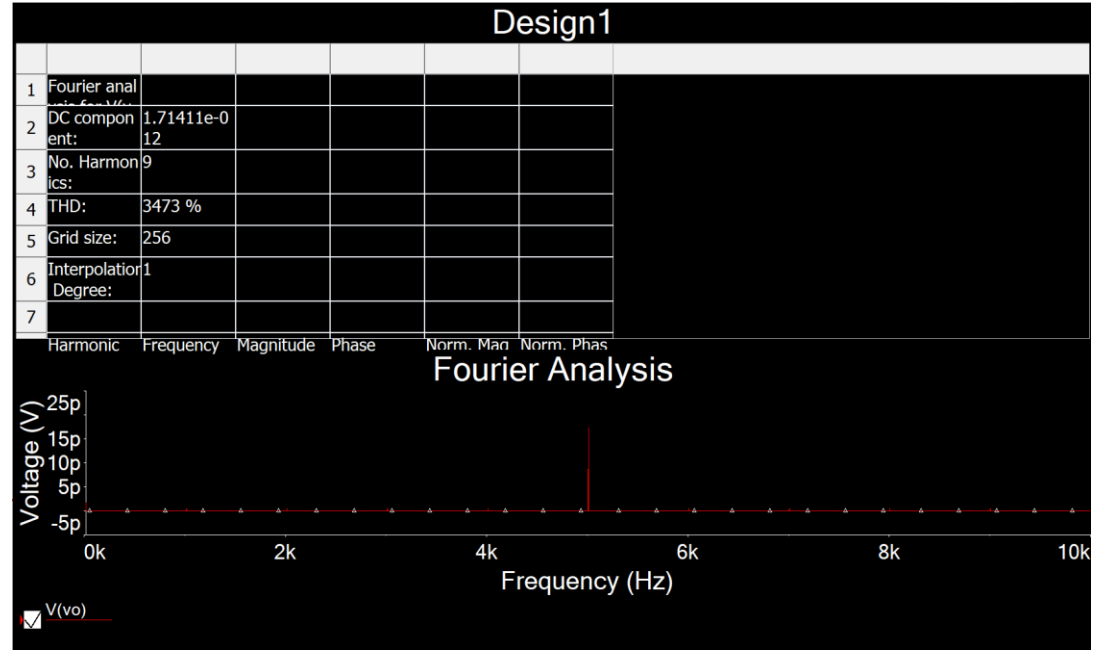


Figure 24: THD Waveform for Fig. 9(a)