

Lab 10:

Characterization of the MOSFET

Name: Wan-Yu Liao

ECEN 325 Section 514

TA: Mandela

Lab Date: November 7, 2019

Lab Report Due Date: November 12, 2019

Simulations

(1) NMOS using 2N7000G

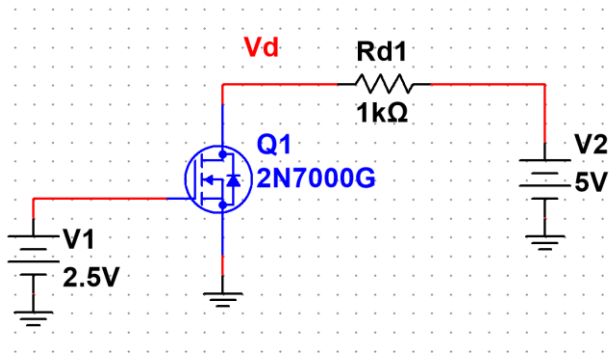


Figure 1: Schematic for NMOS using 2N7000G ▲

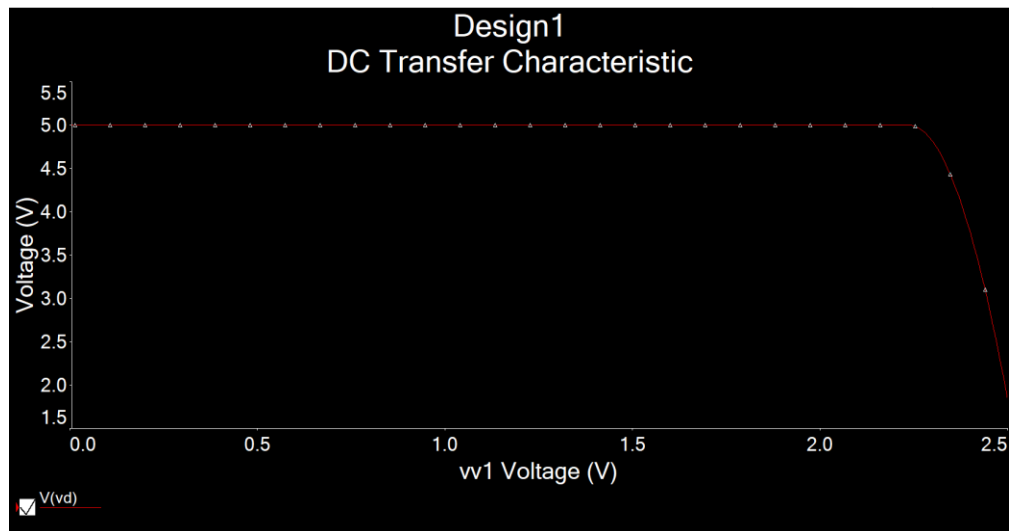


Figure 2: Simulation of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V ▲

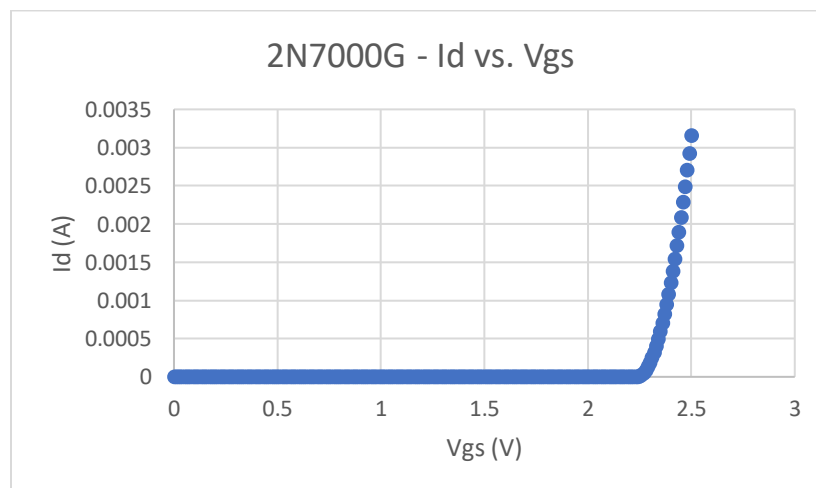


Figure 3: Excel plot of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V, where $I_d = (5 - V_d)/1000$ ▲

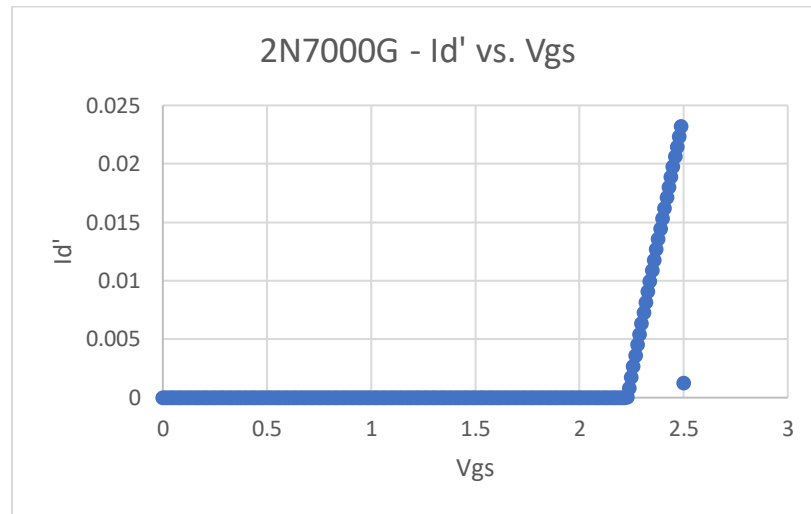


Figure 4: Excel plot of NMOS characterization of derivative of Id' vs. Vgs ▲

Threshold Voltage $V_t = 2.23V$

Transconductance parameter = $(0.023218 - 0)/(2.5 - 2.23) = 0.086$

(2) NMOS using CD4007N

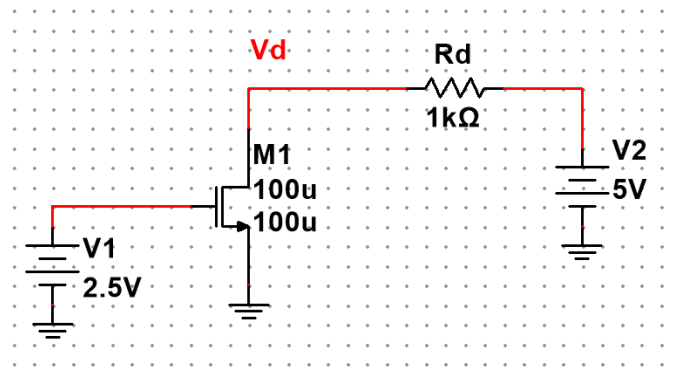


Figure 5: Schematic for NMOS using CD4007N ($\beta = 102\text{mA/V}^2$, $V_{TN} = 2.0V$) ▲

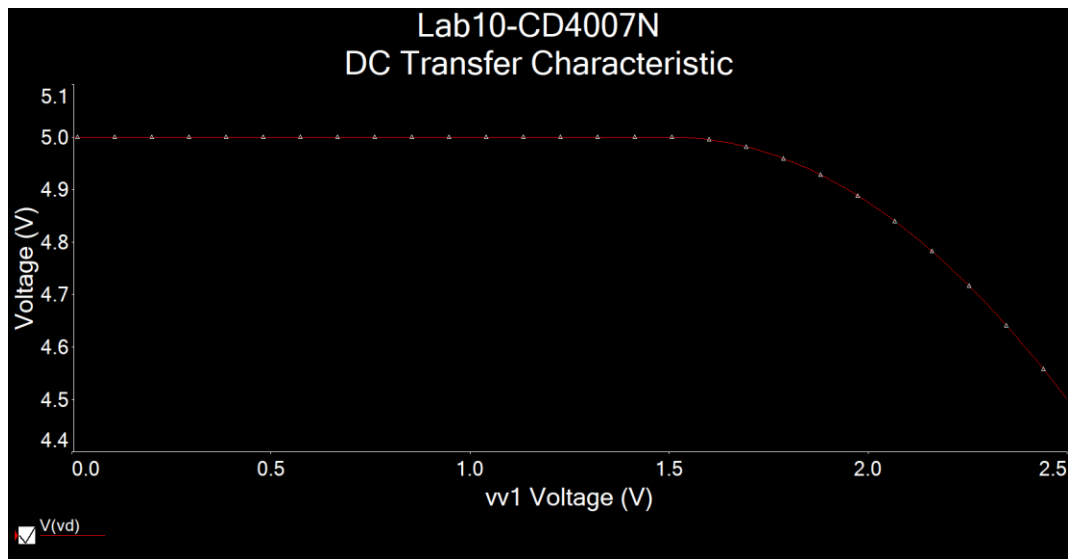


Figure 6: Simulation of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V ▲

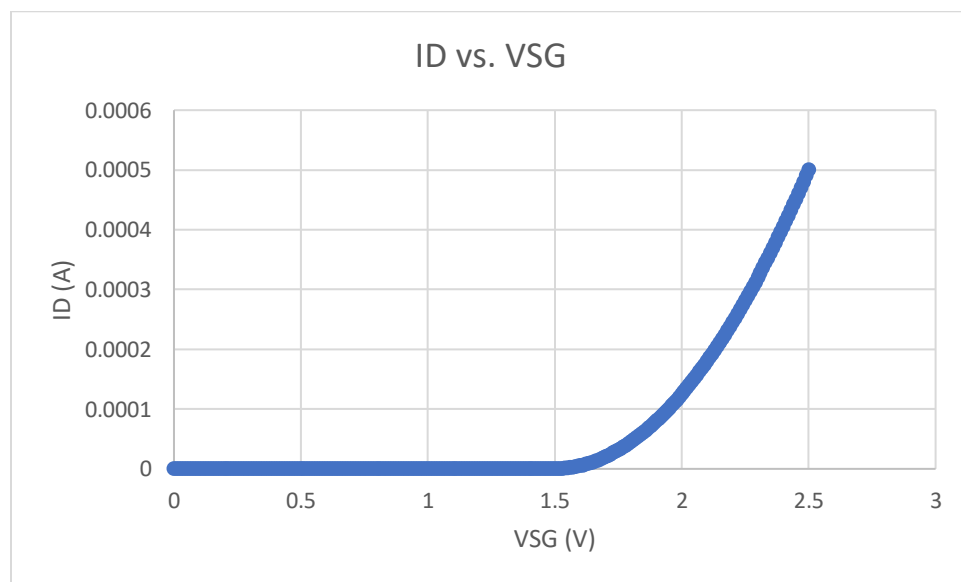


Figure 7: Excel plot of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V, where $I_d = (5 - V_d)/1000$ ▲

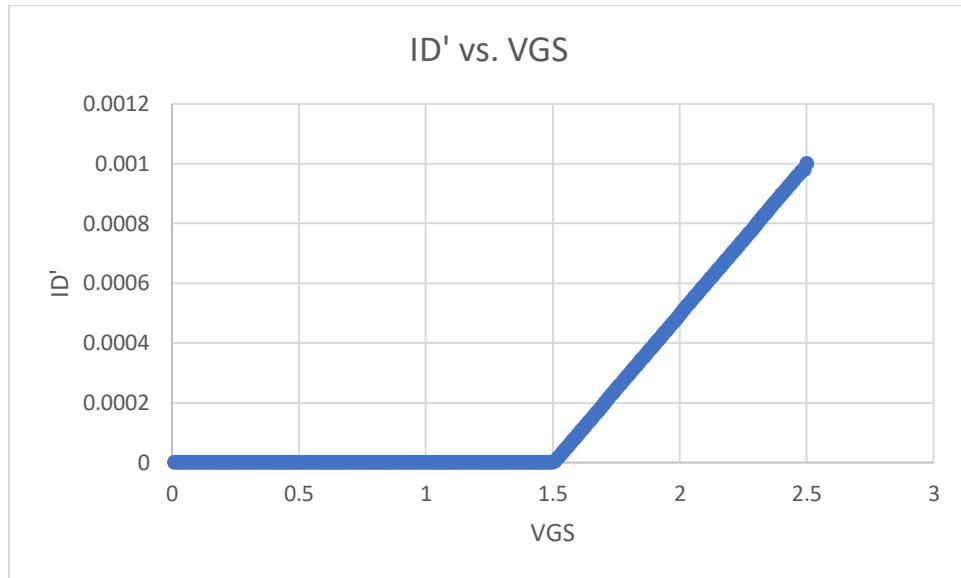


Figure 8-1: Excel plot of NMOS characterization of derivative of Id' vs. Vgs ▲

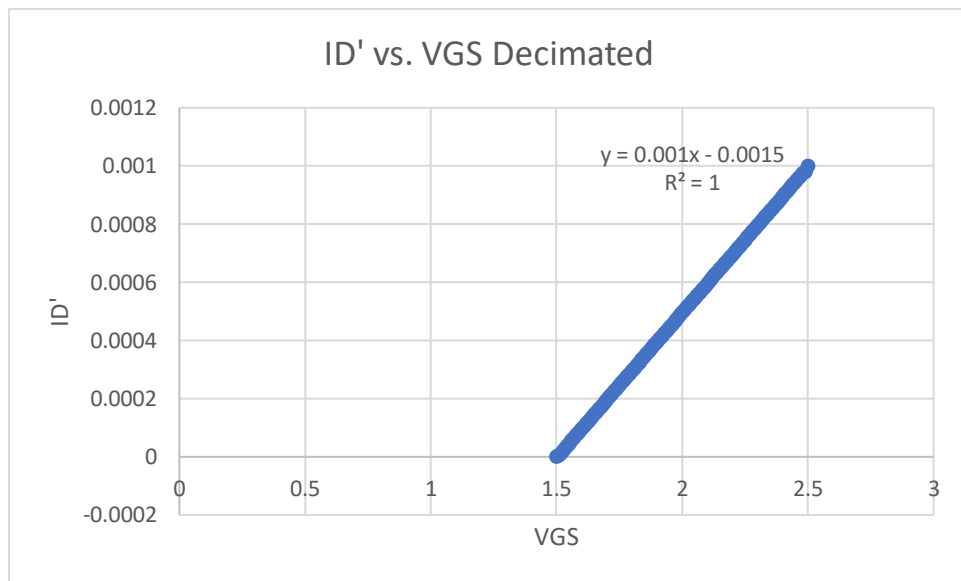


Figure 8-2: Excel plot of NMOS characterization of derivative of Id' vs. Vgs Decimated ▲

Threshold Voltage $V_t = 1.5V$

Transconductance parameter = $0.001A/V^2$

(3) PMOS using CD4007P

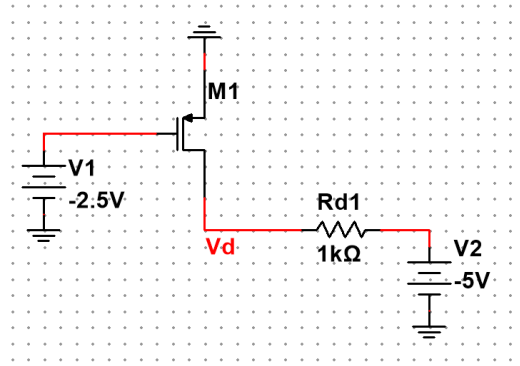


Figure 9: Schematic for PMOS using CD4007P ($\beta=102\text{mA/V}^2$, $V_{TN}=2.0\text{V}$) ▲

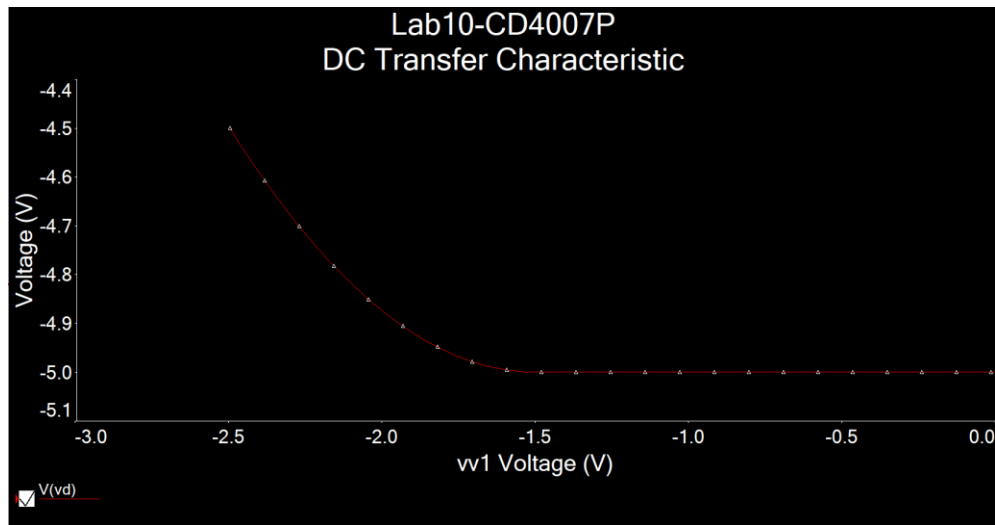


Figure 10: Simulation of PMOS characterization circuit using DC sweep of V1 from -2.5 to 0V, while V2 = -5V ▲

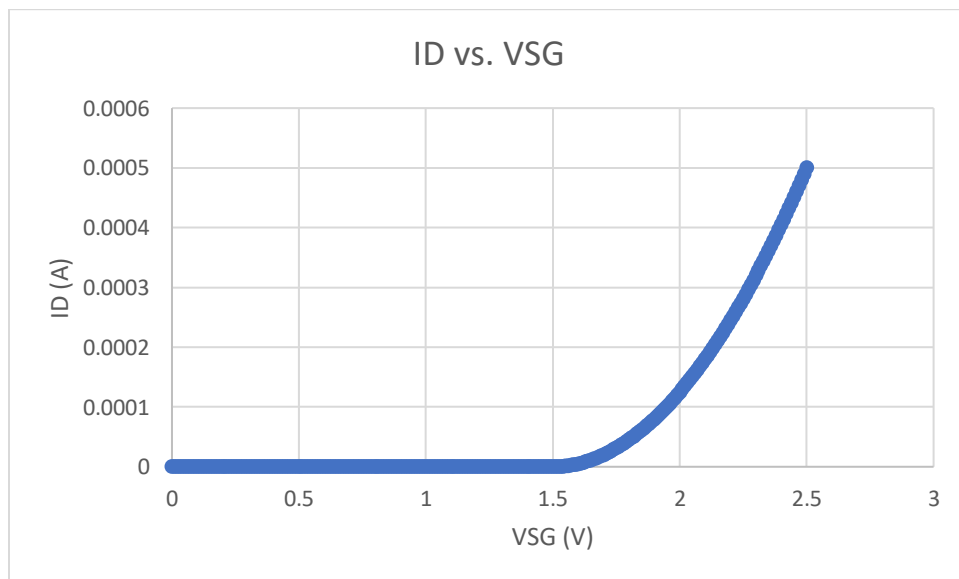


Figure 11: Excel plot of PMOS characterization circuit using DC sweep of V1 from -2.5 to 0V, while V2 = -5V, where $I_d = (V_d + 5)/1000$ ▲

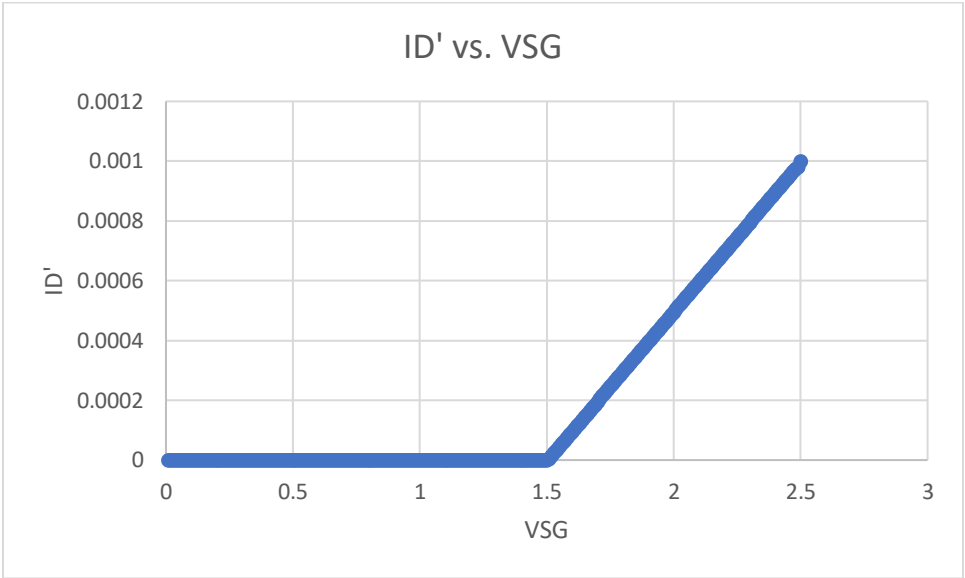


Figure 12-1: Excel plot of PMOS characterization of derivative of I_d' vs. V_{sg} ▲

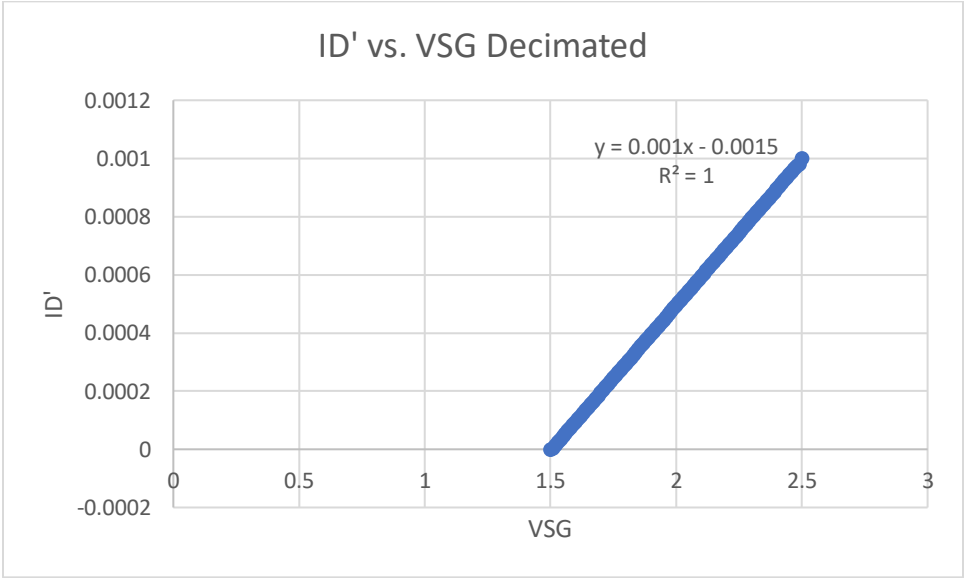


Figure 12-2: Excel plot of PMOS characterization of derivative of I_d' vs. V_{sg} Decimated ▲

Threshold Voltage $V_t = 1.5V$

Transconductance parameter = $0.001A/V^2$

Measurements

(1) NMOS using 2N7000G

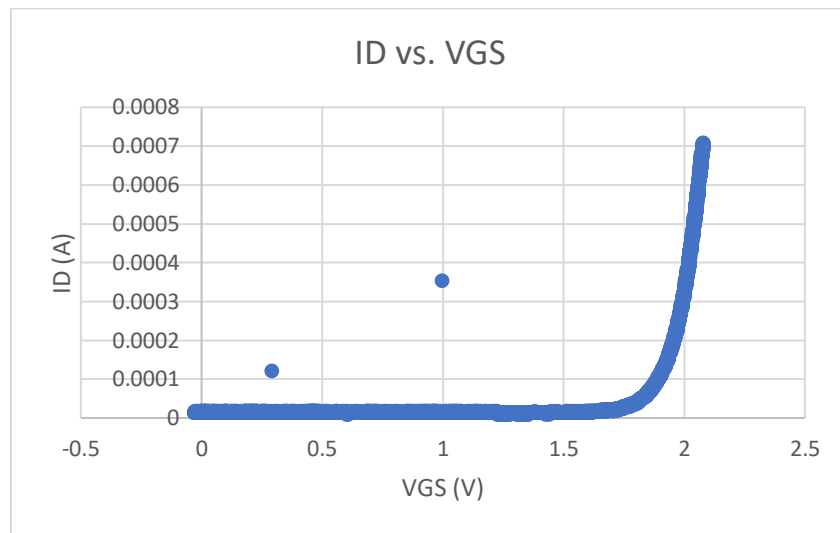


Figure 13: Plot of I_D vs. V_{GS} ▲

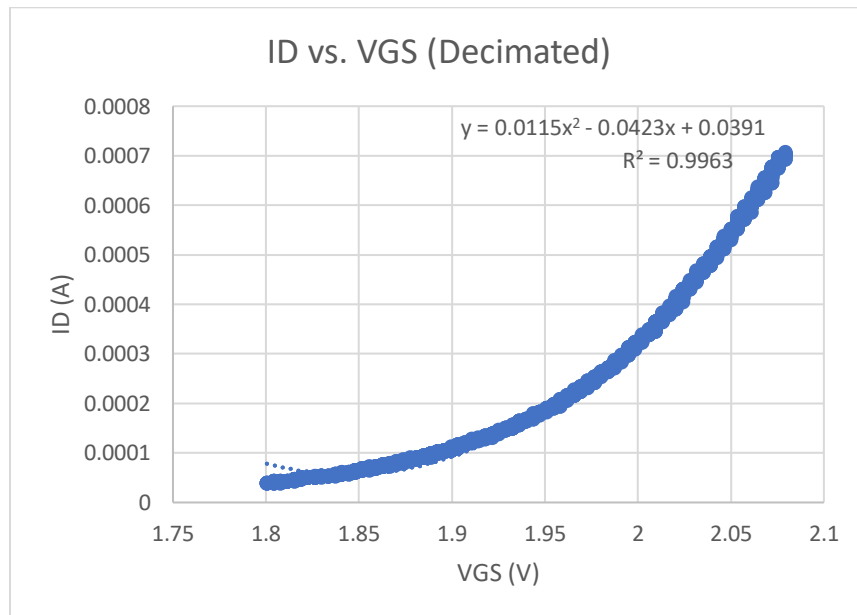


Figure 14: Plot of decimated I_D vs. decimated V_{GS} ▲

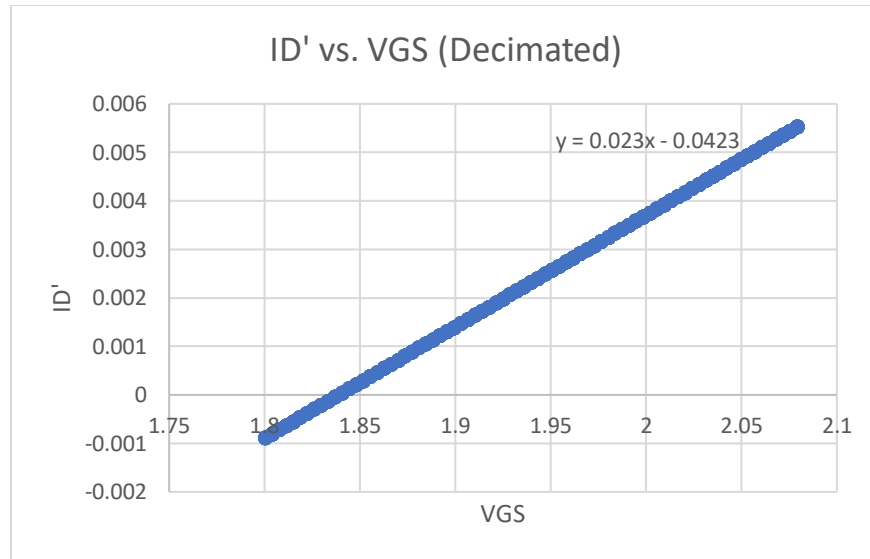


Figure 15: Plot of decimated $\frac{dI_D}{dV_{GS}}$ vs. decimated V_{GS} ▲

$$\beta = 0.023 \text{ A/V}^2, V_t = 1.84\text{V}$$

(2) NMOS using CD4007N

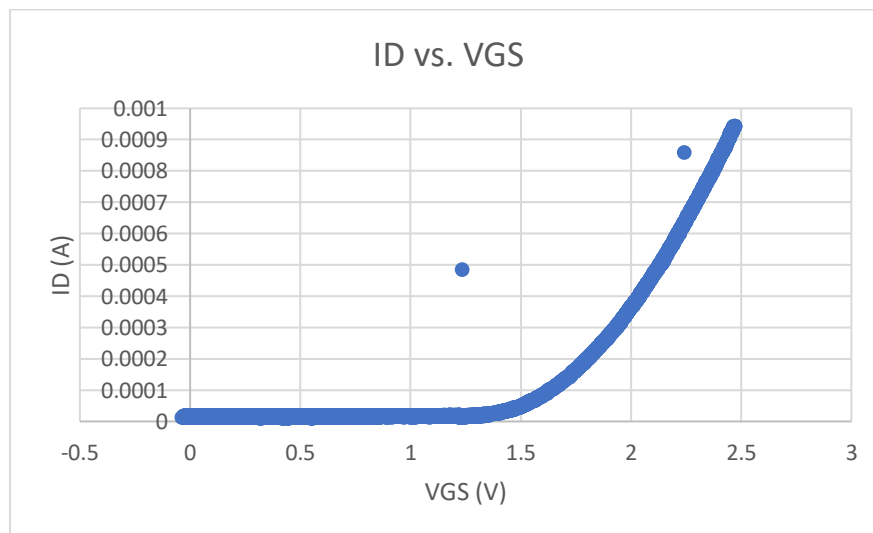


Figure 16: Plot of I_D vs. V_{GS} ▲

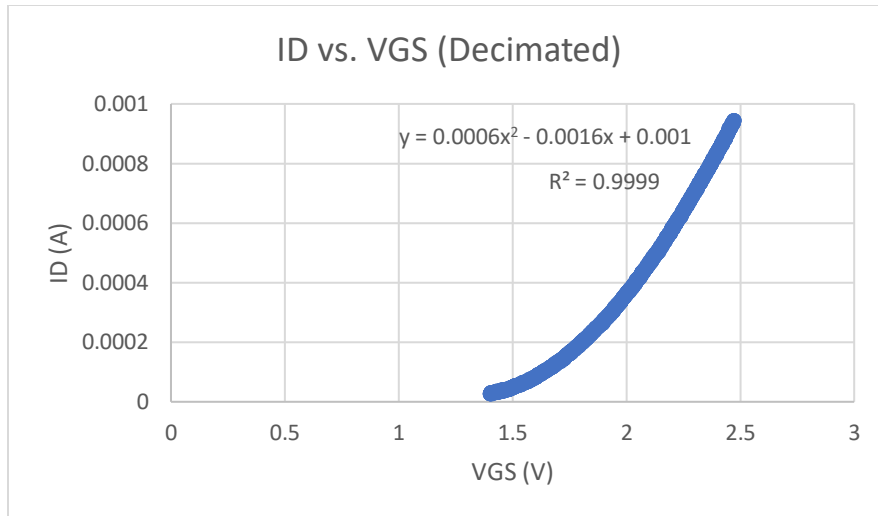


Figure 17: Plot of decimated I_D vs. decimated V_{GS} ▲

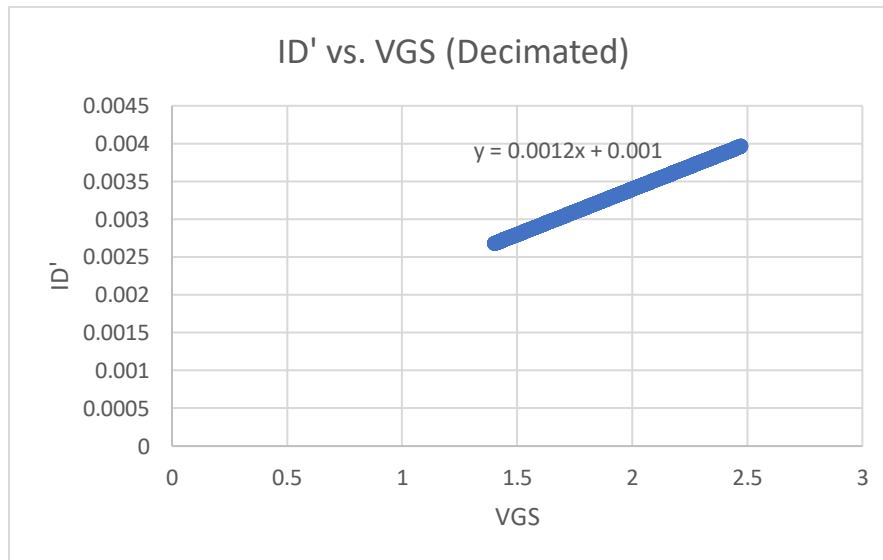


Figure 18: Plot of decimated $\frac{dI_D}{dV_{GS}}$ vs. decimated V_{GS} ▲

$$\beta = 0.0012 \text{ A/V}^2, V_t = 1.4\text{V}$$

(3) PMOS using CD4007P

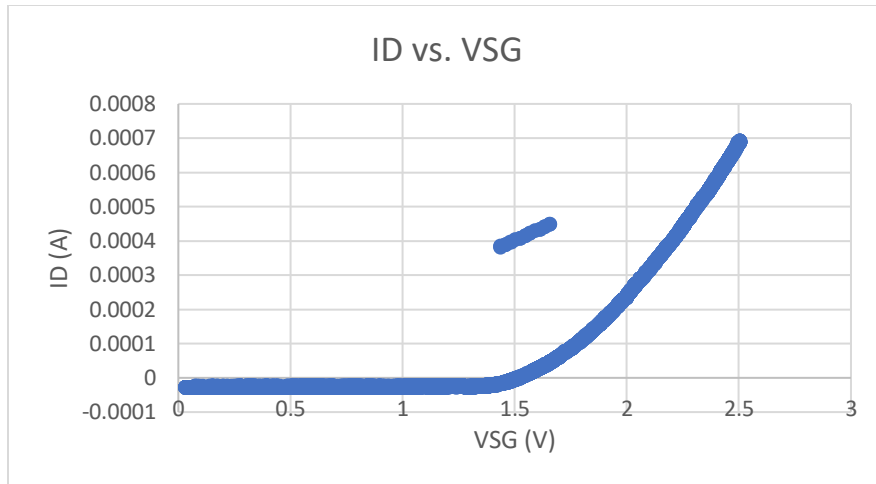


Figure 19: Plot of I_D vs. V_{SG} ▲

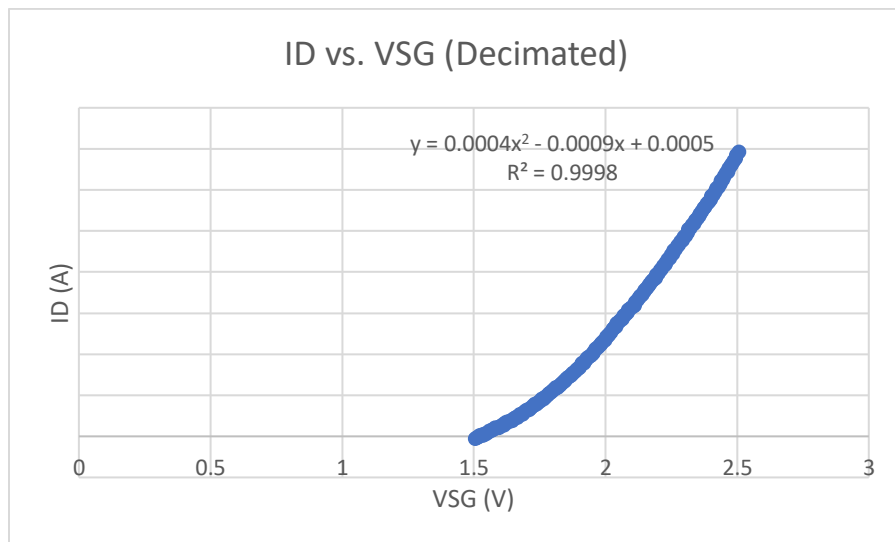


Figure 20: Plot of decimated I_D vs. decimated V_{SG} ▲

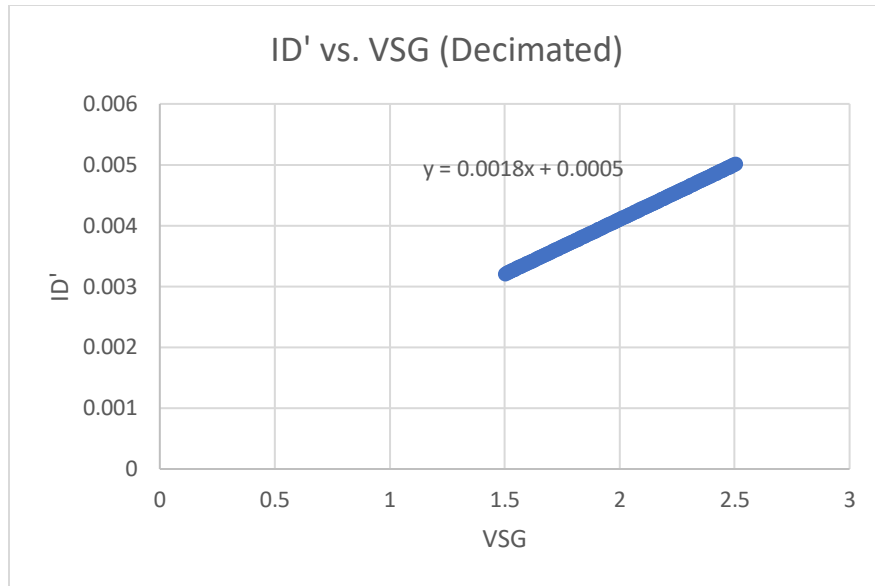


Figure 21: Plot of decimated $\frac{dI_D}{dV_{SG}}$ vs. decimated V_{SG} ▲

$$\beta = 0.0018 \text{ A/V}^2, V_t = 1.5\text{V}$$

Table

	Simulation		Measurement	
	β (A/V ²)	V _t (V)	β (A/V ²)	V _t (V)
2N7000G	0.086	2.23	0.023	1.84
CD4007N	0.001	1.5	0.0012	1.4
CD4007P	0.001	1.5	0.0018	1.5

Comment

In the prelab simulation, I used $\beta = 0.001\text{A/V}^2$ and $V_t = 1.5\text{V}$. For both CD4007N and CD4007P, the simulation and measurement values are similar. For 2N7000G, the simulation value and measurement value are kind of different. This might due to the real-world component has others factors that affect the output values.