

Pre-Lab 10:

Characterization of the MOSFET

Name: Wan-Yu Liao

ECEN 325 Section 514

TA: Mandela

Date: November 7, 2019

Simulations

(1) NMOS using 2N7000G

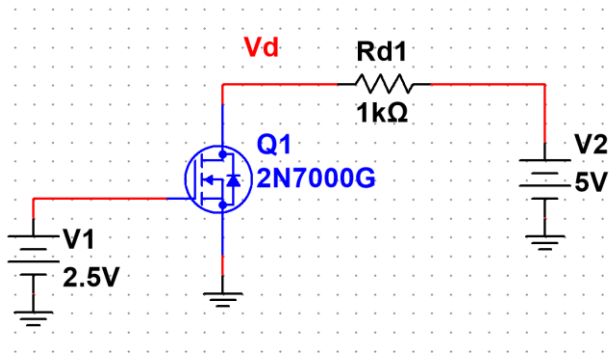


Figure 1: Schematic for NMOS using 2N7000G ▲

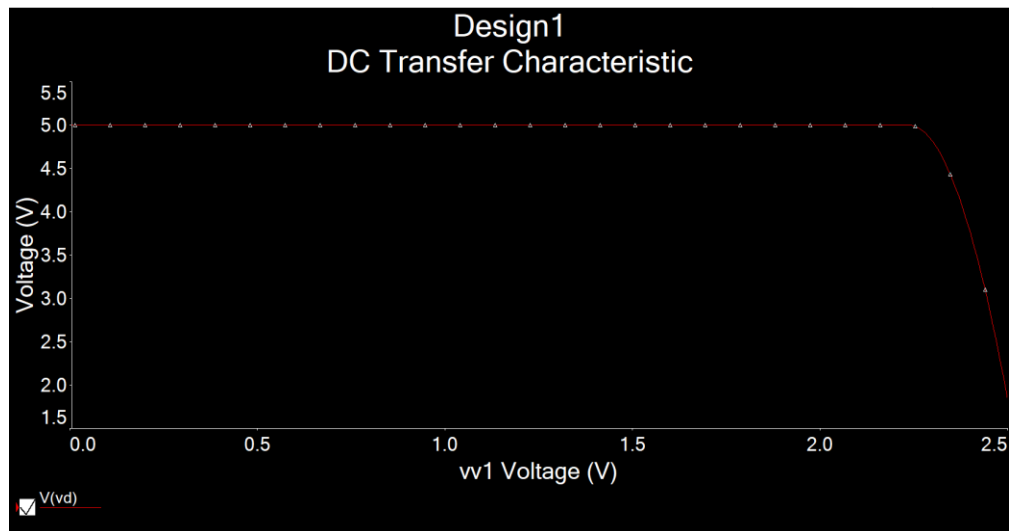


Figure 2: Simulation of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V ▲

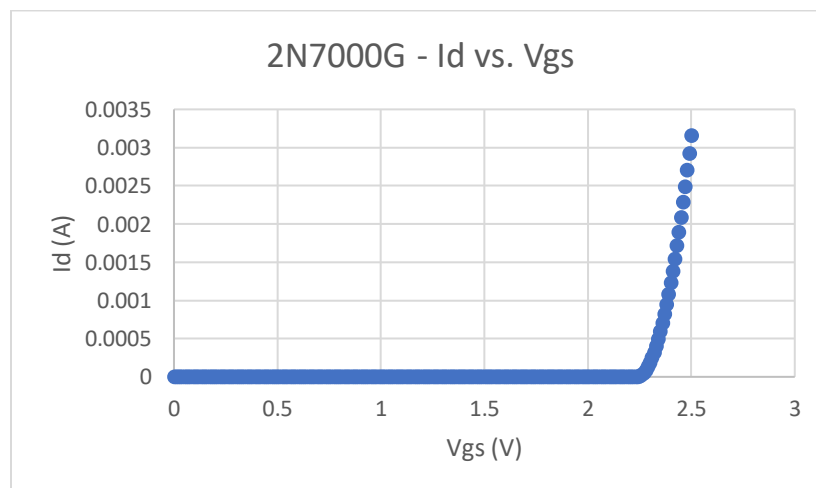


Figure 3: Excel plot of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V, where $I_d = (5 - V_d)/1000$ ▲

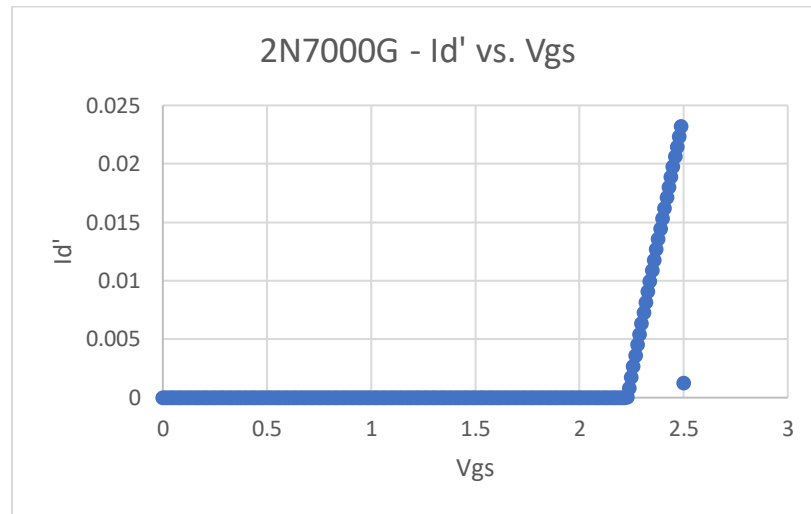


Figure 4: Excel plot of NMOS characterization of derivative of Id' vs. Vgs ▲

Threshold Voltage $V_t = 2.23V$

Transconductance parameter = $(0.023218 - 0)/(2.5 - 2.23) = 0.086$

(2) NMOS using CD4007N

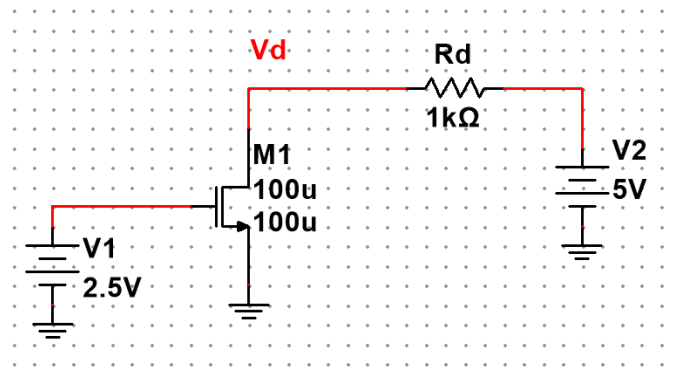


Figure 5: Schematic for NMOS using CD4007N ($\beta = 102\text{mA/V}^2$, $V_{TN} = 2.0V$) ▲

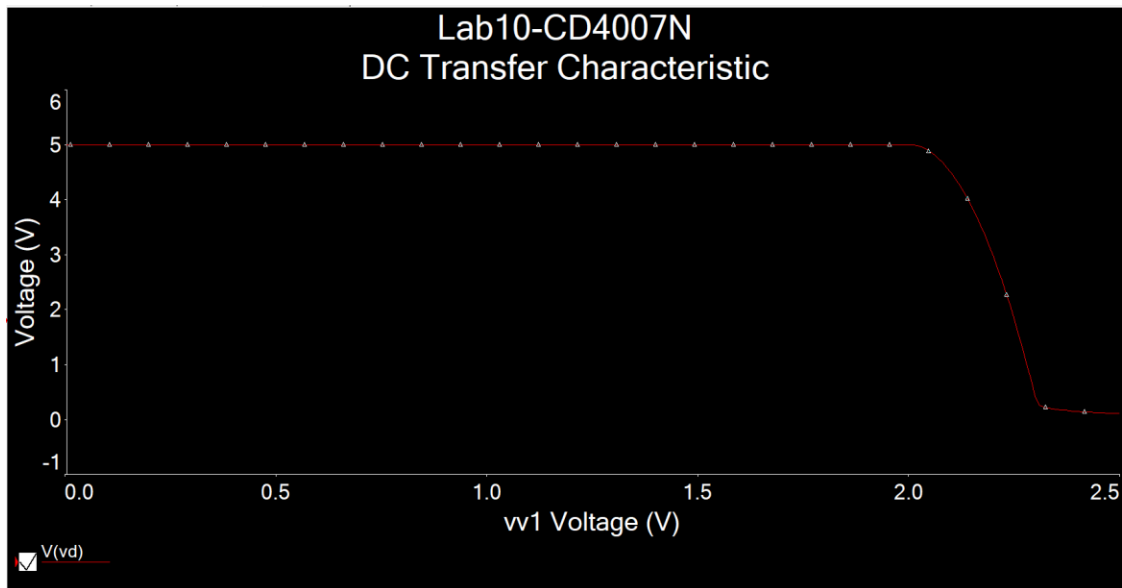


Figure 6: Simulation of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V ▲

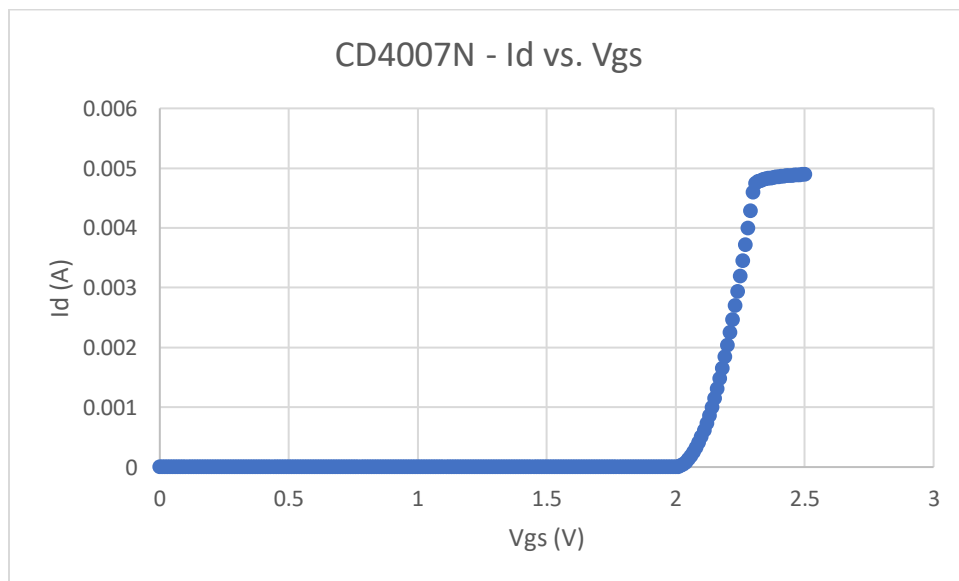


Figure 7: Excel plot of NMOS characterization circuit using DC sweep of V1 from 0 to 2.5V, while V2 = 5V, where $I_d = (5 - V_d)/1000$ ▲

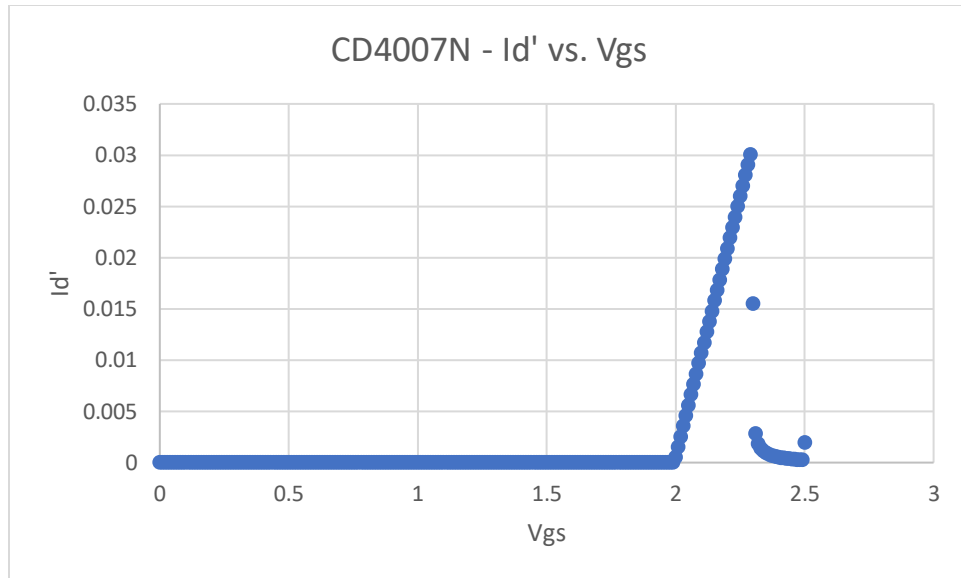


Figure 8: Excel plot of NMOS characterization of derivative of Id' vs. Vgs ▲

Threshold Voltage $V_t = 2\text{V}$

Transconductance parameter = $(0.03009-0)/(2.3-2) = \mathbf{0.1003}$

(3) PMOS using CD4007P

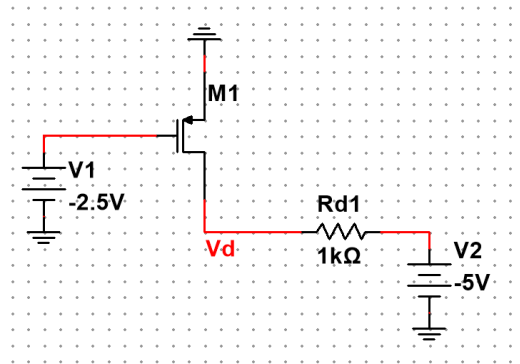


Figure 9: Schematic for PMOS using CD4007P ($\beta=102\text{mA/V}^2$, $V_{TN}=2.0\text{V}$) ▲

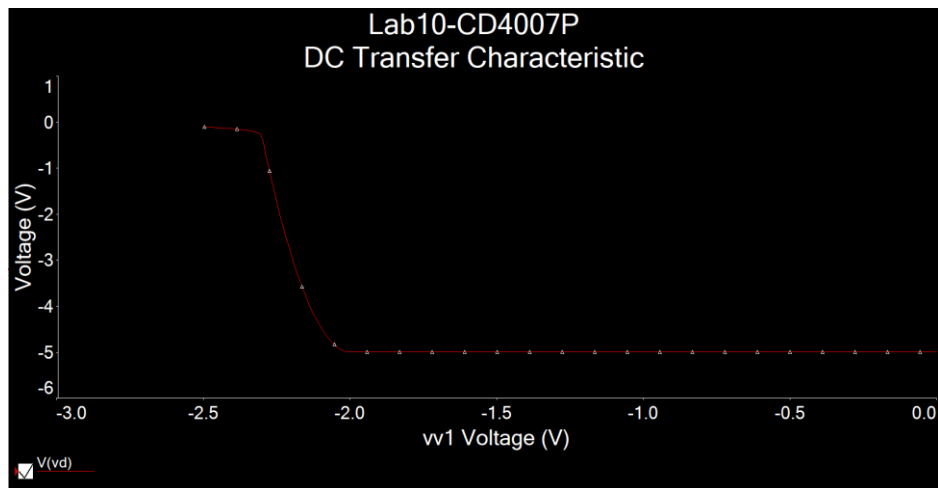


Figure 10: Simulation of PMOS characterization circuit using DC sweep of V1 from -2.5 to 0V, while V2 = -5V ▲

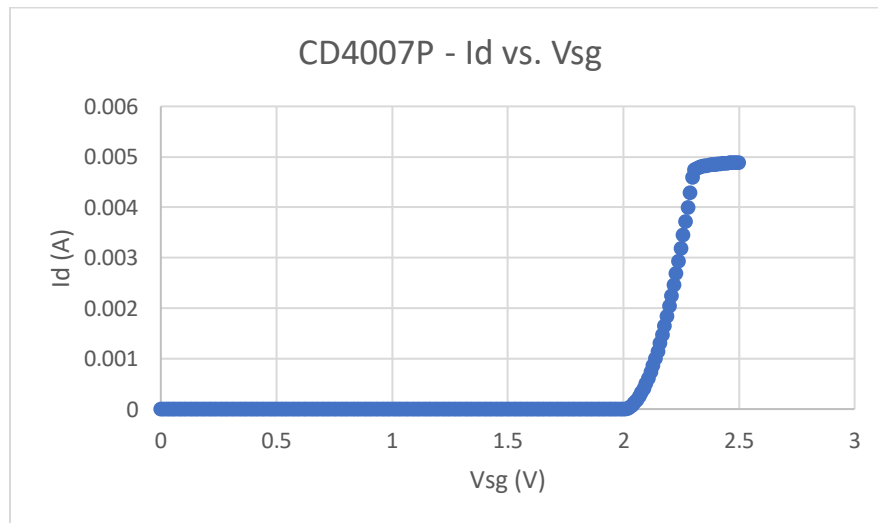


Figure 11: Excel plot of PMOS characterization circuit using DC sweep of V1 from -2.5 to 0V, while V2 = -5V, where $I_d = (V_d + 5)/1000$ ▲

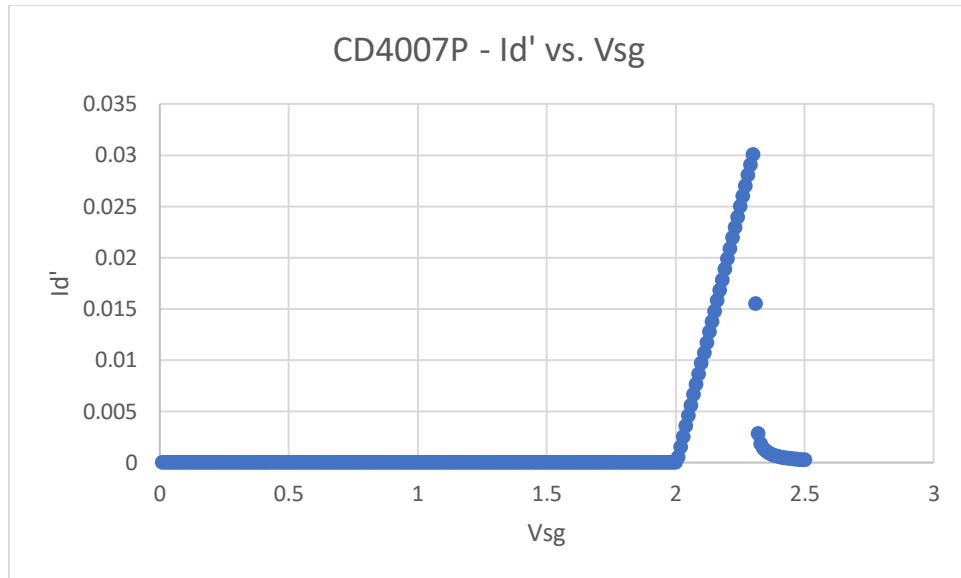


Figure 12: Excel plot of PMOS characterization of derivative of Id' vs. Vgs ▲

Threshold Voltage $V_t = 2.01V$

Transconductance parameter = $(0.03009-0)/(2.3-2.01) = 0.1037$