

Lab 4:

Operational Amplifiers – Part II

Name: Wan-Yu Liao

ECEN 325 Section 514

TA: Mandela

Lab Date: September 27, 2019

Lab Report Due Date: September 30, 2019

Calculations

(1)

$$V_o = - \left(\frac{R_3}{R_1} V_{i1} + \frac{R_3}{R_2} V_{i2} \right) = - (V_{i1} + 2V_{i2}) , \quad R_3 = 15 \text{ k}\Omega$$

$$\frac{R_3}{R_1} = 1 \Rightarrow R_1 = 15 \text{ k}\Omega \quad \frac{R_3}{R_2} = 2 \Rightarrow R_2 = 7.5 \text{ k}\Omega$$

(2)

$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}) = V_{i2} - V_{i1} , \quad R_2 = R_3 = R_4 = 10 \text{ k}\Omega$$

$$\frac{R_2}{R_1} = 1 \Rightarrow R_1 = 10 \text{ k}\Omega$$

(3)

$$V_o = \left(1 + \frac{2R}{R_{\text{gain}}} \right) (V_{i2} - V_{i1}) = 3(V_{i2} - V_{i1}) , \quad R_{\text{gain}} = 1 \text{ k}\Omega$$

$$1 + \frac{2R}{R_{\text{gain}}} = 3 \Rightarrow \frac{2R}{1 \text{ k}\Omega} = 2 \Rightarrow R = 1 \text{ k}\Omega$$

(4)

$$V_{i1} = 0.2 \sin(2\pi 1000t) , \quad V_{i2} = 0.3 \text{ V}$$

$$\text{Circuit 1} : V_o = - (V_{i1} + 2V_{i2}) = -0.2 \sin(2\pi 1000t) - 0.6$$


$$\text{Circuit 2} : V_o = V_{i2} - V_{i1} = 0.3 - 0.2 \sin(2\pi 1000t)$$

$$\text{Circuit 3} : V_o = 3(V_{i2} - V_{i1}) = 0.9 - 0.6 \sin(2\pi 1000t)$$


Simulations

Circuit 1 (Summing Amplifier):

(a)

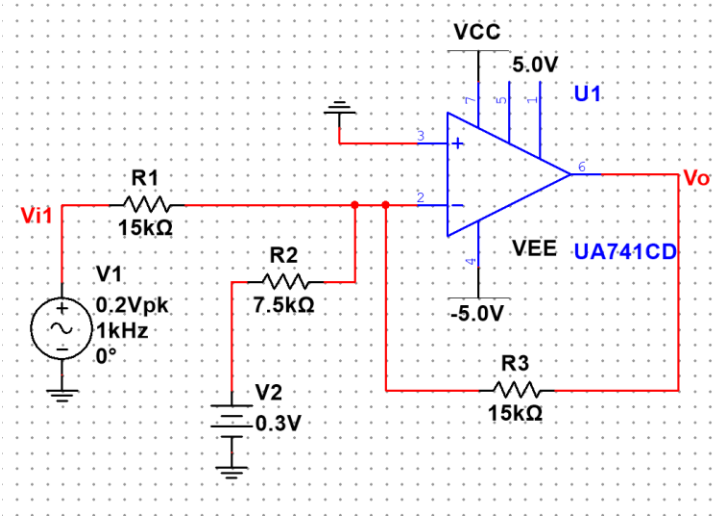

(b)

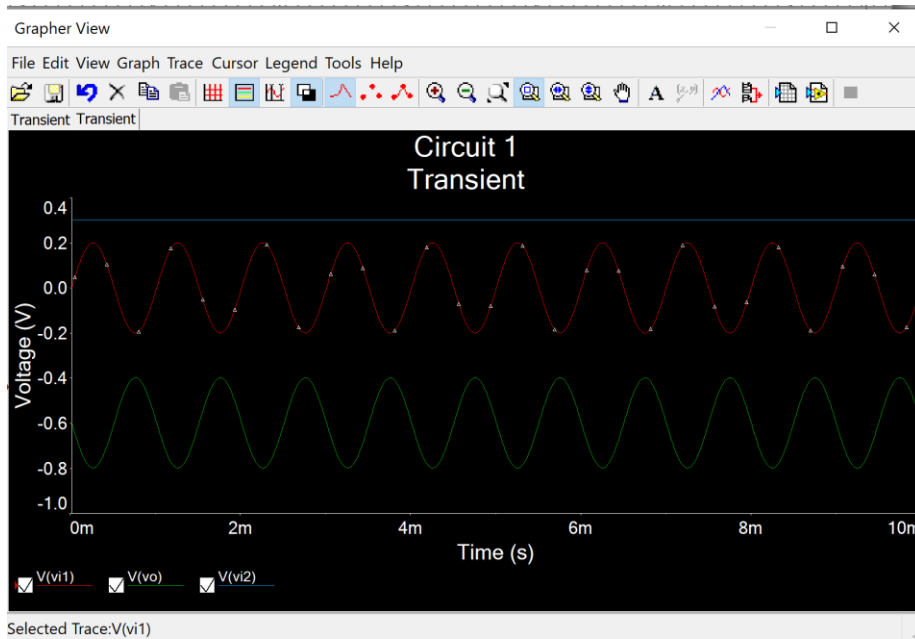


$$V_{i1} = 0.2 \sin(2\pi 1000t)$$


$v_o = -0.2 \sin(2\pi 1000t) - 0.6$, which is opposite the V_{i1} and shift down by 0.6.

Circuit 2 (Differential Amplifier):

(a)

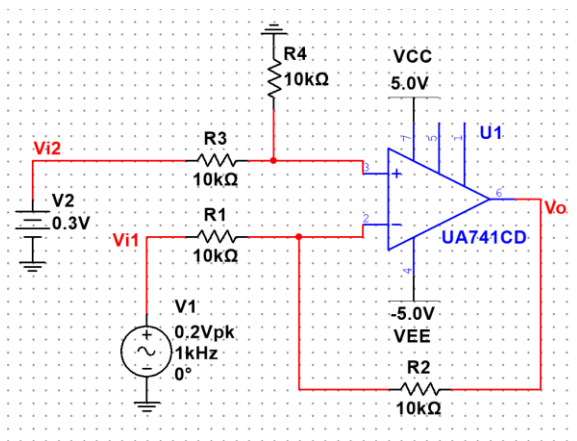

(b)

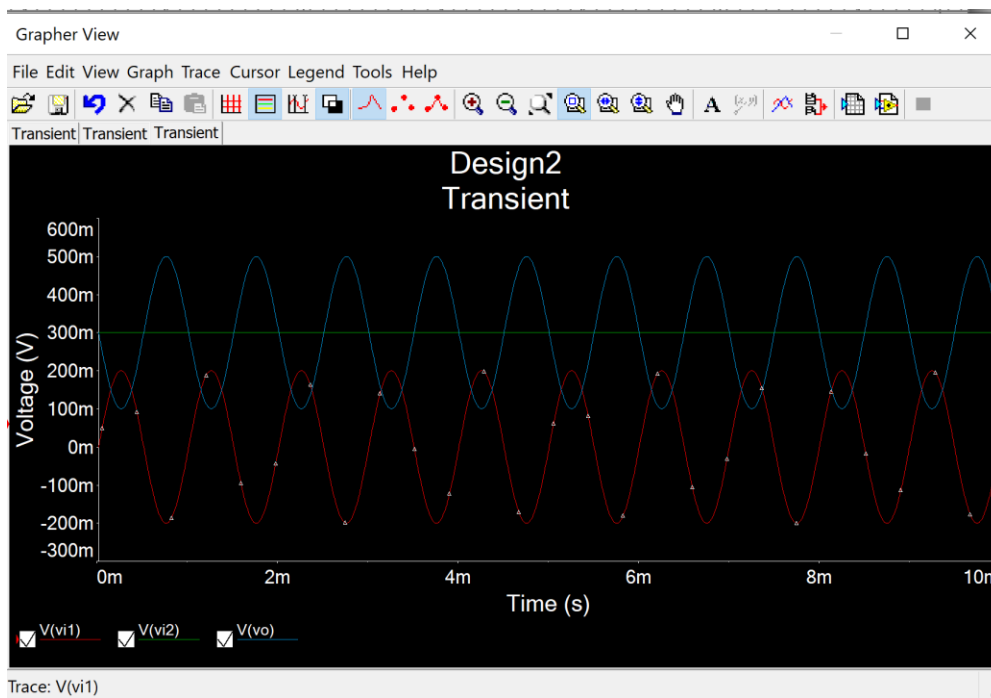


$$V_{i1} = 0.2 \sin(2\pi 1000t)$$


$$v_0 = -0.2 \sin(2\pi 1000t) + 0.3 \quad , \text{ which is opposite the } V_{i1} \text{ and shift up by } 0.3.$$

Circuit 3 (Instrumentation Amplifier):

(a)

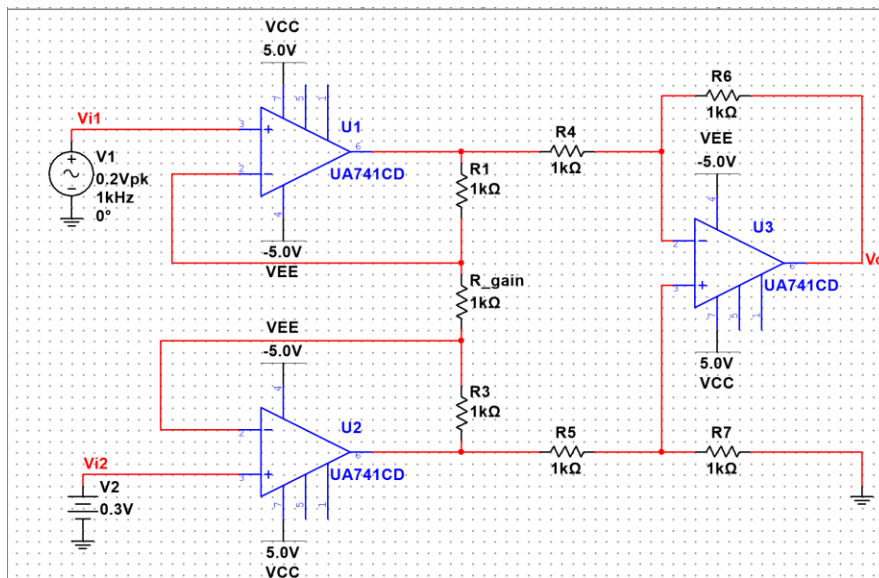

(b)

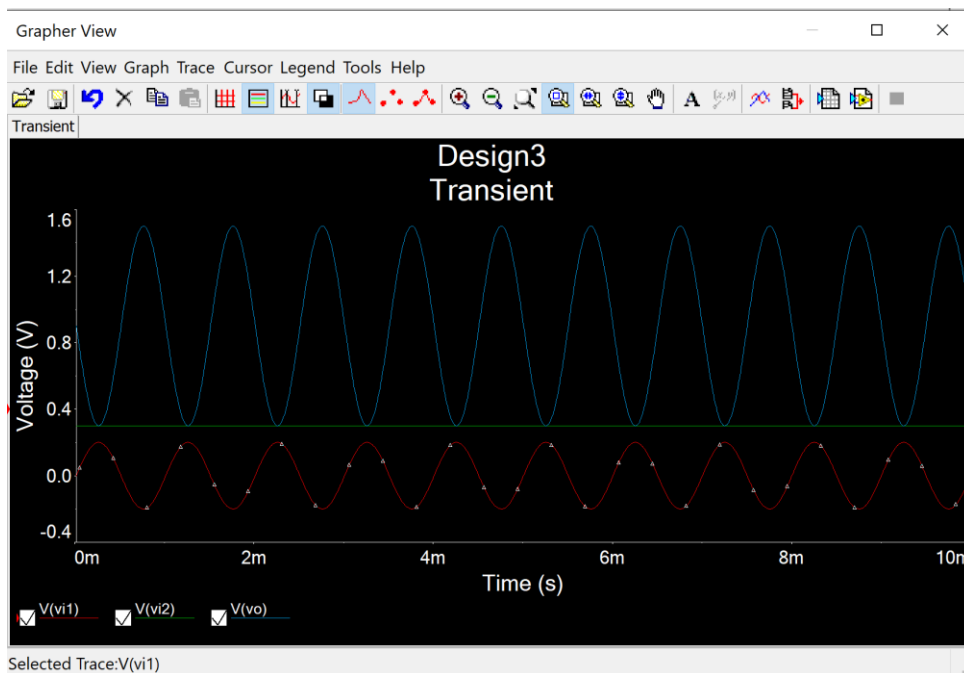

$$V_{i1} = 0.2 \sin(2\pi 1000t)$$

$$v_o = -0.6 \sin(2\pi 1000t) + 0.9$$


which is opposite the V_{i1} with amplitude of 0.6 and shift up by 0.9.

Measurements

Circuit 1 (Summing Amplifier):


Time-Domain Waveform

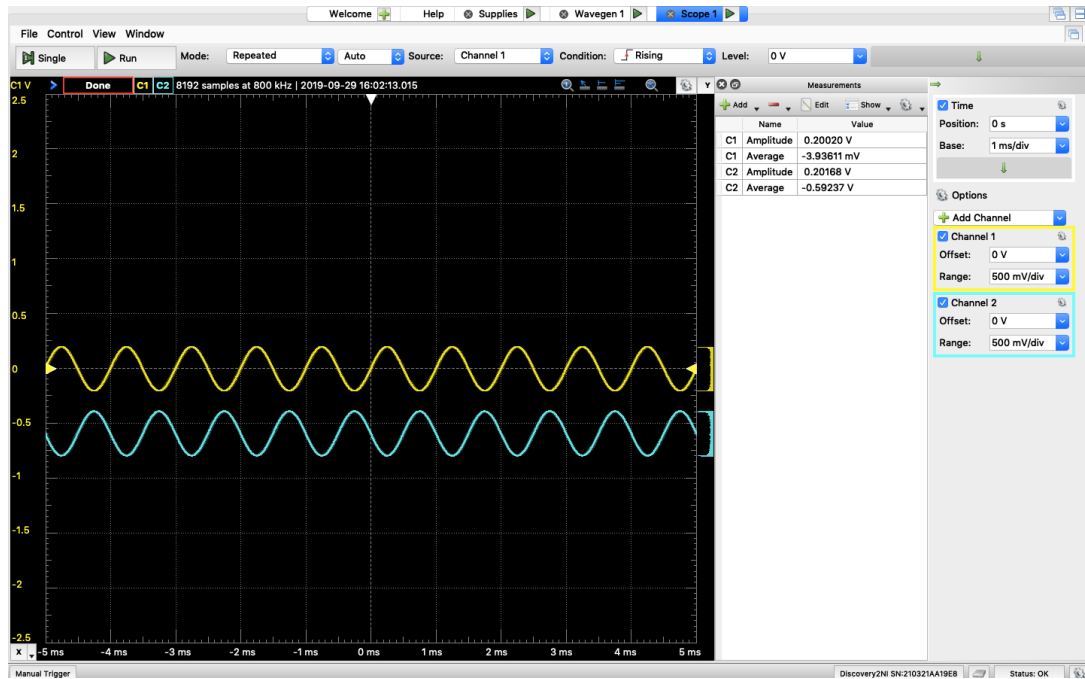V_o (C2) shifted down 0.6 and is opposite to V_i (C1).




Clipping Waveform Generator

$$V_2 = 1.5V$$

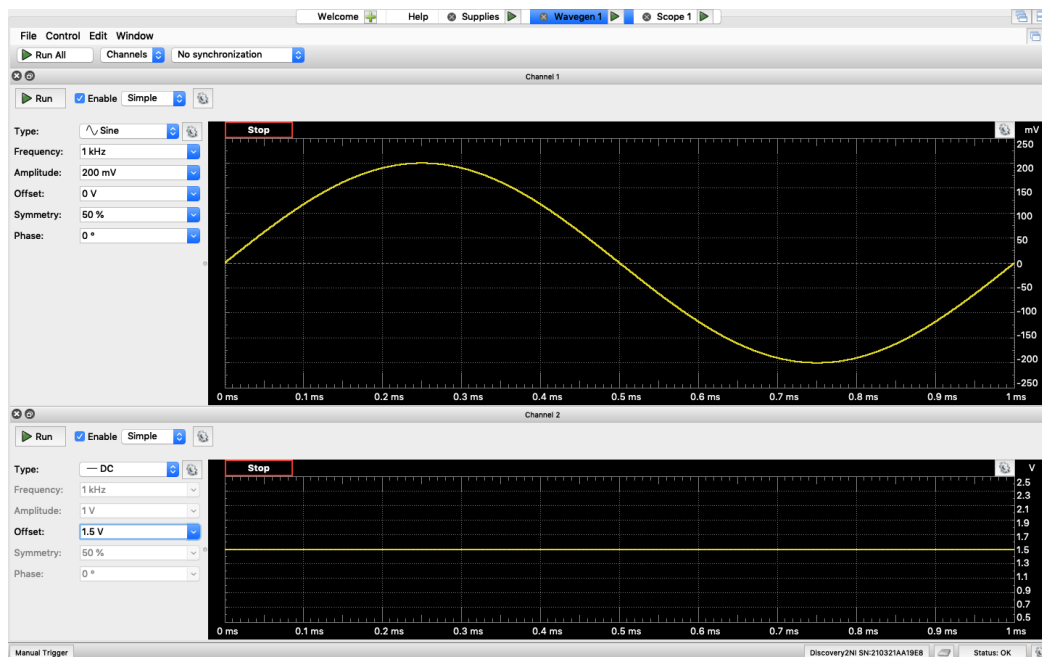


Clipping Time-Domain Waveform

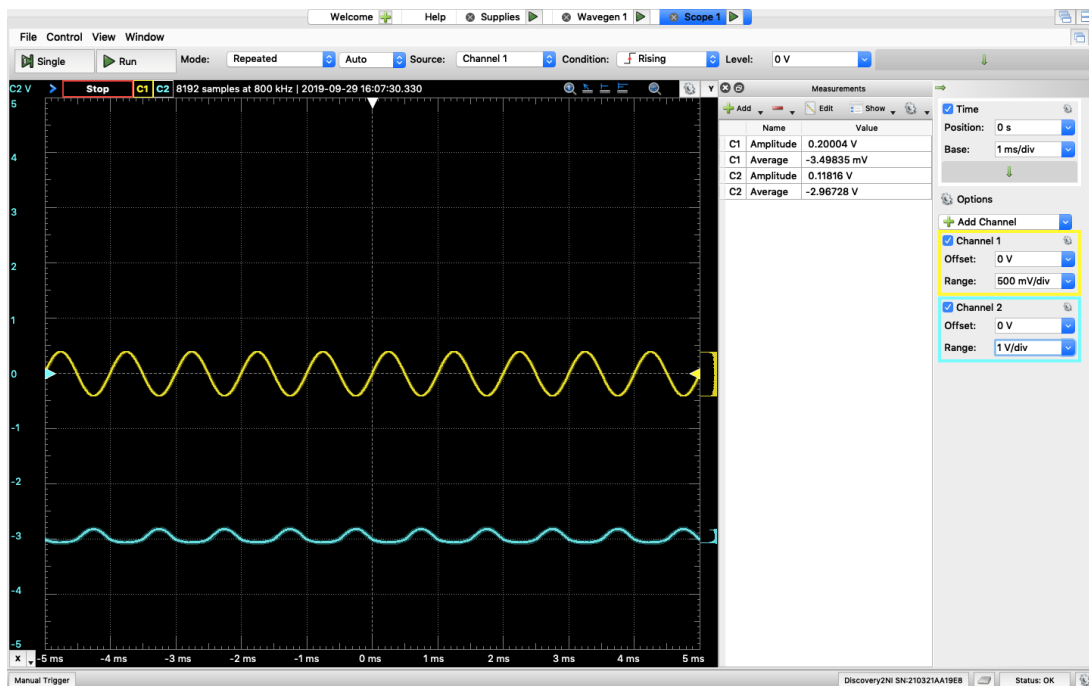

Circuit 2 (Differential Amplifier):


Time-Domain Waveform

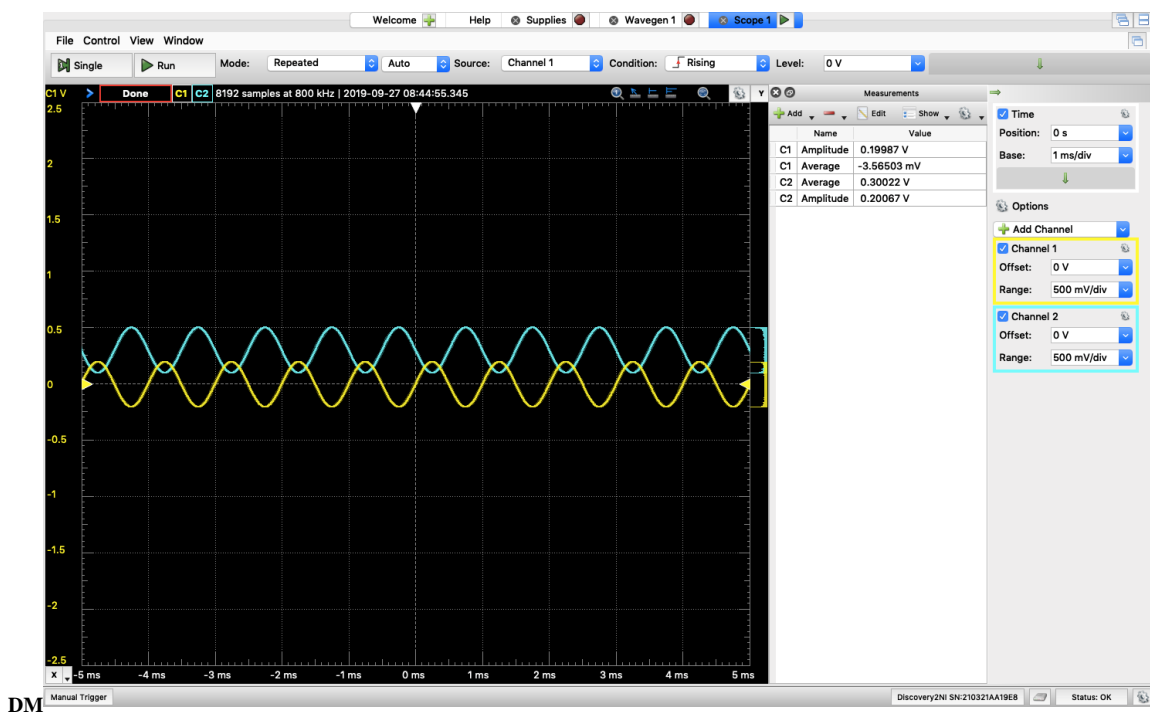V_o (C1) shifted up 0.3 and opposite to V_i (C2).




ADM Time-Domain Waveform
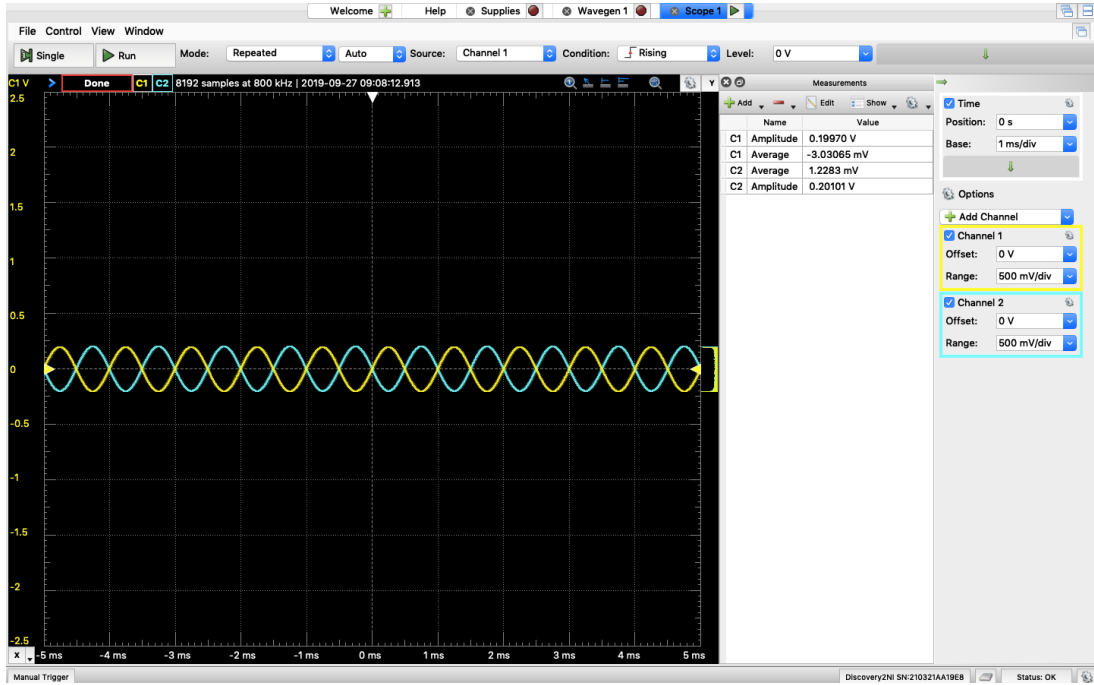
$$A_{DM} = \frac{V_{out}}{V_{in}} = \frac{0.201}{0.200} = 1.005$$



ACM Time-Domain Waveform
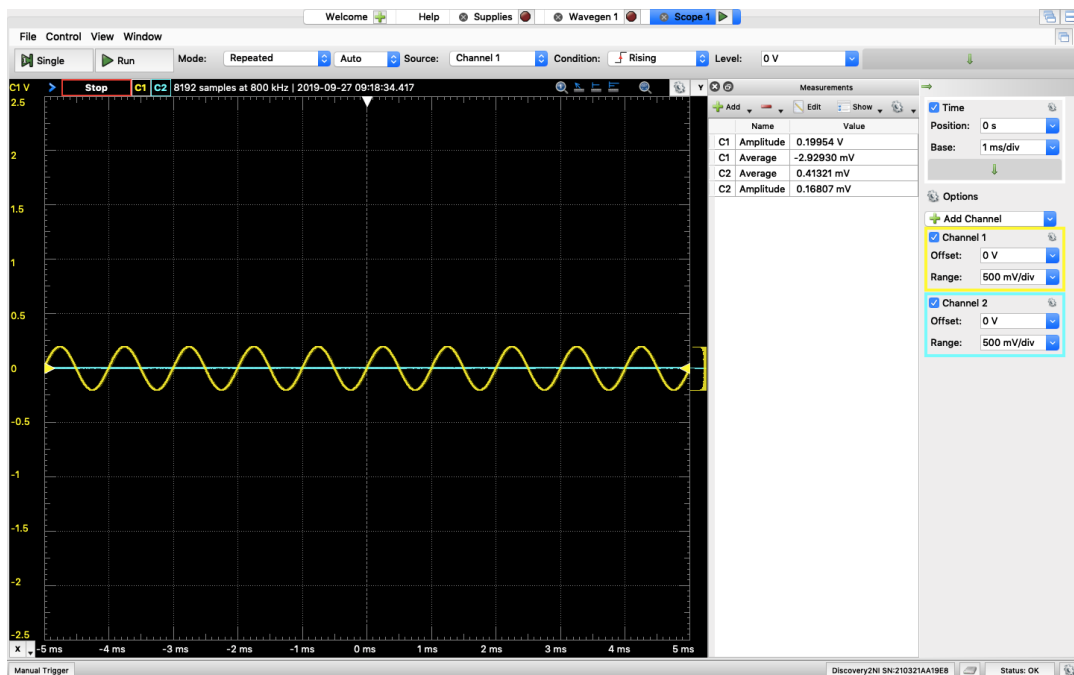
$$A_{CM} = \frac{V_{out}}{V_{in}} = \frac{0.168 * 10^{-3}}{0.199} = 0.000844$$




$$CMRR = \frac{A_{DM}}{A_{CM}} = \frac{1.005}{0.000844} = 1190.76$$

Circuit 3 (Instrumentation Amplifier):

Time-Domain Waveform

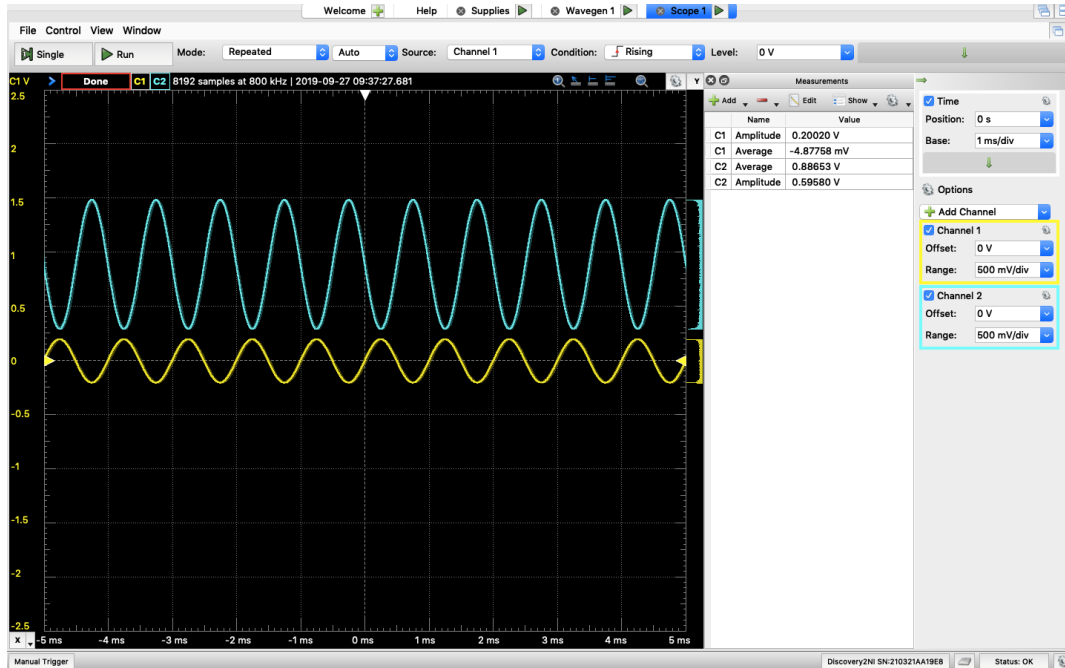V_o (C2) shifted up 0.9 and is opposite to V_i (C1) and the amplitude increase to 0.6.



Saturated Point for UA741 (Extra Question):

Positive $V_{sat} = 4.381V$

Negative $V_{sat} = -3.129V$

Tables

	Amplitude	Average	Opposite to V_1
Circuit 1 Calculated	0.2	-0.6	Yes
Circuit 1 Simulated	0.2	-0.6	Yes
Circuit 1 Measurement	0.202	-0.592	Yes
Circuit 2 Calculated	0.2	0.3	Yes
Circuit 2 Simulated	0.2	0.3	Yes
Circuit 2 Measurement	0.201	0.300	Yes
Circuit 3 Calculated	0.6	0.9	Yes
Circuit 3 Simulated	0.6	0.9	Yes
Circuit 3 Measurement	0.596	0.886	Yes

Comments

The results from calculated part, simulated part, and measurement part are similar. The slightly different for measurement results are due to the real-world amplifiers and resistors have some tolerance.

CMRR value calculated in Circuit 2 Measurement part is 1190.76. The ideal CMRR value supposed to be infinity, A_{DM} supposed to be 1, and A_{CM} supposed to be 0. However, in real-world, A_{DM} can only be close to 1, and A_{CM} can only be close to 0. Therefore, CMRR value cannot be infinity but it would be a large value.