

# **Pre-Lab 9:**

## **BJT Amplifier Design**

Name: Wan-Yu Liao

ECEN 325 Section 514

TA: Mandela

Date: November 1, 2019

## Calculation

$$V_{RE} = 1.2V, \hat{V}_D = 1.2V, R_L = 100, A_V = 20, \beta = 200, N = 20, R_i = 1.2k\Omega$$

$$5 - 1.2 - 1.2 - 0.3 \geq V_{RC} \geq 1.2 \Rightarrow V_{RC} = 2.3V$$

$$\frac{2.3 - 0.7 - 1.2}{R_H} \geq \frac{1.2}{100} \Rightarrow 33.33 \geq R_H \Rightarrow R_H = 33.33\Omega$$

$$I_{C2} = \frac{2.3 - 0.7}{33.33} = 0.048 = 48mA$$

$$\frac{20 - 0.048}{200} \leq I_{C1} \leq \frac{200}{1.2k} \frac{1}{\frac{20}{1.2 + 0.7} + \frac{20}{5 - 1.2 - 0.7} + \frac{20}{2.3}} \Rightarrow 48mA \leq I_{C1} \leq 6.49mA$$

$$I_{C1} = 5mA$$

$$R_C = \frac{2.3}{5mA} = 460\Omega \quad R_E = \frac{1.2}{5mA} = 240\Omega \quad r_{e1} = \frac{V_T}{I_E} = \frac{0.025 \cdot 240}{1.2} = 5$$

$$R_G = \frac{460}{20} - 5 = 23 - 5 = 18\Omega$$

$$R_{B1} = \frac{200(5 - 1.2 - 0.7)}{20 \cdot 5m} = 6.2k\Omega \quad R_{B2} = \frac{200(5 + 0.7)}{20 \cdot 5m} = 11.4k\Omega$$

$$A_{V2} = \frac{33.3 \parallel 100}{5 + (33.3 \parallel 100)} = 0.833$$

$$R_{i2} = (200 + 1)(5 + (33.3 \parallel 100)) = 6.029k\Omega$$

## Simulation

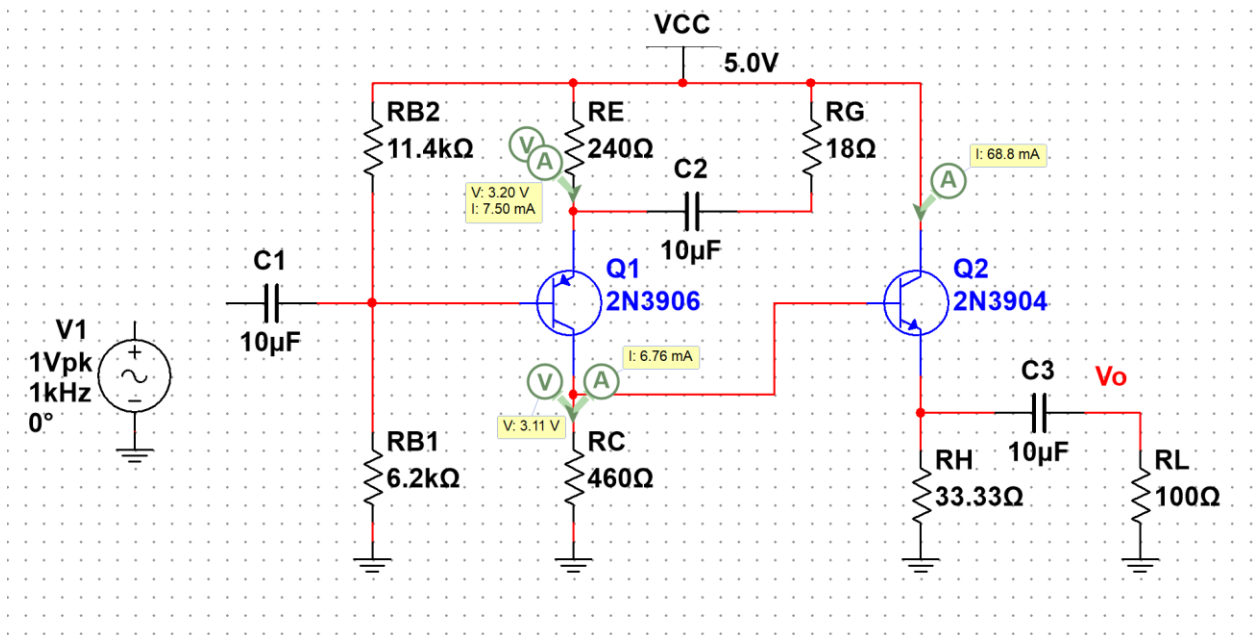


Figure 1: DC solutions

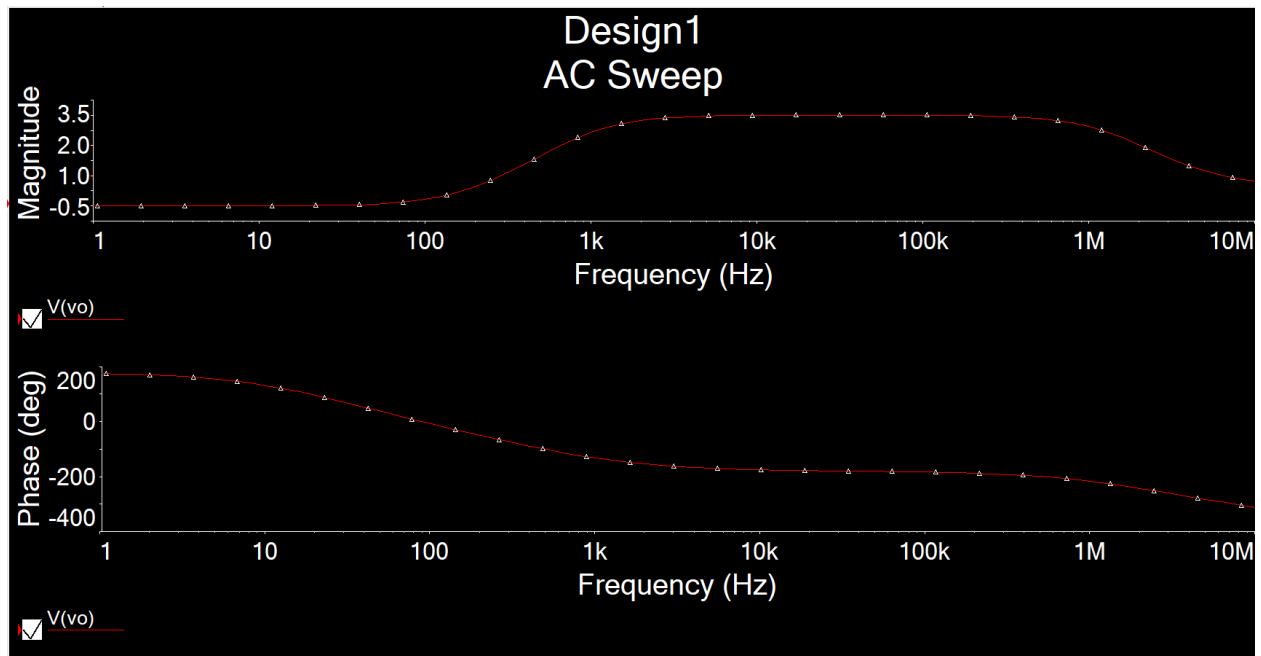


Figure 2-1: Av

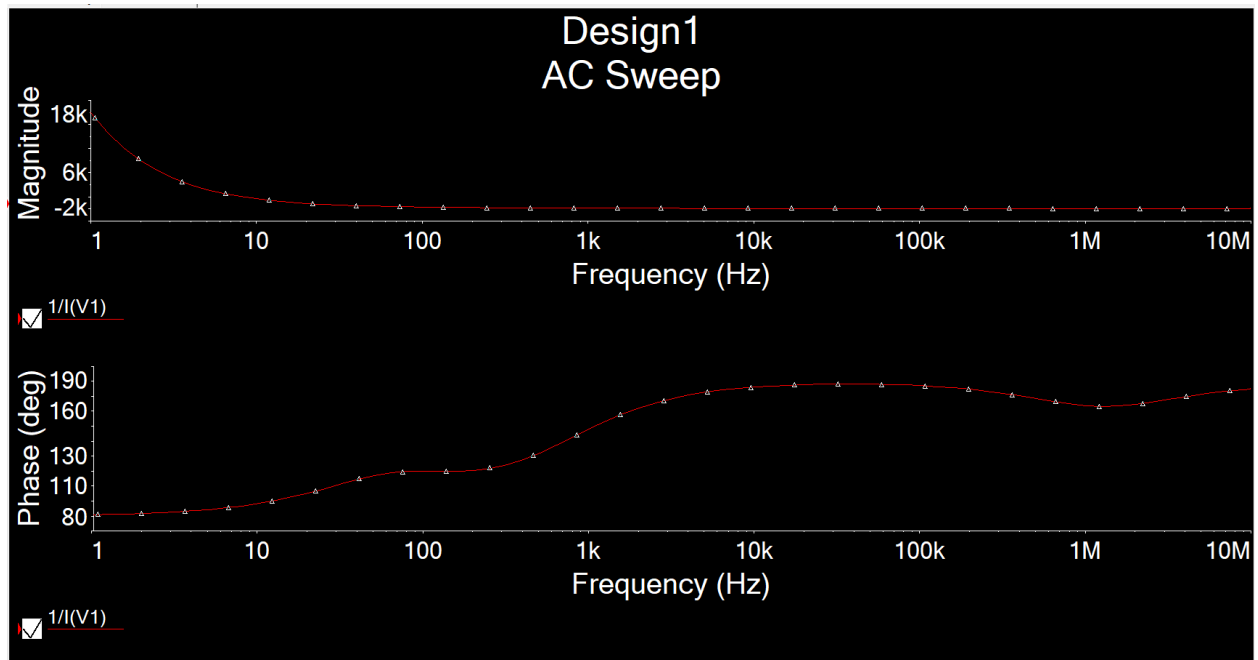


Figure 2-2: Ri

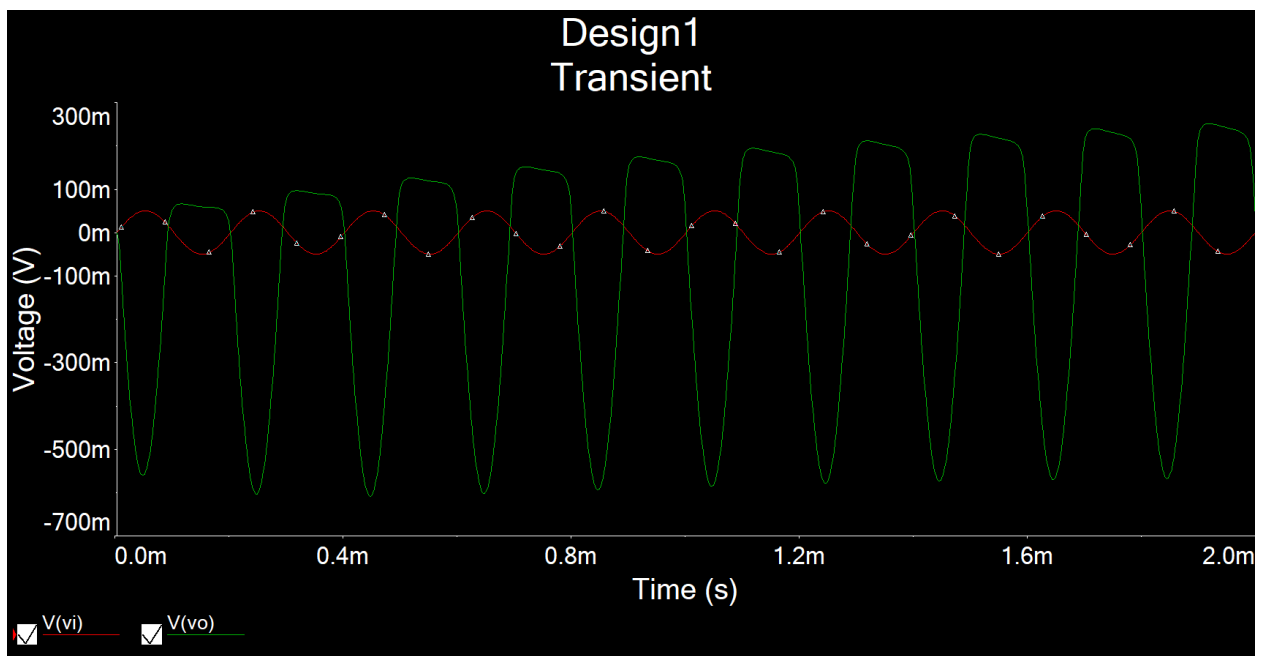


Figure 3: Time-domain waveform

(I've worked on the values of  $R_c$  but still can't find unclipped waveform)

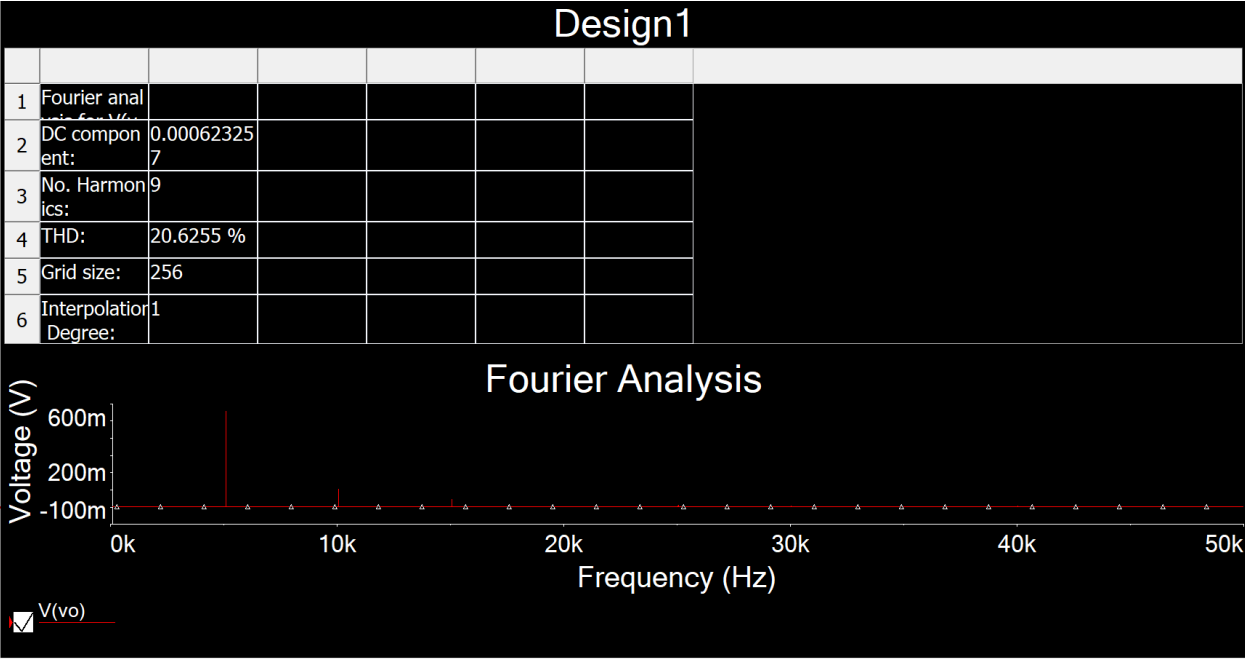


Figure 4: THD

(Since the time-domain waveform is off, the THD value is also off)