

Lab 3:

Second Order Circuit

Name: Wan-Yu Liao

ECEN 325 Section 514

TA: Mandela

Lab Date: September 20, 2019

Report Due Date: September 23, 2019


Calculation

1. Read the data sheet for the UA741 opamp and write down the typical values of the following parameters:

Supply Voltage:	5V to 15V -5V to -15V	Power Consumption:	50mW
Input Resistance:	2MΩ	Input Offset Voltage:	1mV
Output Resistance:	75Ω	Input Offset Current:	20nA
Voltage Gain:	106dB	Bandwidth:	1MHz
Slew Rate:	0.5V/μs		

2. Derive the voltage gains

Circuit A

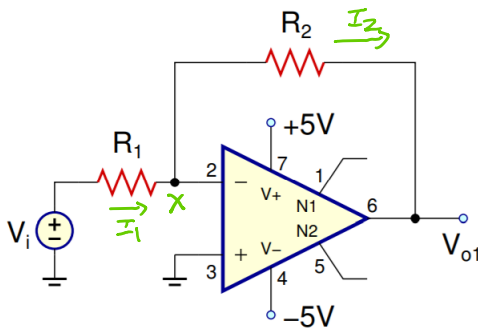


$$V_x = 0 \quad I_1 = I_2$$

$$\frac{V_i - V_x}{R_1} = \frac{V_x - V_{o1}}{R_2}$$

$$\boxed{\frac{V_{o1}}{V_i} = -\frac{R_2}{R_1}}$$

Circuit B

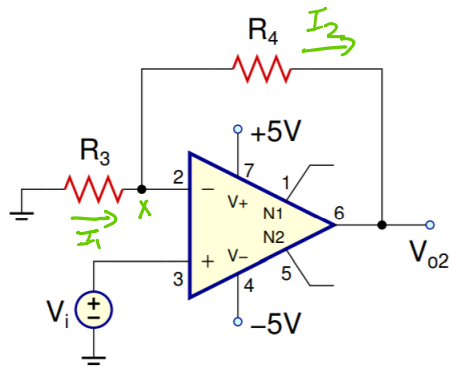


$$V_x = V_i$$

$$\frac{0 - V_x}{R_3} = \frac{V_x - V_{02}}{R_4}$$

$$\boxed{\frac{V_{02}}{V_i} = 1 + \frac{R_4}{R_3}}$$

Circuit C

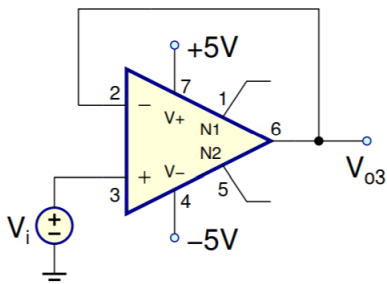

$$V_{03} = V_i$$

$$\boxed{\frac{V_{03}}{V_i} = 1}$$


3. If $R_1 = R_3 = 10\text{k}\Omega$, find R_2 and R_4 such that $V_{01}/V_i = -3$ and $V_{02}/V_i = 6$.

$$\frac{V_{01}}{V_i} = -\frac{R_2}{R_1} \Rightarrow -3 = -\frac{R_2}{10\text{k}} \Rightarrow \boxed{R_2 = 30\text{k}\Omega}$$


$$\frac{V_{02}}{V_i} = 1 + \frac{R_4}{R_3} \Rightarrow 6 = 1 + \frac{R_4}{10\text{k}} \Rightarrow \boxed{R_4 = 50\text{k}\Omega}$$

Simulations

Circuit A

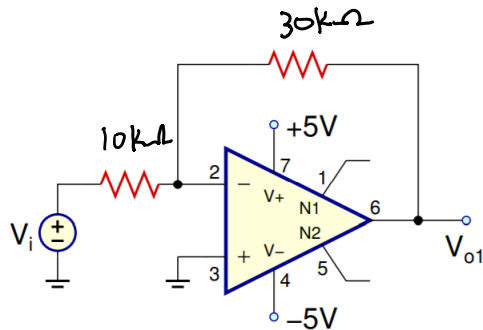


(a) Bode Plot

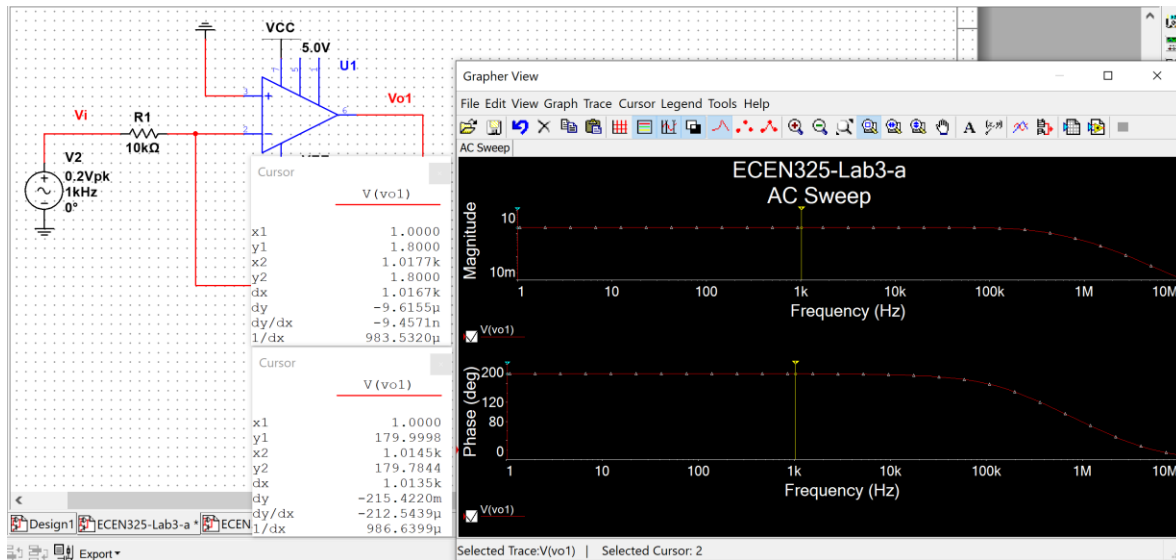

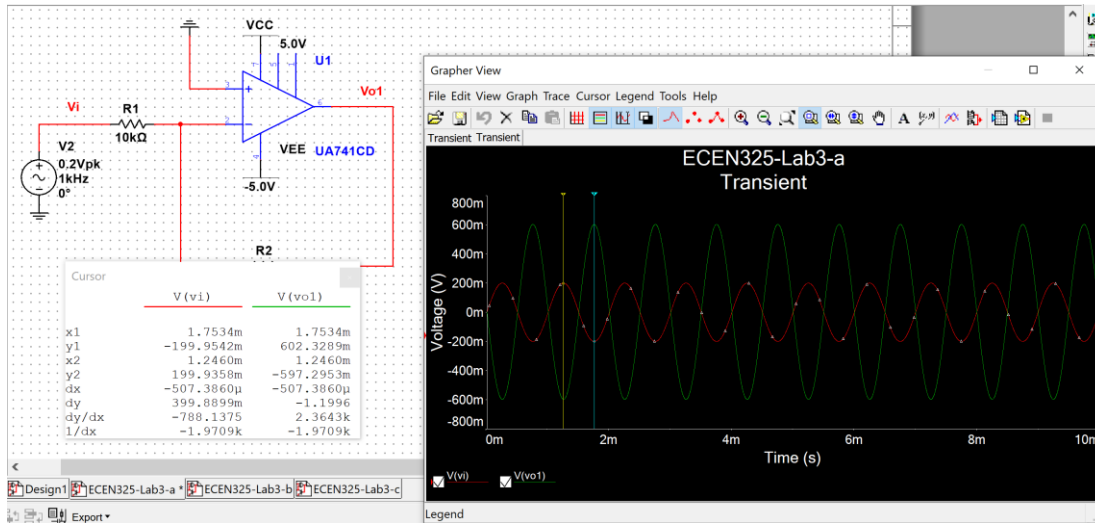
(b) Time-Domain Waveforms

This simulation is different from pre-lab because in the pre-lab, I connected the wrong vcc and vee to the op amp and I didn't get the correct graph.



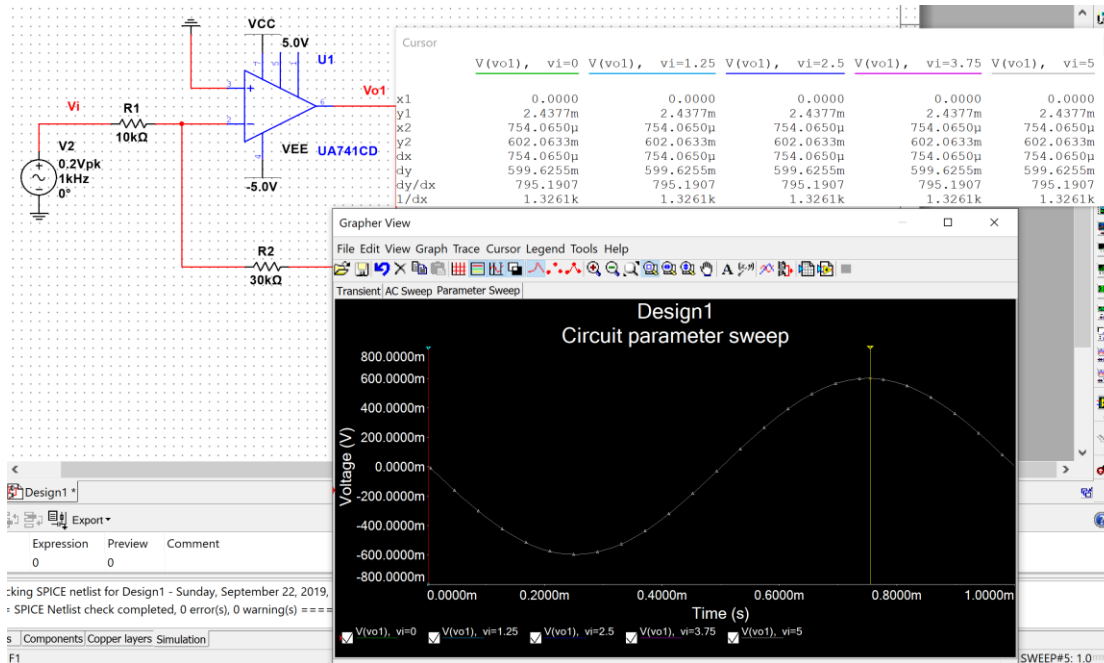
(c) Parameter Sweep

This graph is also different from the pre-lab. Maximum amplitude is 0.6V.




(d)

Applied $V_i(t) = 0.6 \sin(2\pi 1000t)$.

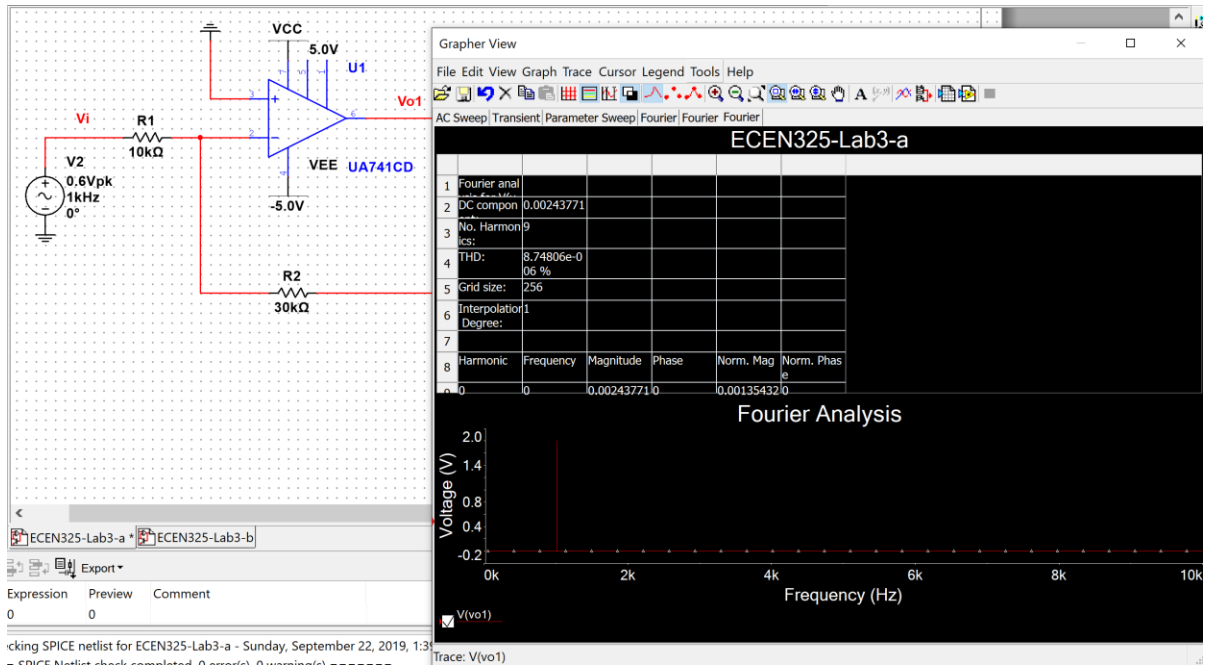


Circuit B

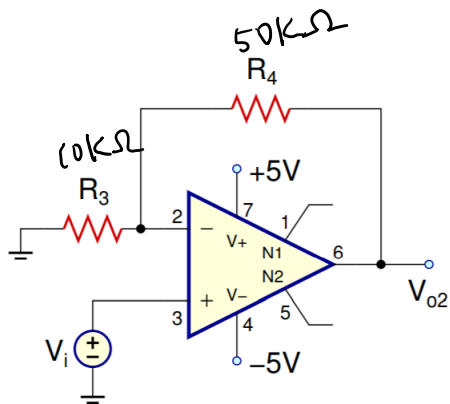


Simulation pictures for circuit B are all different from pre-lab because I used the wrong resistor value in pre-lab and connected the wrong vcc and vee in the pre-lab.

(a) Bode Plot

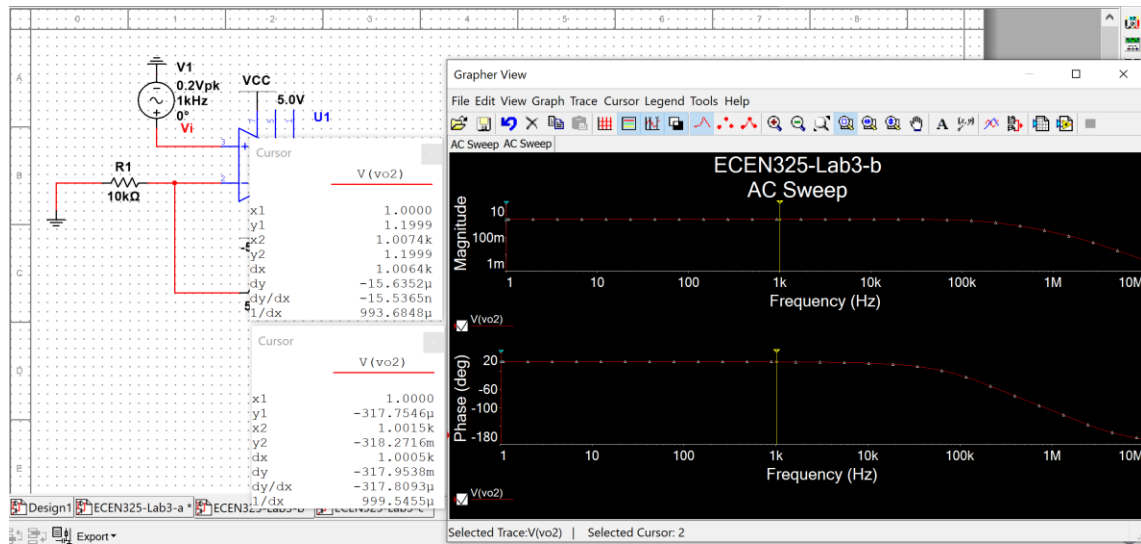


(b) Time-Domain Waveforms

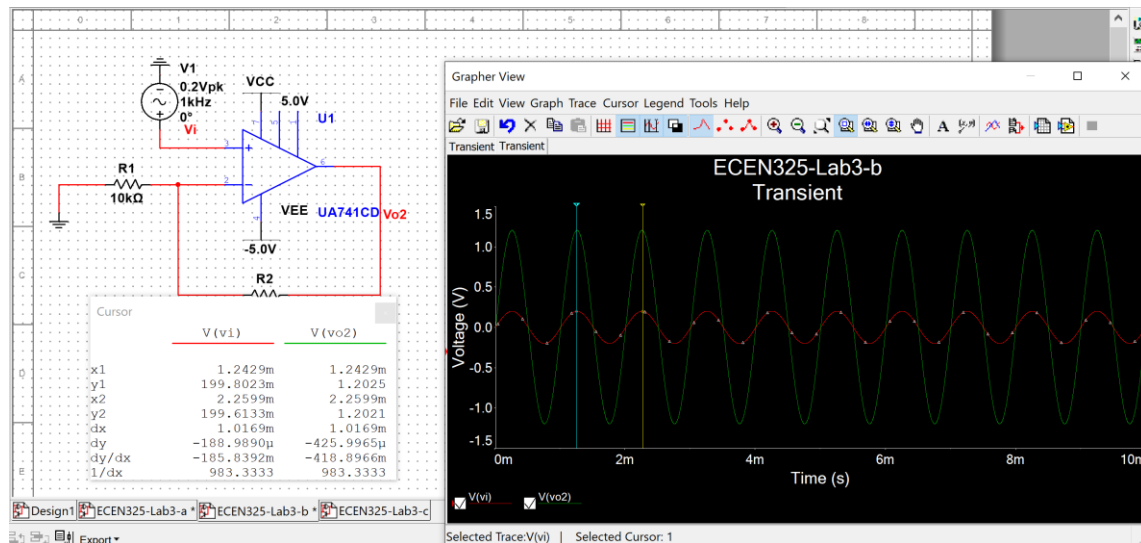


(c) Parameter Sweep

The max amplitude is about 1.2V.

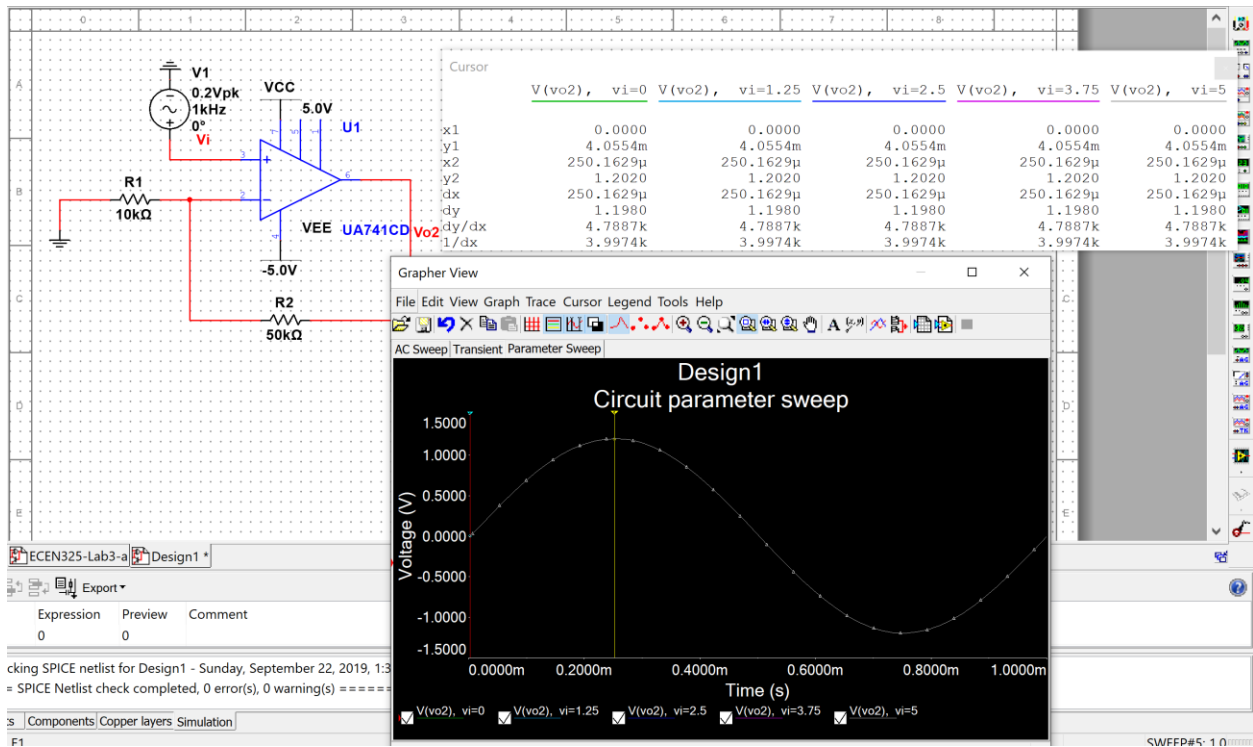


(d)

Applied $V_i(t) = 1.2 \sin(2\pi 1000t)$.

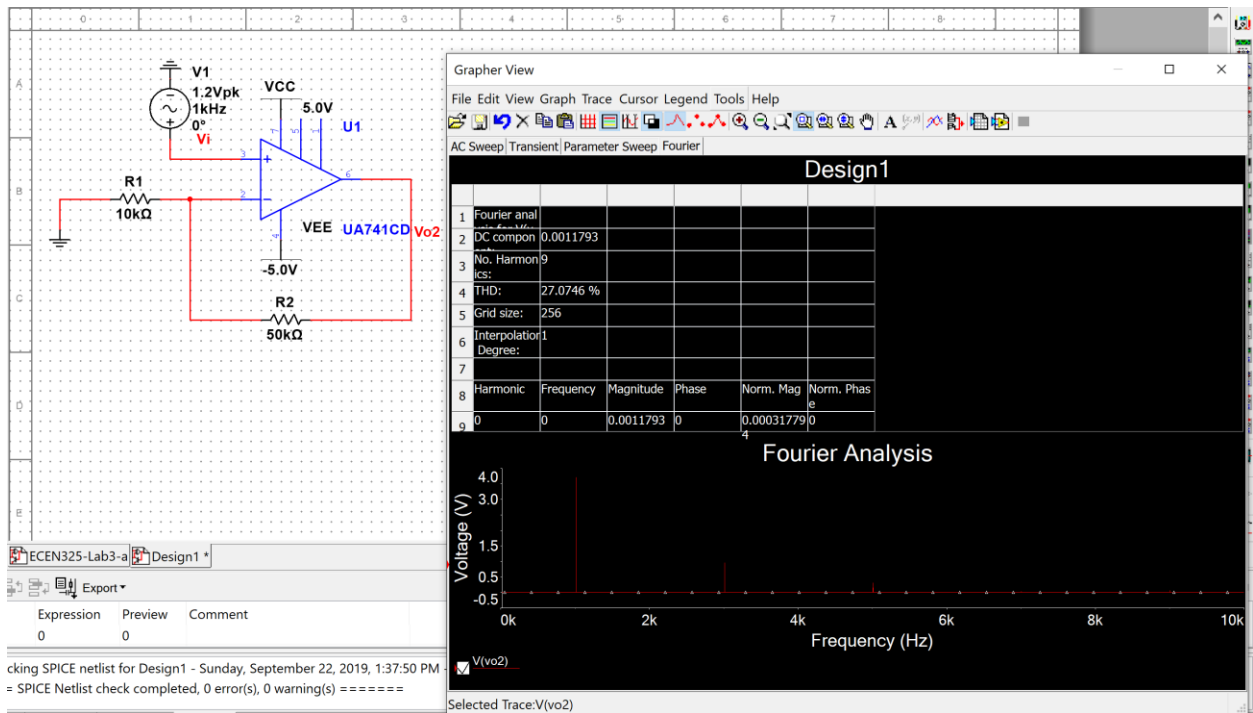


Circuit C

(a)

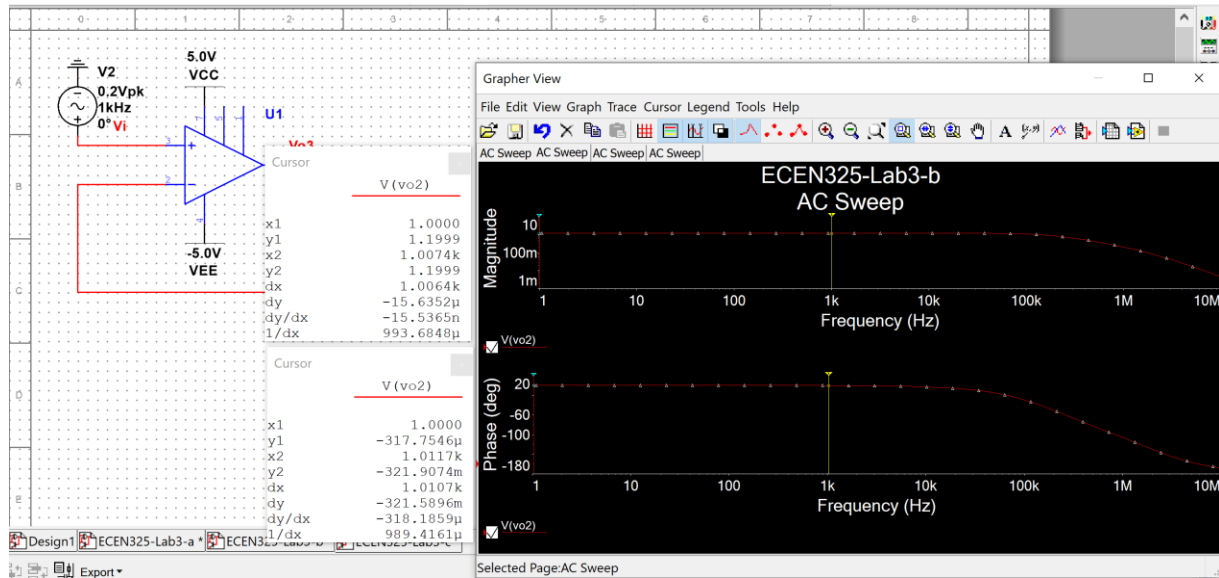


(b)

Time-Domain Waveform

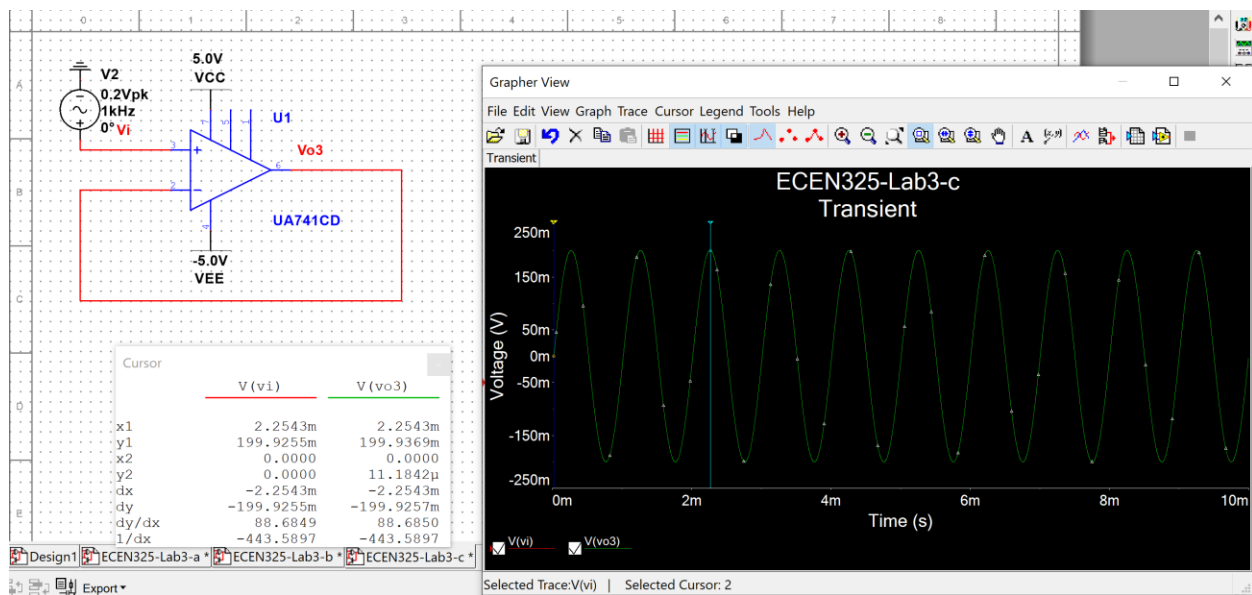


(c)

Max amplitude is about 0.2V.

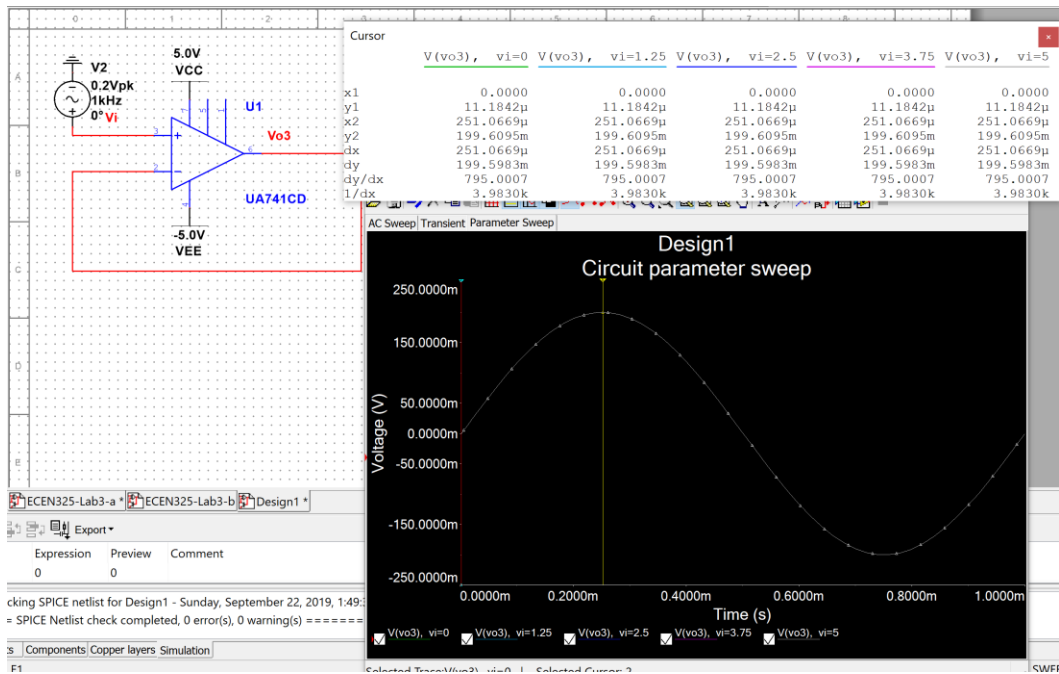

(d)


Applied $V_i(t) = 0.2 \sin(2\pi 1000t)$.

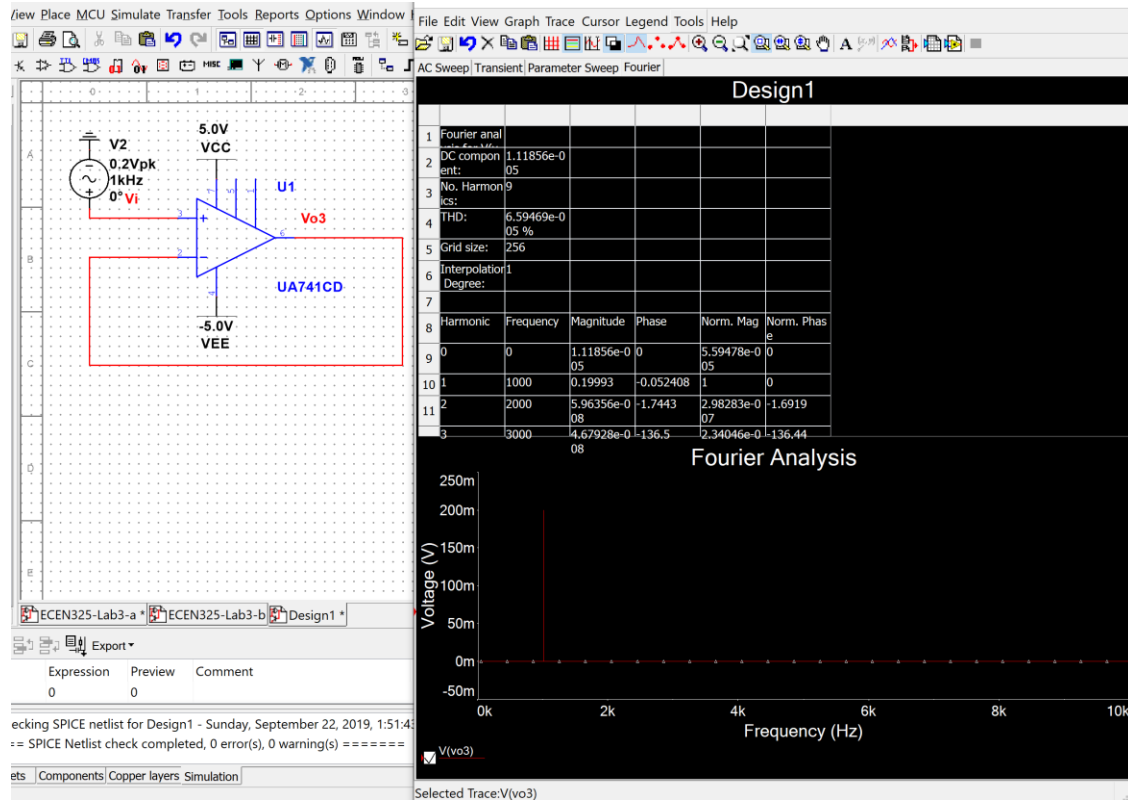


Measurement

Input Offset Current

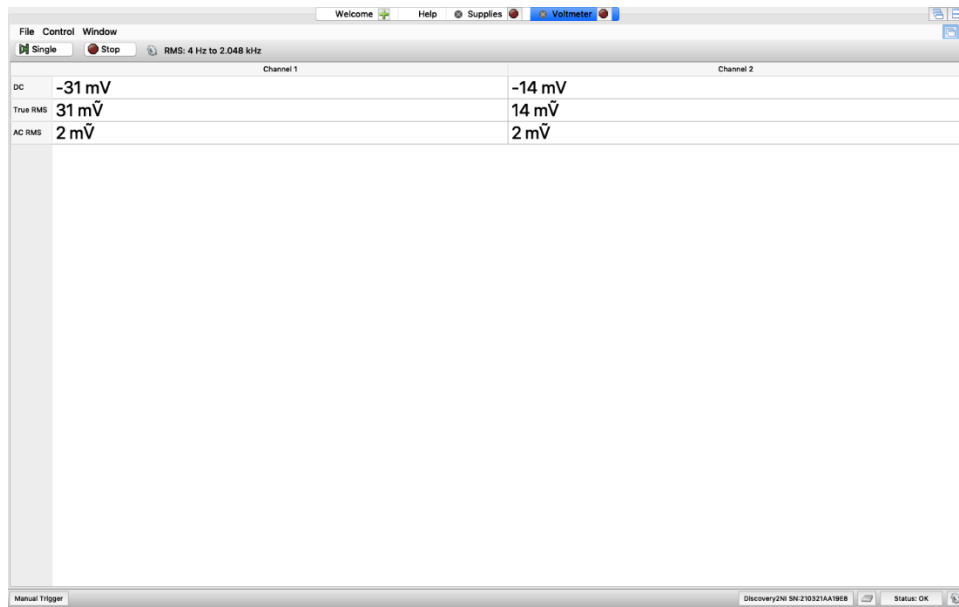Voltage Across Resistor @ Negative Terminal



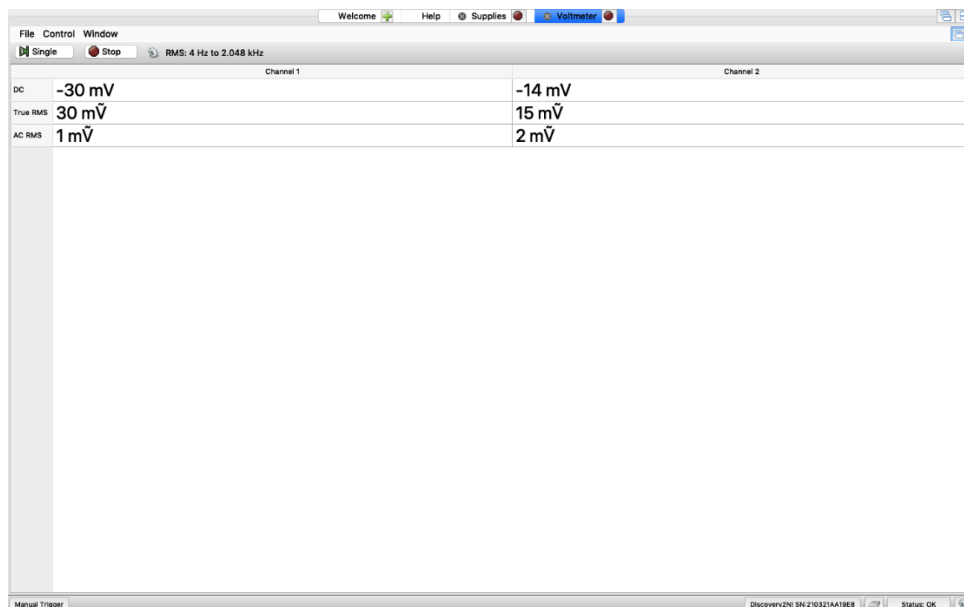Voltage Across Resistor @ Positive Terminal



$$I (\text{negative terminal}) = -31 \cdot 10^{-3} \cdot 10^{-5} = -31 \cdot 10^{-8}$$

$$I (\text{positive terminal}) = -30 \cdot 10^{-3} \cdot 10^{-5} = -30 \cdot 10^{-8}$$

$$\text{Input offset} = 1 \cdot 10^{-8} = 100 \mu\text{A}$$

DC Offset Voltage

Before placing the potentiometer:

$$\text{Output voltage offset} = 2 \text{ mV}$$


$$\text{Input voltage offset} = 2 \text{ mV} / 6 = 0.33 \text{ mV}$$

After placing the potentiometer:


$$\text{Output voltage} = 1 \text{ mV}$$

Circuit A


Boode Plot

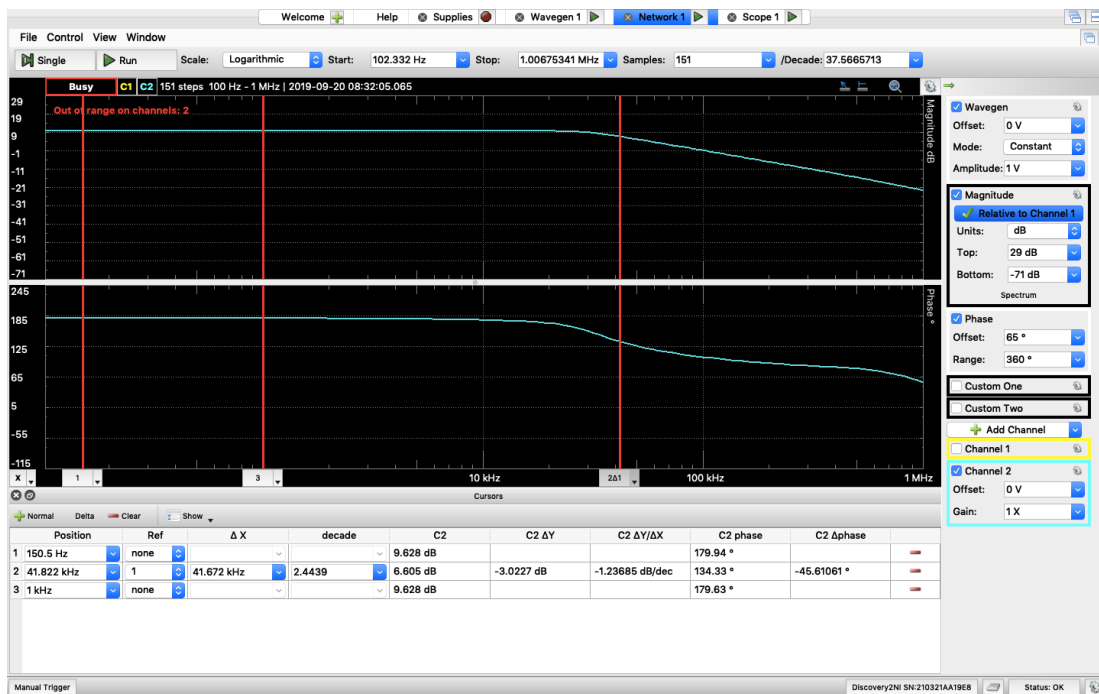


Time-Domain Waveform

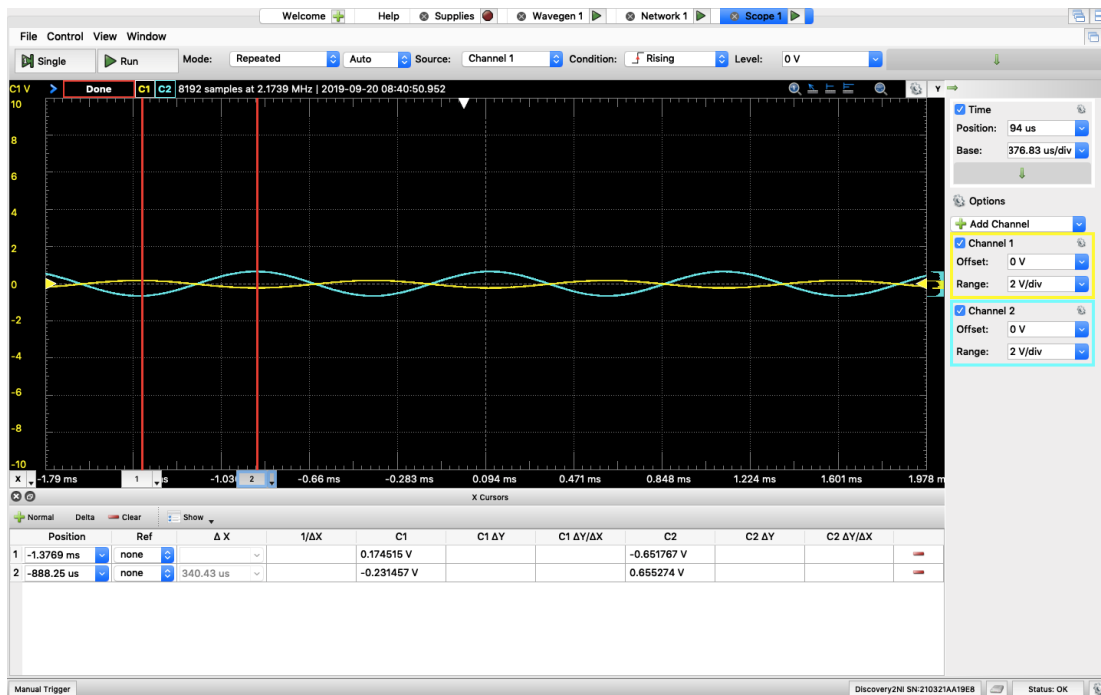

Clipping Point

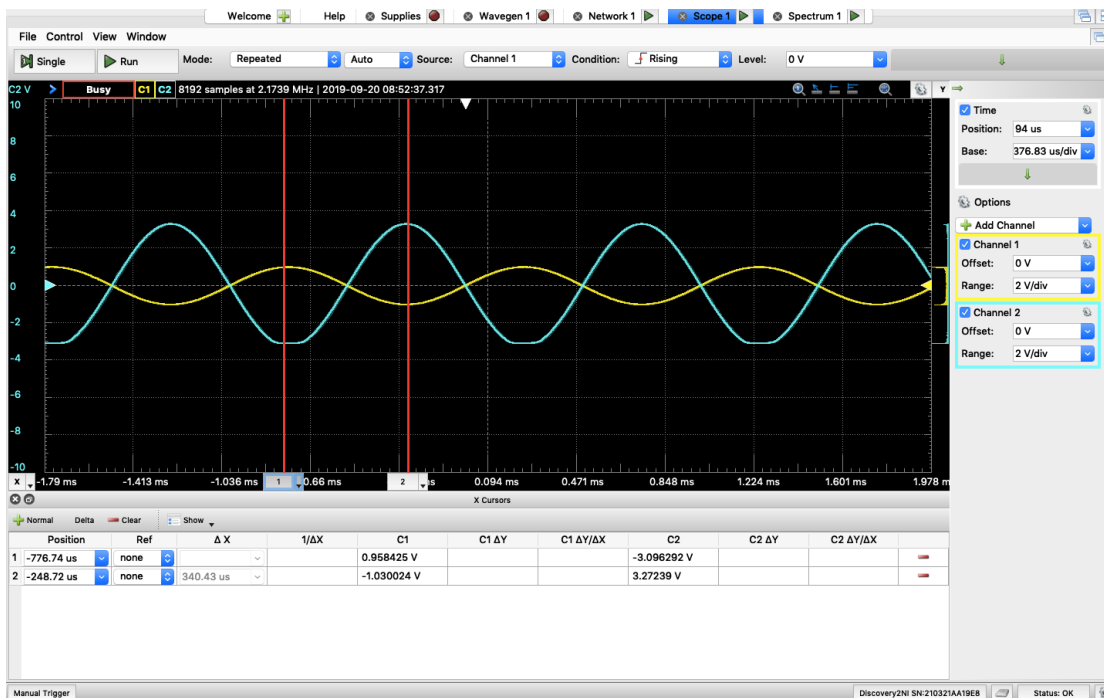


Total Harmonic Distortion

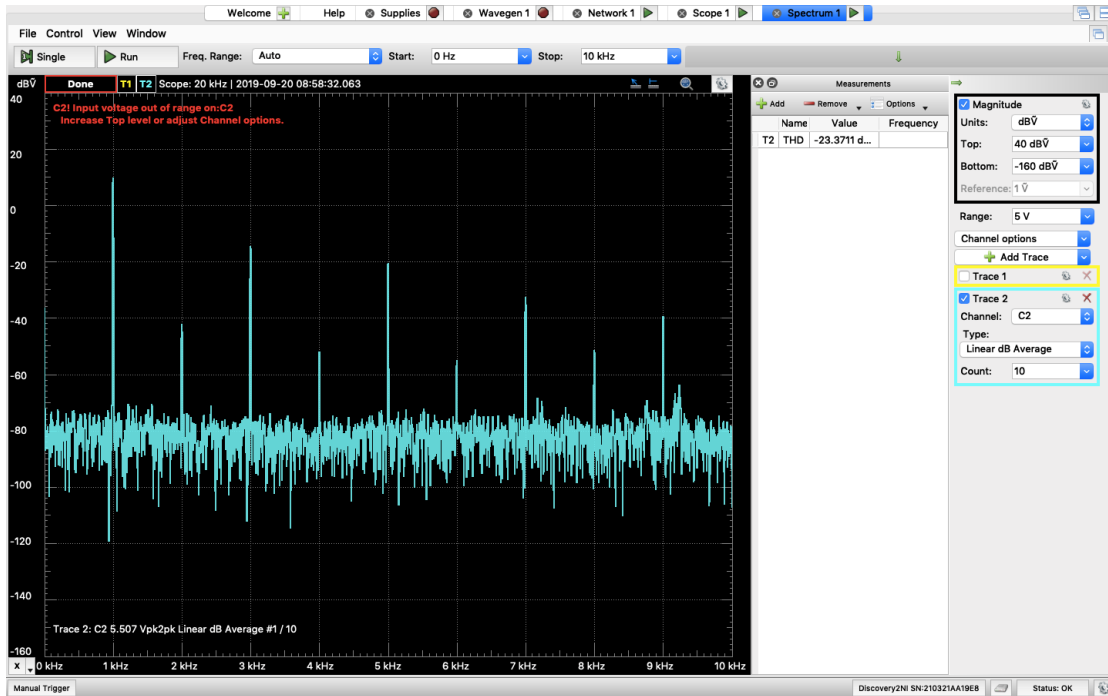


Circuit B


Bode Plot

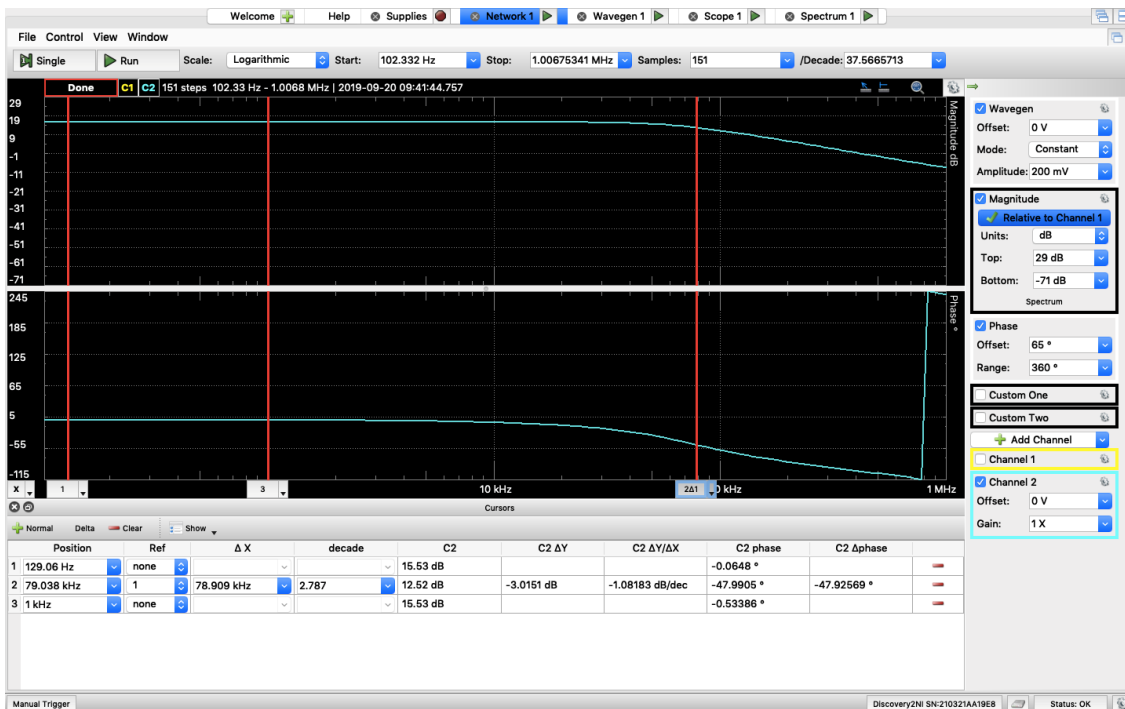


Time-Domain Waveform

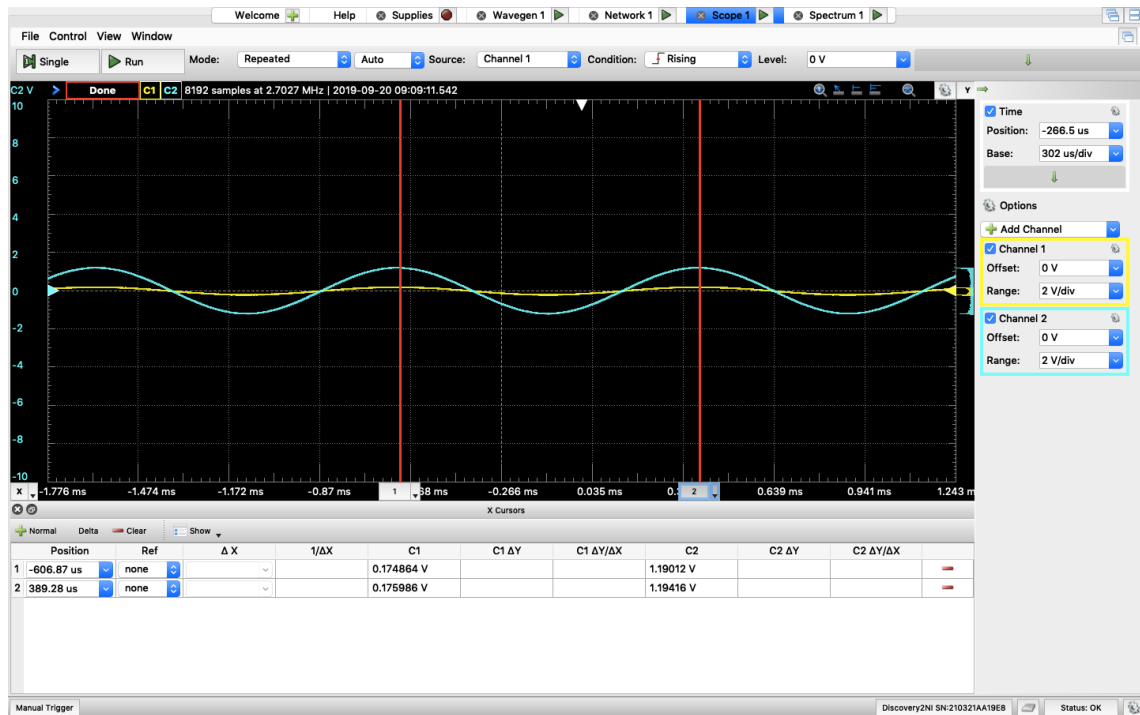

Clipping Point

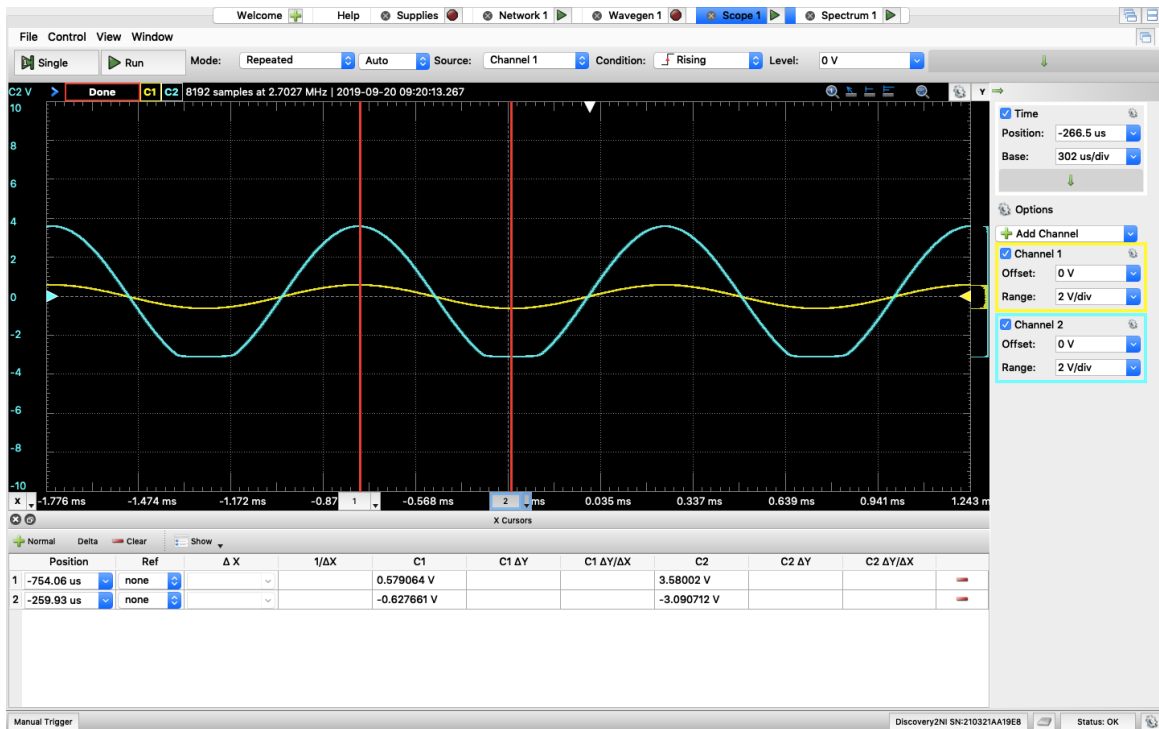


Total Harmonic Distortion

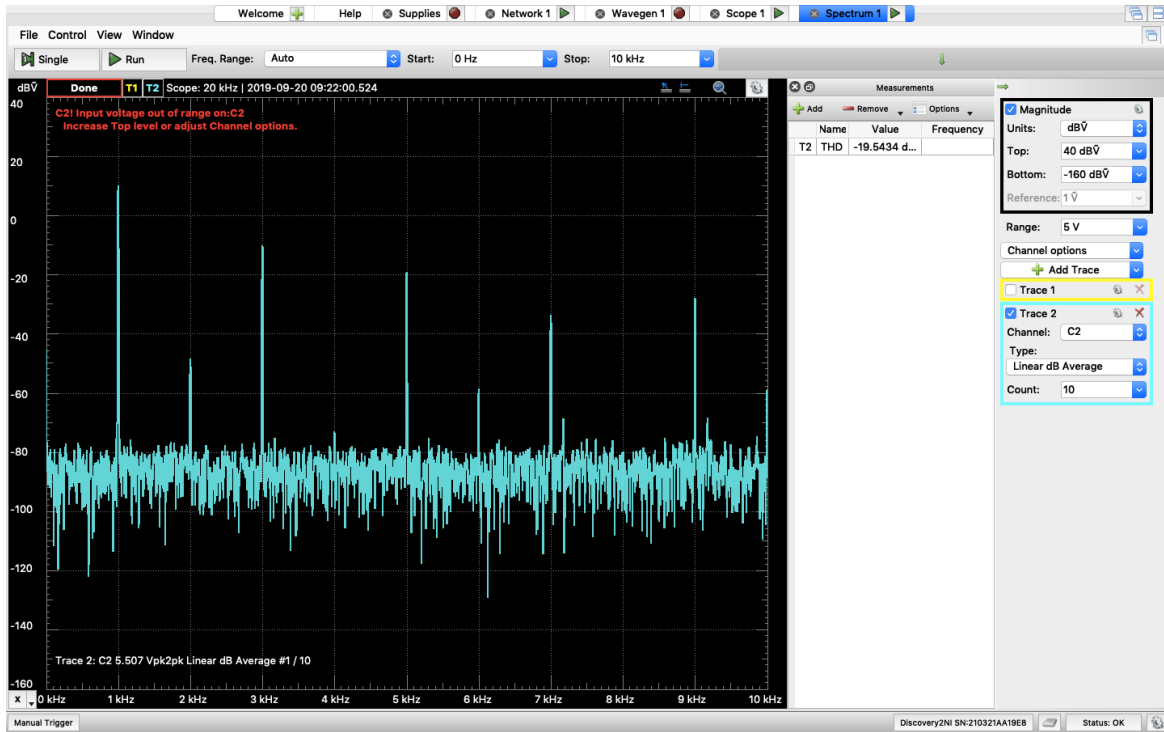


Circuit C


Bode Plot

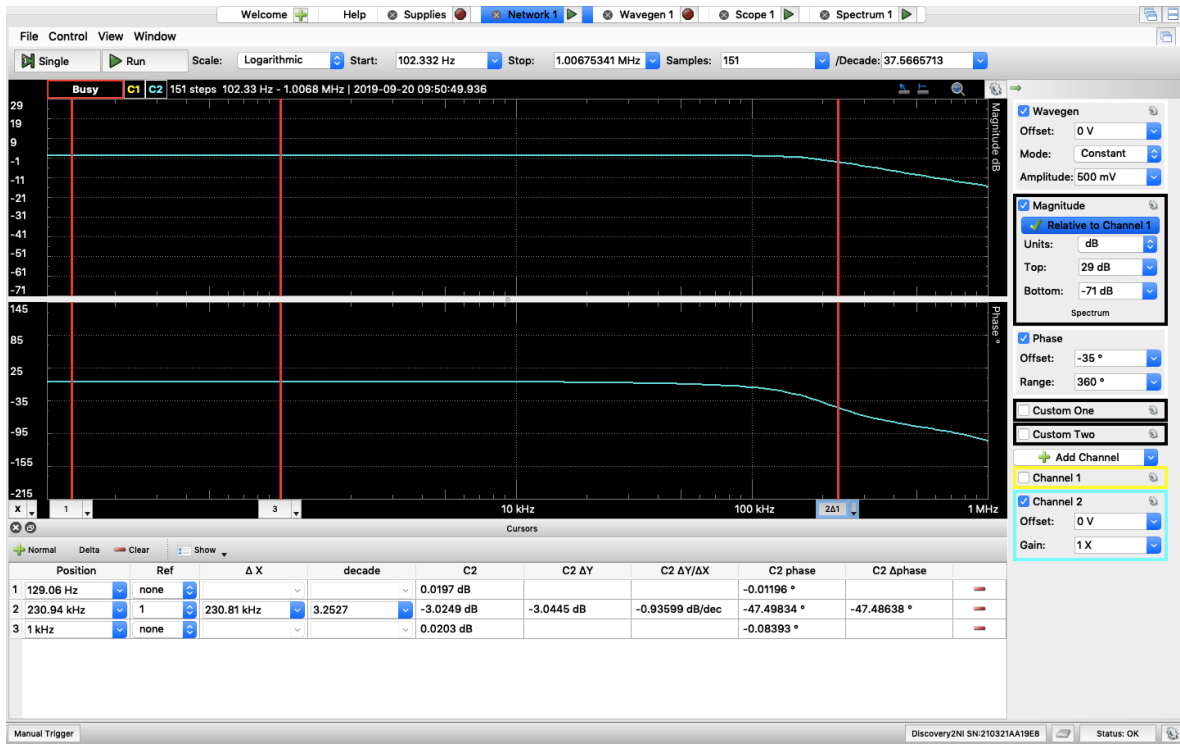

Time-Domain Waveform

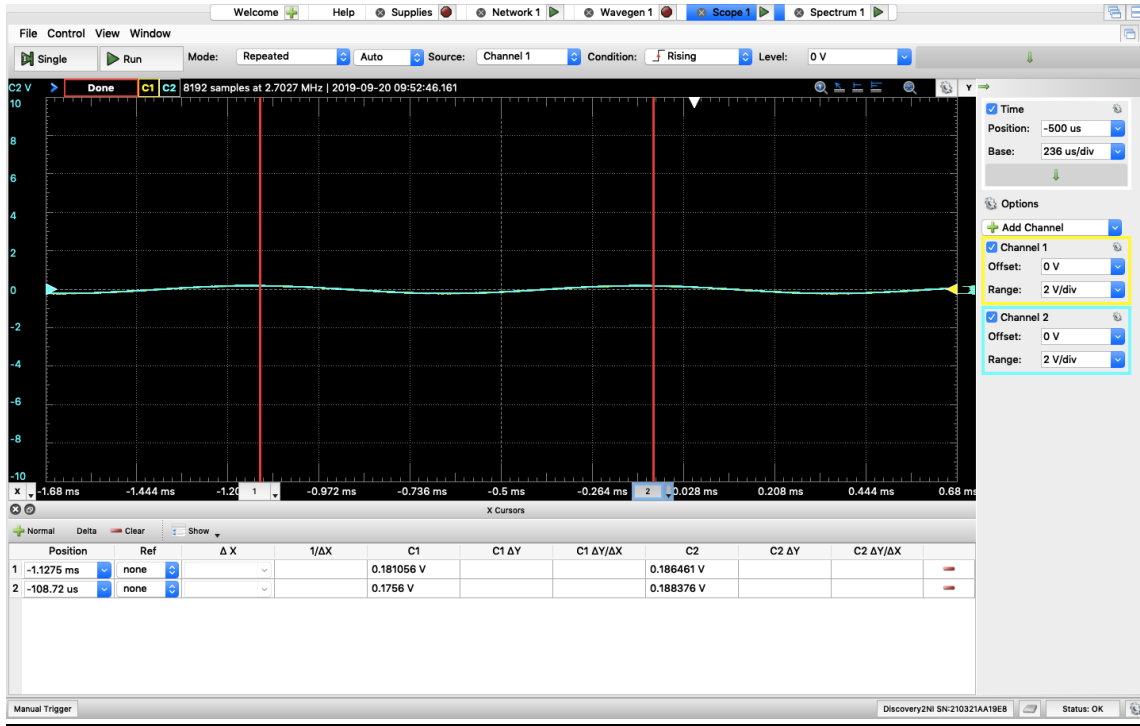

Total Harmonic Distortion

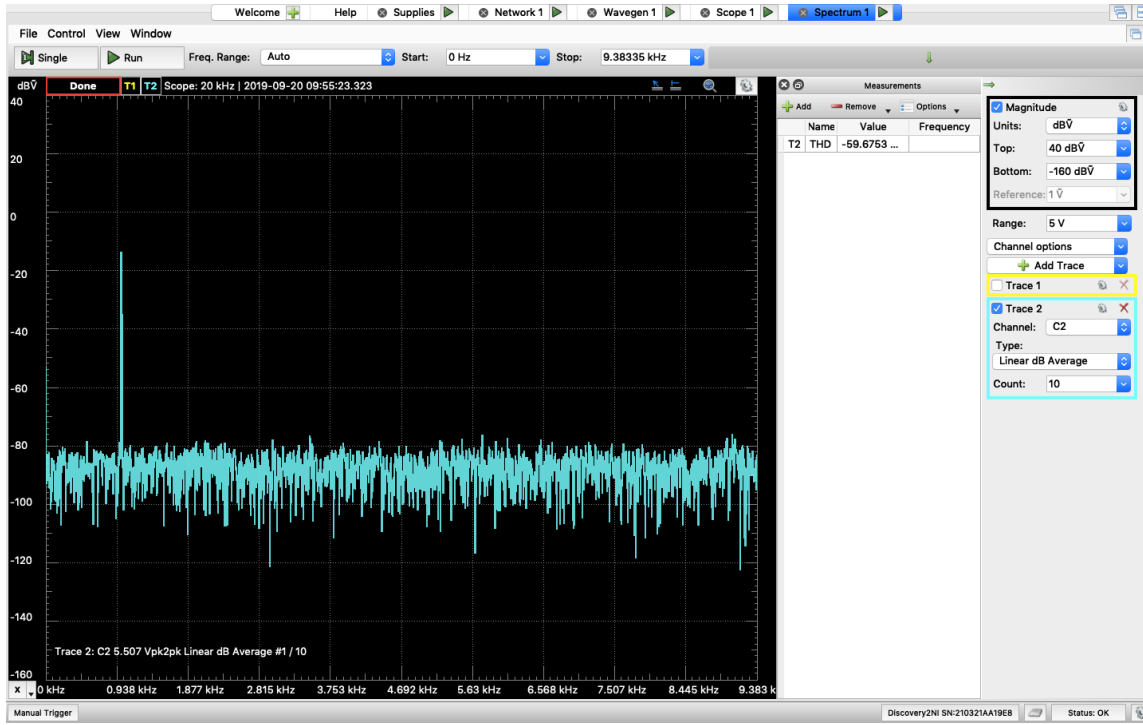

Tables

Data Sheet Value vs. Measured Value

	Data Sheet Value	Measured Value
Input Voltage Offset	1mV	0.33mV
Input Current Offset	TYP: 20nA MAX: 200nA	0.1nA

Calculated vs. Simulated vs. Measured

	V_o/V_i	$ H $	$\angle H$	$V_{i, \max}$	THD%	DC Gain
Circuit A Calculated	-3					3
Circuit A Simulated	-602.3m/200.0m = -3.01	$20\log(1.8)$ = 5.1dB	179.7°	0.6V	$8.75 \cdot 10^{-6}$	1.8
Circuit A Measured	-0.652/0.174 = -3.76	9.63dB	179.63°	1V	0.0678	$10^{9.6/20} =$ 3.02
Circuit B Calculated	6					6
Circuit B Simulated	1200m/199.6m = 6.01	$20\log(1.2)$ = 1.58dB	-0.322°	1.2V	27.1	1.2
Circuit B Measured	1.194/0.175 = 6.82	15.53dB	-0.534°	0.6V	0.105	$10^{15.5/20} =$ 5.6
Circuit C Calculated	1					1
Circuit C Simulated	199.94m/199.92m = 1.00	$20\log(1.2)$ = 1.58dB	-0.053°	0.2V	$6.59 \cdot 10^{-5}$	1.2
Circuit C Measured	0.188/0.181 = 1.04	0.02dB	-0.084°	0.2V	0.00104	$10^{0.0197/20}$ = 1.002

Conclusion

The results of simulation are different from the results of calculation and measurement. It might be because I used Vee for the negative power supply on simulation circuits or the values I entered are wrong.

For the DC voltage offset part, after placing the potentiometer, the output voltage should be 0V but not 1mV. It might be because I didn't turn the potentiometer to the right place.

For ideal amplifier, the Bode Plot should be a horizontal line. However, in reality, there are CMOS in the amplifier, and it is dependent on A/s. Therefore, when the frequency gets very large, there is a pole that makes the Bode plot go down. That's the reason why in the measurement plots, the Bode plot for 3 circuits all decrease at the large frequency value.