

**Pre-Lab 7:**  
**Characterization and DC Biasing of  
the BJT**

Name: Wan-Yu Liao

ECEN 325 Section 514


TA: Mandela

Date: October 18, 2019

## Calculations

(1)

### NPN Resistive DC Biasing Circuit

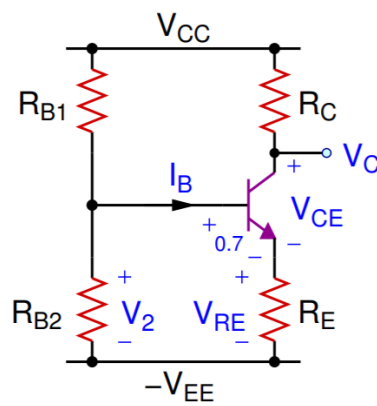

#### NPN

$I_C$	$1\text{mA}$
$V_C$	$3.5\text{V}$
$V_{CE}$	$\geq 1\text{V}$
$V_{RE}$	$\geq 1\text{V}$
$V_{CC}$	$5\text{V}$
$V_{EE}$	$0$
$\beta$	$100$
$V_T$	$25\text{mV}$
$I_{\text{supply}}$	$\leq 2\text{mA}$

$$R_C = 1.5\text{k}\Omega$$

$$V_{RE} = 2.222\text{V}$$

$$V_2 = 2.922\text{V}$$

$$R_E = 2.2\text{k}\Omega$$

$$R_{B1} = 1.95\text{k}\Omega$$

$$R_{B2} = 2.7\text{k}\Omega$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5 - 3.5}{1\text{m}} = 1.5\text{k}\Omega$$

$$I_E \approx I_C = 1\text{mA}$$

$$V_{RE} + V_{CE} = 3.5\text{V} \quad (\text{Assume } V_{CE} = 1.278\text{V})$$

$$V_{RE} = 2.222\text{V}$$


$$R_E = \frac{V_{RE}}{I_E} = \frac{2.222\text{V}}{1\text{m}} = 2.2\text{k}\Omega$$

$$V_2 - V_{RE} = 0.7\text{V} \Rightarrow V_2 = 2.922\text{V}$$

$$5 \cdot \frac{R_{B2}}{R_{B1} + R_{B2}} = 2.922 \Rightarrow \frac{R_{B2}}{R_{B1} + R_{B2}} = \frac{2.922}{5}$$

$$R_{B2} = 2.7\text{k}\Omega \quad R_{B1} = 1.95\text{k}\Omega = 3.3\text{k}\Omega \parallel 4.7\text{k}\Omega$$

## PNP Resistive DC Biasing Circuit

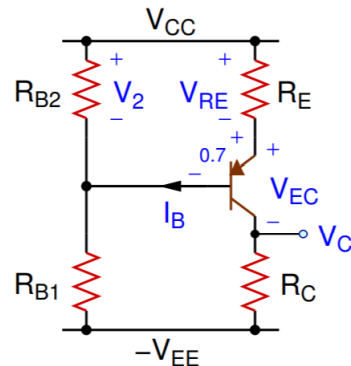

### PNP

$I_C$	$1\text{mA}$
$V_C$	$1.5\text{V}$
$V_{EC}$	$\geq 1\text{V}$
$V_{RE}$	$\geq 1\text{V}$
$V_{CC}$	$5\text{V}$
$V_{EE}$	$0$
$\beta$	$100$
$V_T$	$25\text{mV}$
$I_{\text{supply}}$	$\leq 2\text{mA}$

$$R_C = 1.5\text{k}\Omega$$

$$V_{RE} = 2.2\text{V}$$

$$V_2 = 2.9\text{V}$$

$$R_E = 2.2\text{k}\Omega$$

$$R_{B1} = 1.8\text{k}\Omega$$

$$R_{B2} = 2.47\text{k}\Omega$$

$$R_C = \frac{V_C}{I_C} = \frac{1.5}{1\text{m}} = 1.5\text{k}\Omega$$

$$I_E \approx I_C = 1\text{mA}$$

$$V_{RE} = 5 - 1.3 - 1.5 = 2.2\text{V} \quad (\text{Assume } V_{EC} = 1.3\text{V})$$

$$5 - V_2 = 2.1\text{V} \Rightarrow V_2 = 2.9\text{V}$$

$$R_E = \frac{2.2}{1\text{m}} = 2.2\text{k}\Omega$$



$$5 \cdot \frac{R_{B1}}{R_{B2} + R_{B1}} = 2.1$$

$$\Rightarrow R_{B1} = 1.8\text{k}\Omega, R_{B2} = 2.47\text{k}\Omega$$

$$= 2\text{k} + 470\Omega$$

(2)

### NPN DC Biasing Circuit

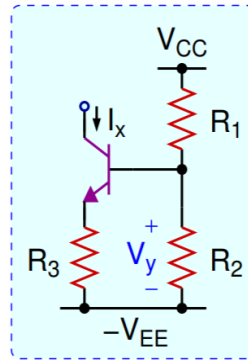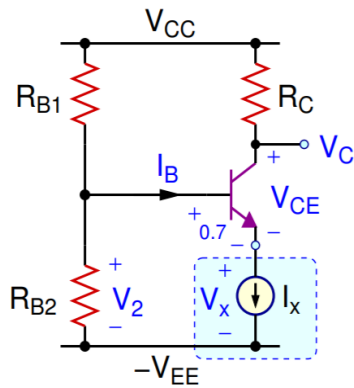

#### NPN

$I_C$	$2\text{mA}$
$V_C$	$3.5\text{V}$
$V_{CE}$	$\geq 1\text{V}$
$V_x$	$\geq 1.5\text{V}$
$V_{CC}$	$5\text{V}$
$V_{EE}$	$0$
$\beta$	$100$
$V_T$	$25\text{mV}$
$I_{\text{supply}}$	$\leq 5\text{mA}$

$$R_C = 0.75\text{k}\Omega \quad R_1 = 1\text{k}\Omega \quad R_2 = 1.5\text{k}\Omega \quad R_3 = 1.2\text{k}\Omega$$

$$R_{B1} = 1.8\text{k}\Omega \quad R_{B2} = 3.3\text{k}\Omega$$

$$R_C = \frac{5 - 3.5}{2\text{mA}} = 0.75\text{k}\Omega$$

$$I_E \approx I_C = 2\text{mA} = I_x \approx I_{R3}$$

$$2\text{mA} \cdot R_3 + 0.7 = V_y = 5 \cdot \frac{R_2}{R_2 + R_1} \quad (\text{Assume } V_y = 3\text{V})$$

$$R_3 = 1.2\text{k}\Omega \quad R_1 = 1\text{k}\Omega \quad R_2 = 1.5\text{k}\Omega$$

$$V_x + V_{CE} = V_C = 3.5\text{V} \quad (\text{Assume } V_{CE} = 1\text{V})$$



$$V_x = 2.5\text{V}$$

$$V_2 = V_x + 0.7\text{V} = 3.2\text{V}$$

$$3.2\text{V} = 5 \cdot \frac{R_{B2}}{R_{B2} + R_{B1}}$$

$$R_{B1} = 1.8\text{k}\Omega \quad R_{B2} = 3.3\text{k}\Omega$$

# PNP DC Biasing Circuit

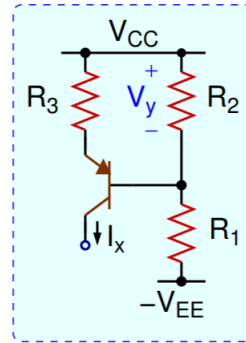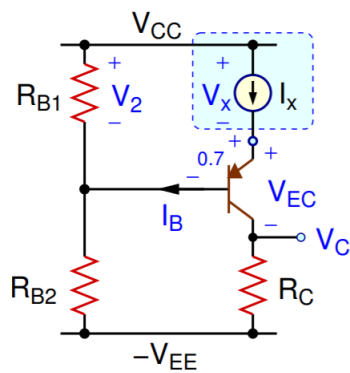

## PNP

$I_C$	2mA
$V_C$	1.5V
$V_{EC}$	$\geq 1V$
$V_x$	$\geq 1.5V$
$V_{CC}$	5V
$V_{EE}$	0
$\beta$	100
$V_T$	25mV
$I_{supply}$	$\leq 5mA$

$$R_C = 0.75K\Omega \quad R_1 = 1.5K \quad R_2 = 1K \quad R_3 = 650$$

$$R_{B1} = 3.2K \quad R_{B2} = 1.8K$$

$$R_C = \frac{1.5}{2m} = 0.75K$$

$$I_E \approx I_C = 2mA = I_x$$

$$5 \cdot \frac{R_1}{R_1 + R_2} = 3V \quad (\text{Assume } V_y = 2V)$$

$$\Rightarrow R_1 = 1.5K \quad R_2 = 1K$$

$$R_3 = \frac{5 - (3 + 0.7)}{2m} = 650\Omega$$

$$5 = V_x + V_{EC} + V_C \Rightarrow V_x = 2.5V \quad (\text{Assume } V_{EC} = 1V)$$

$$5 - V_2 = 1.8V$$

$$5 \cdot \frac{R_{B2}}{R_{B1} + R_{B2}} = 1.8V$$

$$R_{B2} = 1.8K \quad R_{B1} = 3.2K$$

## Simulations

(1)

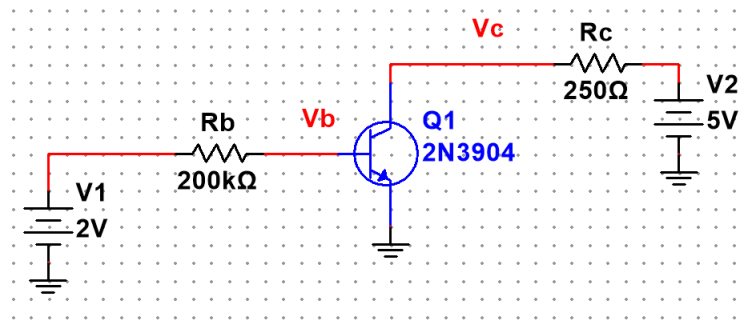


Figure 1: Schematic of NPN BJT characterization circuit for Fig. 2 ▲

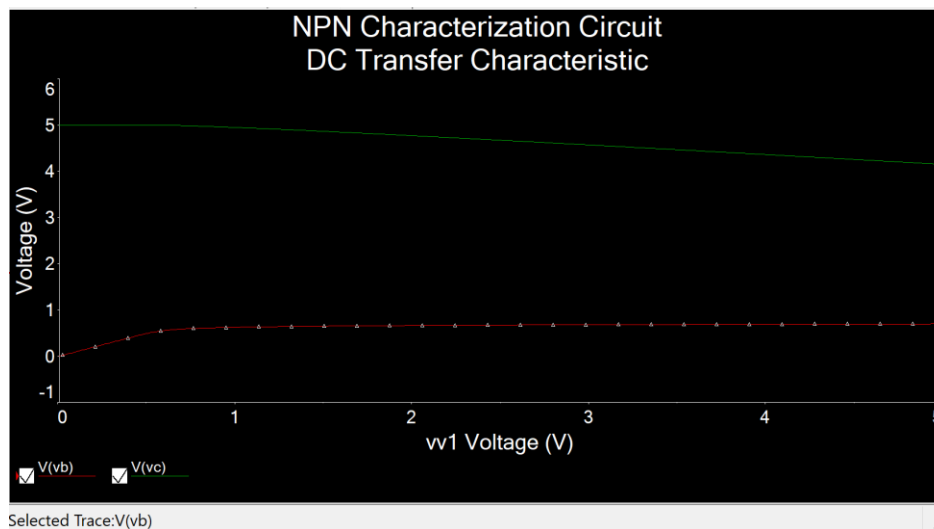


Figure 2: Simulation plot of NPN BJT characterization circuit using DC sweep of V1 from 0 to 5V, while V2 = 5V ▲

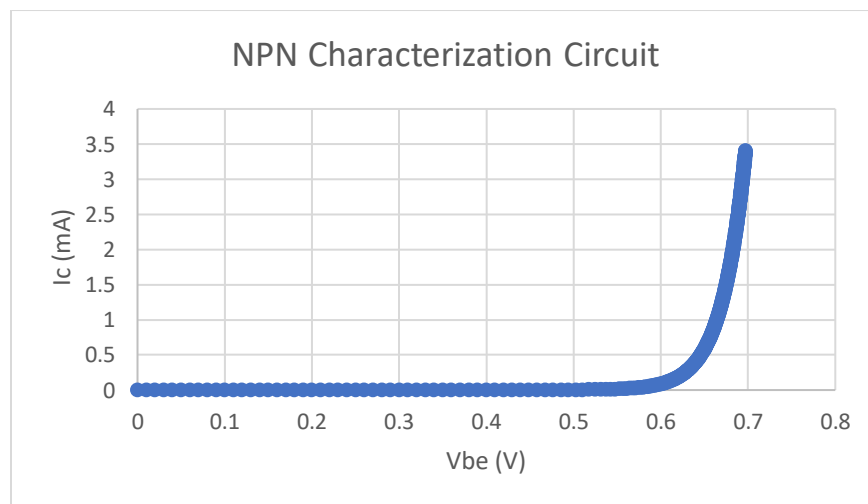


Figure 3: Excel plot for collector current (IC) of an NPN BJT as a function of Vbe ▲

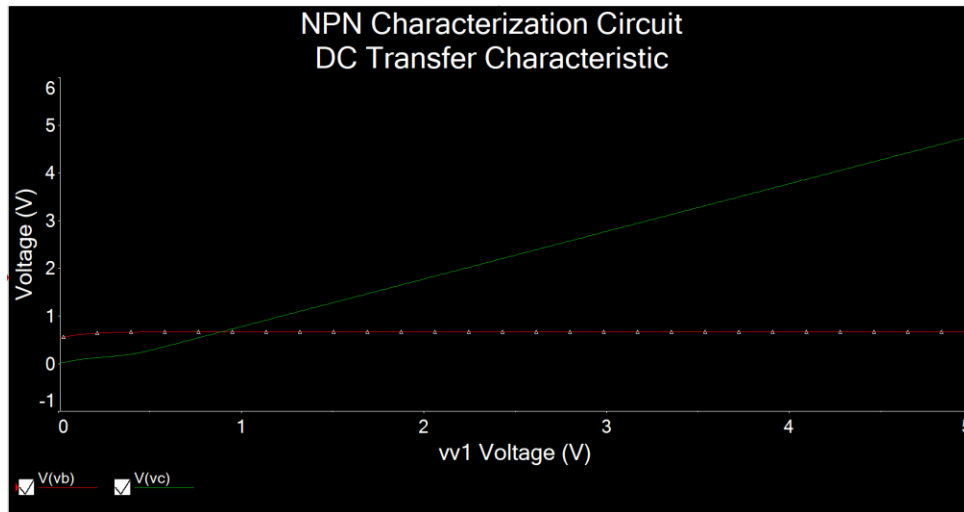


Figure 4: Simulation plot of NPN BJT characterization circuit using DC sweep of  $V_2$  from 0 to 5V, while  $V_1 = 2V$  ▲

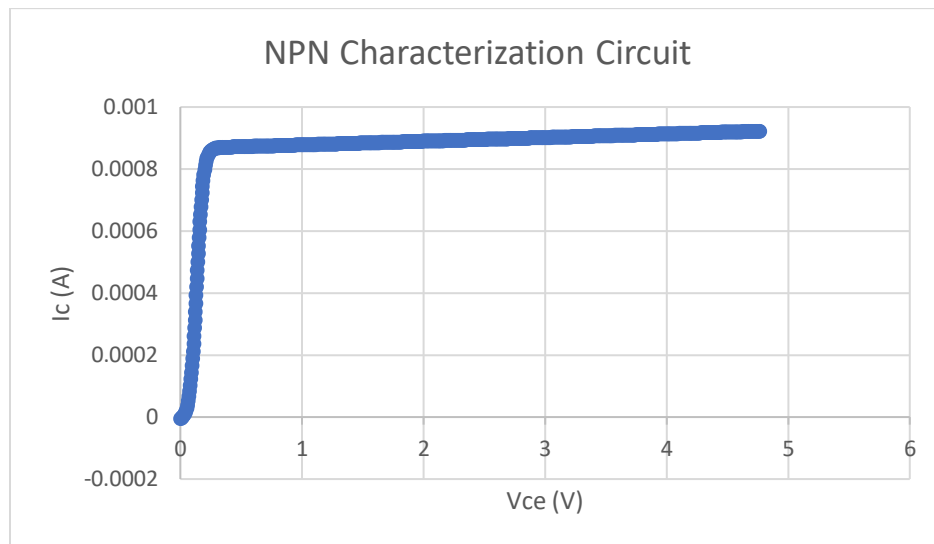


Figure 5: Excel plot for collector current ( $I_c$ ) of an NPN BJT as a function of  $V_{ce}$  ▲

(2)

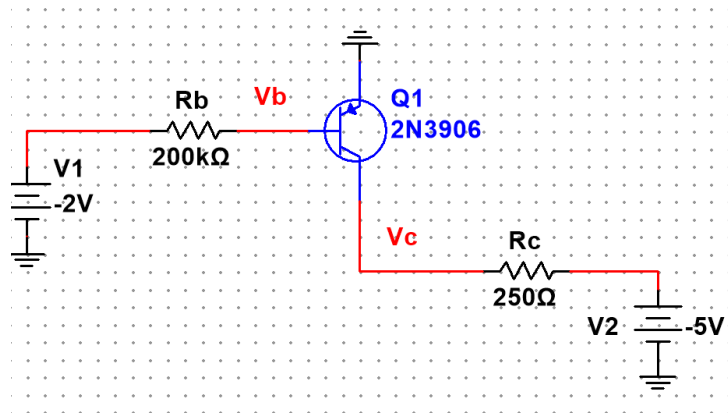


Figure 6: Schematic of NPN BJT characterization circuit for Fig. 4 ▲

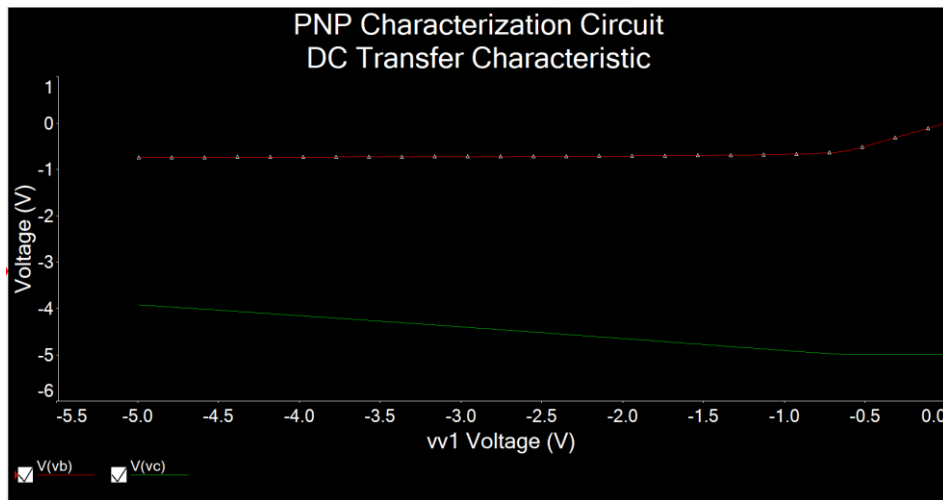


Figure 7: Simulation plot of PNP BJT characterization circuit using DC sweep of V1 from -5 to 0V, while V2 = -5V ▲

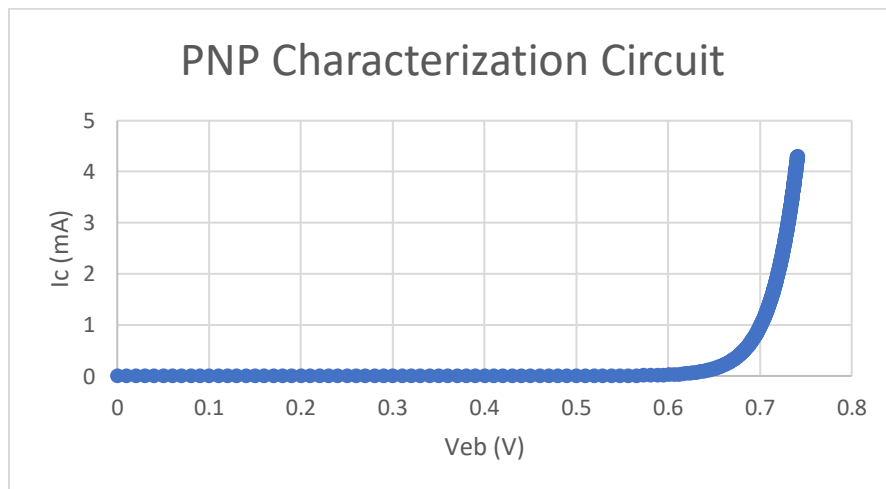


Figure 8: Excel plot for collector current (IC) of an PNP BJT as a function of Veb ▲



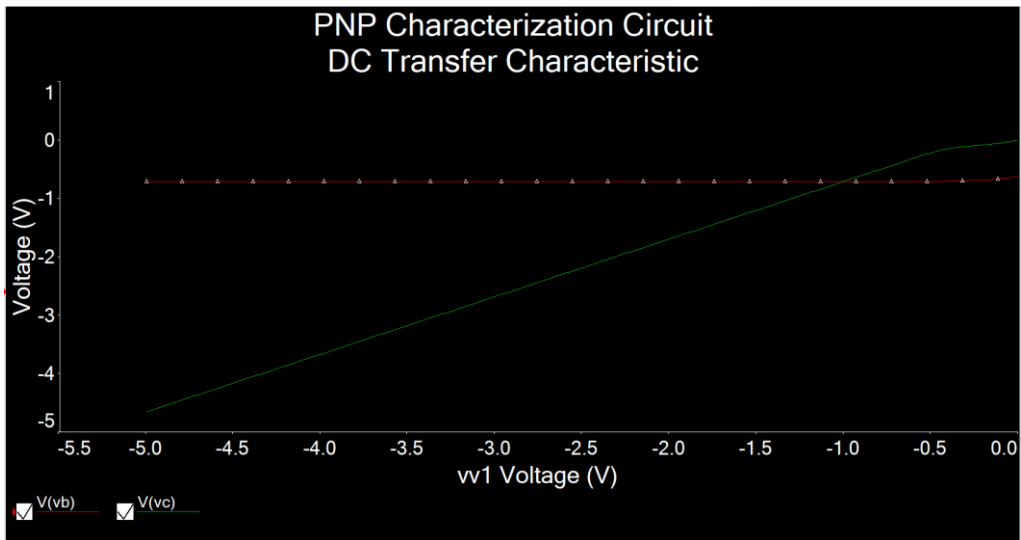


Figure 9: Simulation plot of PNP BJT characterization circuit using DC sweep of  $V_2$  from -5 to 0V, while  $V_1 = -2V$  ▲

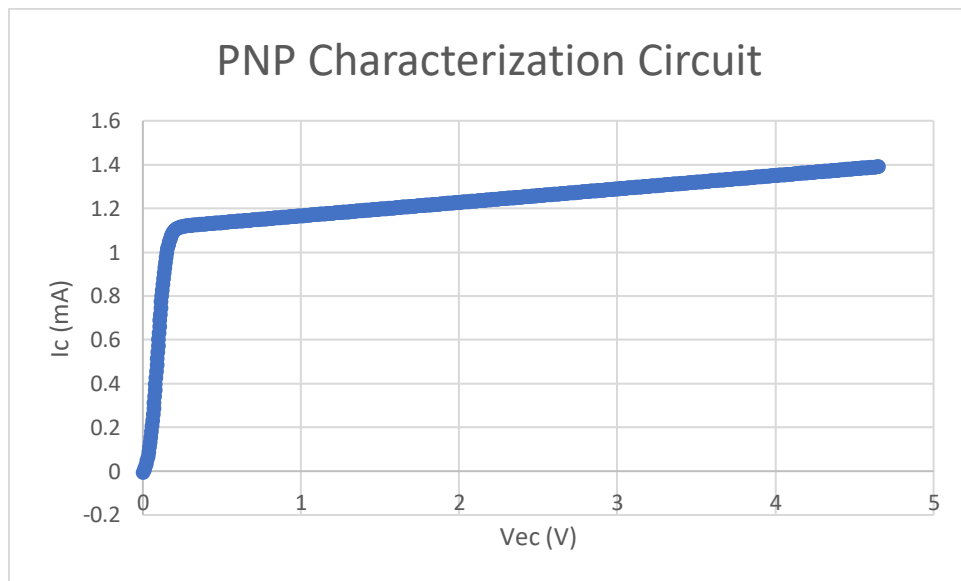


Figure 10: Excel plot for collector current ( $I_c$ ) of an PNP BJT as a function of  $V_{ec}$  ▲

(3)

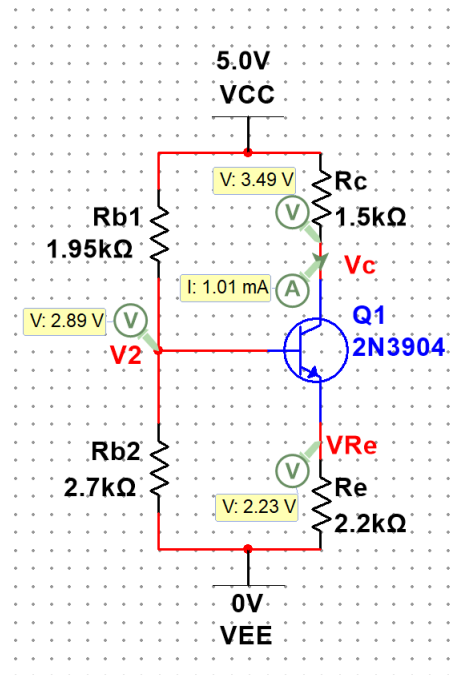


Figure 11: Schematic and interactive simulation for  $I_C$ ,  $V_C$ ,  $V_{RE}$ , and  $V_2$  for NPN Resistive DC biasing circuit in Fig. 6(a) ▲

$$I_C = 1.01 \text{ mA}, V_C = 3.49 \text{ V}, V_{RE} = 2.23 \text{ V}, V_2 = 2.89 \text{ V}$$

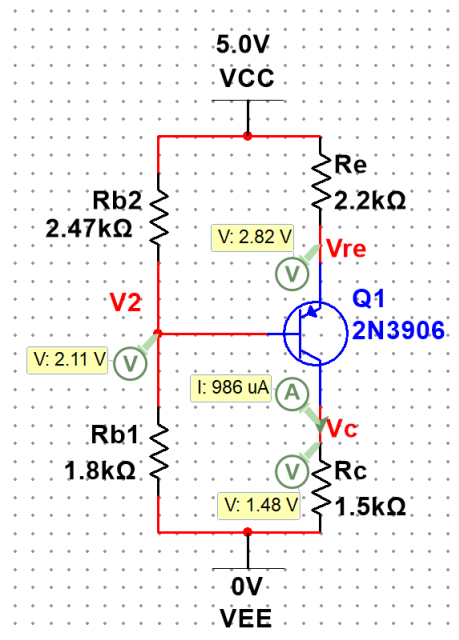


Figure 12: Schematic and interactive simulation for  $I_C$ ,  $V_C$ ,  $V_{RE}$ , and  $V_2$  for PNP Resistive DC biasing circuit in Fig. 6(b) ▲

$$I_C = 0.986 \text{ mA}, V_C = 1.48 \text{ V}, V_{RE} = 2.82 \text{ V}, V_2 = 2.11 \text{ V}$$

(4)

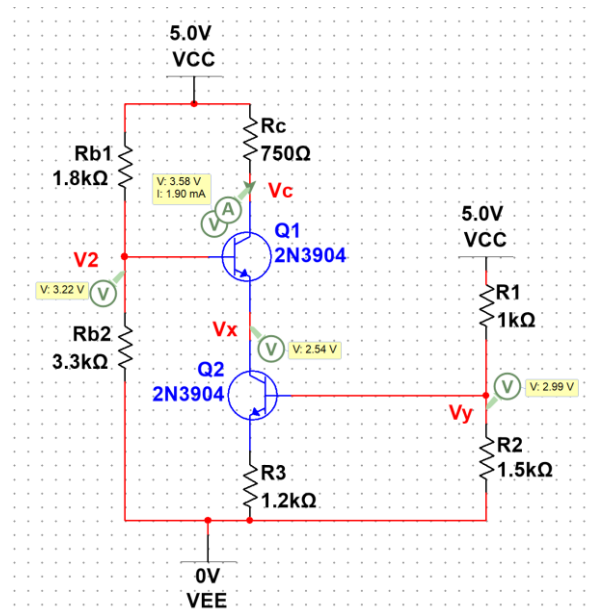


Figure 13: Schematic and interactive simulation for  $I_C$ ,  $V_C$ ,  $V_2$ ,  $V_x$ , and  $V_y$  for NPN DC biasing circuit using current source in Fig. 7(a) and Fig. 7(b) ▲

$$I_C = 1.90 \text{ mA}, V_C = 3.58 \text{ V}, V_2 = 3.22 \text{ V}, V_x = 2.54 \text{ V}, V_y = 2.99 \text{ V}$$

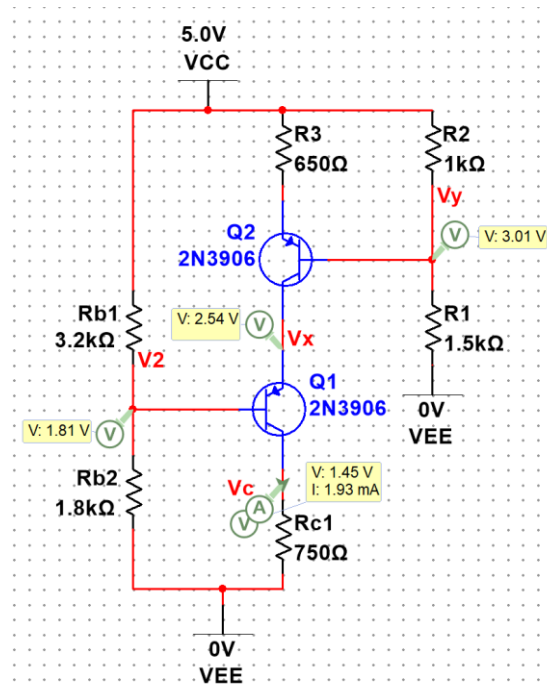


Figure 14: Schematic and interactive simulation for  $I_C$ ,  $V_C$ ,  $V_2$ ,  $V_x$ , and  $V_y$  for NPN DC biasing circuit using current source in Fig. 8(a) and Fig. 8(b) ▲

$$I_C = 1.93 \text{ mA}, V_C = 1.45 \text{ V}, V_2 = 3.19 \text{ V}, V_x = 2.54 \text{ V}, V_y = 1.99 \text{ V}$$