

Lab 9:

BJT Amplifier Design

Name: Wan-Yu Liao

ECEN 325 Section 514

TA: Mandela

Lab Date: November 1, 2019

Lab Report Due Date: November 8, 2019

Calculation

$$\text{choose } V_{RE} = 1.3V \quad V_0 = 1.1V \quad |V_{CE, SAT}| = 0.3V$$

$$5 - 1.1 - 1.3 - 0.3 \geq V_{RC} \geq 1.1 \Rightarrow 2.3 \geq V_{RC} \geq 1.1$$

$$\Rightarrow V_{RC} = 2.3V$$

$$\frac{2.3 - 0.7 - 1.1}{R_H} \geq \frac{1.1}{100} \Rightarrow R_H \leq 45.45 \Rightarrow R_H = 33\Omega$$

$$I_{C2} = \frac{2.3 - 0.7}{33} = 48mA$$

$$\text{choose } N=20, \beta=300, R_i = 1.5K\Omega$$

$$20 \cdot \frac{48m}{350} \leq I_{C1} \leq \frac{300}{1500} \cdot \frac{1}{\frac{20}{1.3+0.7} + \frac{20}{5-1.3-0.7} + \frac{20}{2.3}}$$

$$\Rightarrow 2.74mA \leq I_{C1} \leq 7.9mA \Rightarrow I_{C1} = 4.2mA$$

$$R_C = \frac{2.3}{4.2m} = 547\Omega \quad R_E = \frac{1.3}{4.2m} = 309\Omega$$

$$R_G = \frac{547}{20} - \frac{25}{4.2} = 21\Omega$$

$$R_{B1} = \frac{300(5-1.3-0.7)}{20 \cdot 4.2m} = 10.7K\Omega$$

$$R_{B2} = \frac{300(1.3+0.7)}{20 \cdot 4.2m} = 7.1K\Omega$$

Simulation

(I redo the simulation, since the simulation in pre-lab was wrong)

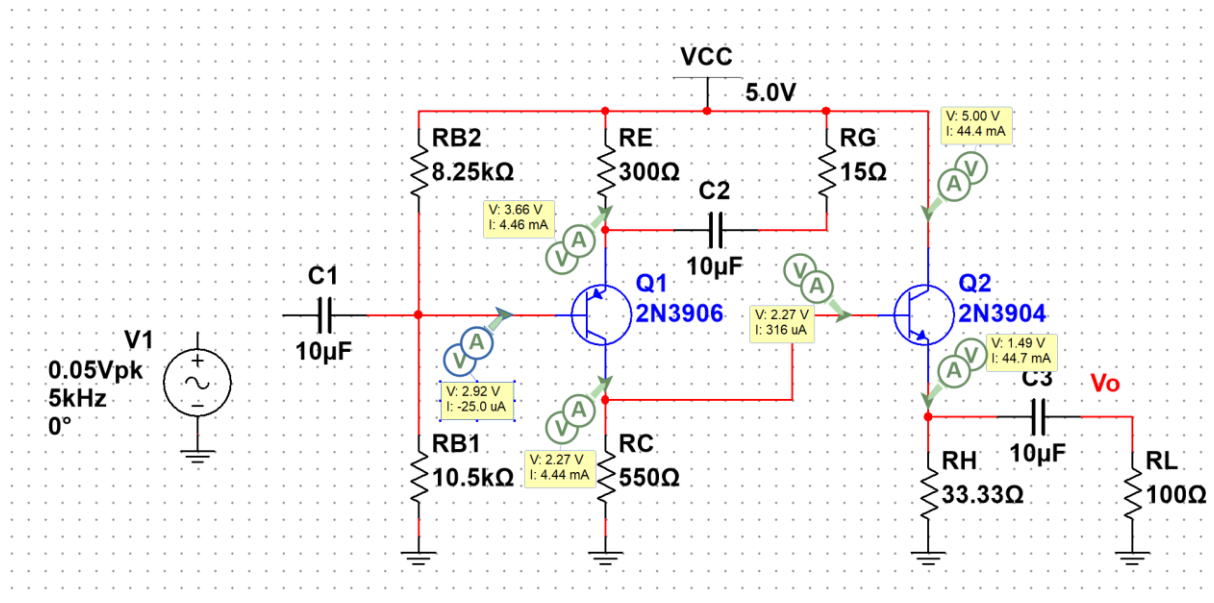


Figure 1: DC solutions

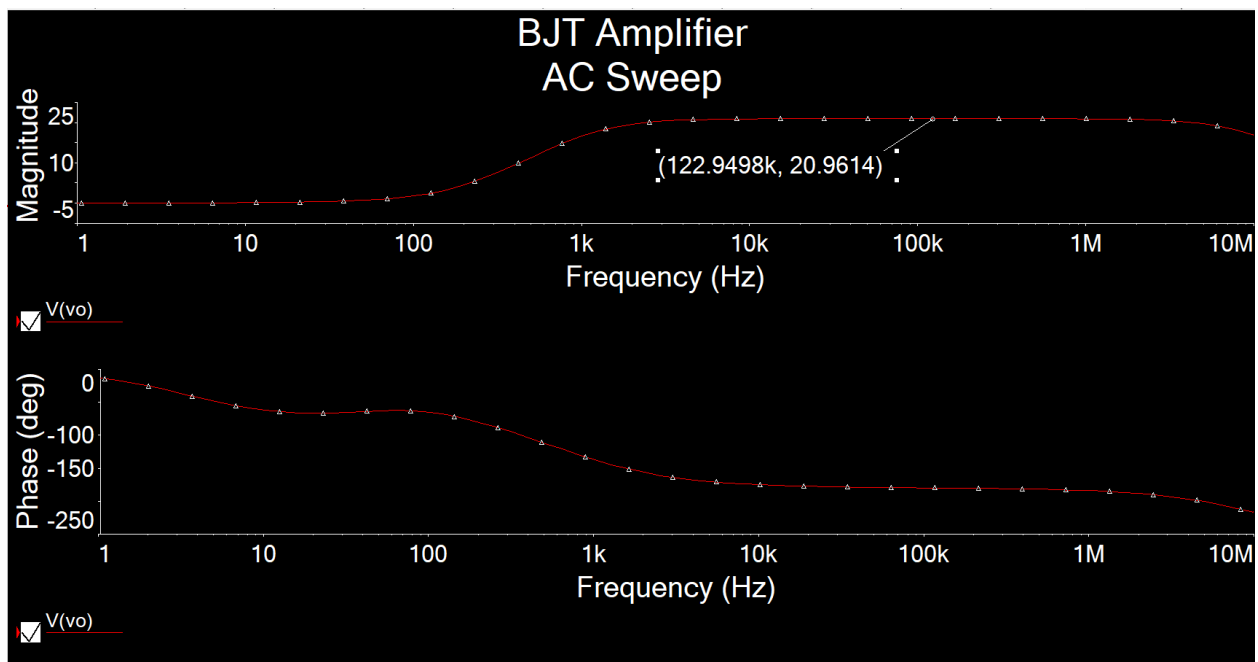


Figure 2-1: AC Simulation of A_v

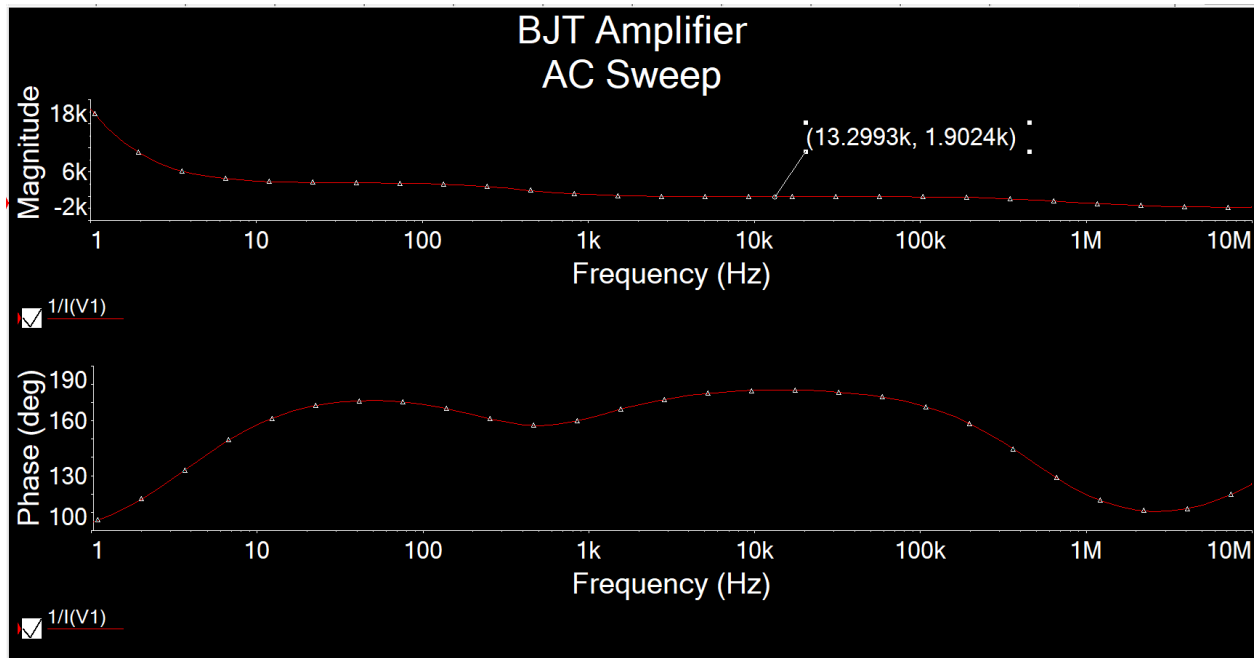


Figure 2-2: AC Simulation of Ri

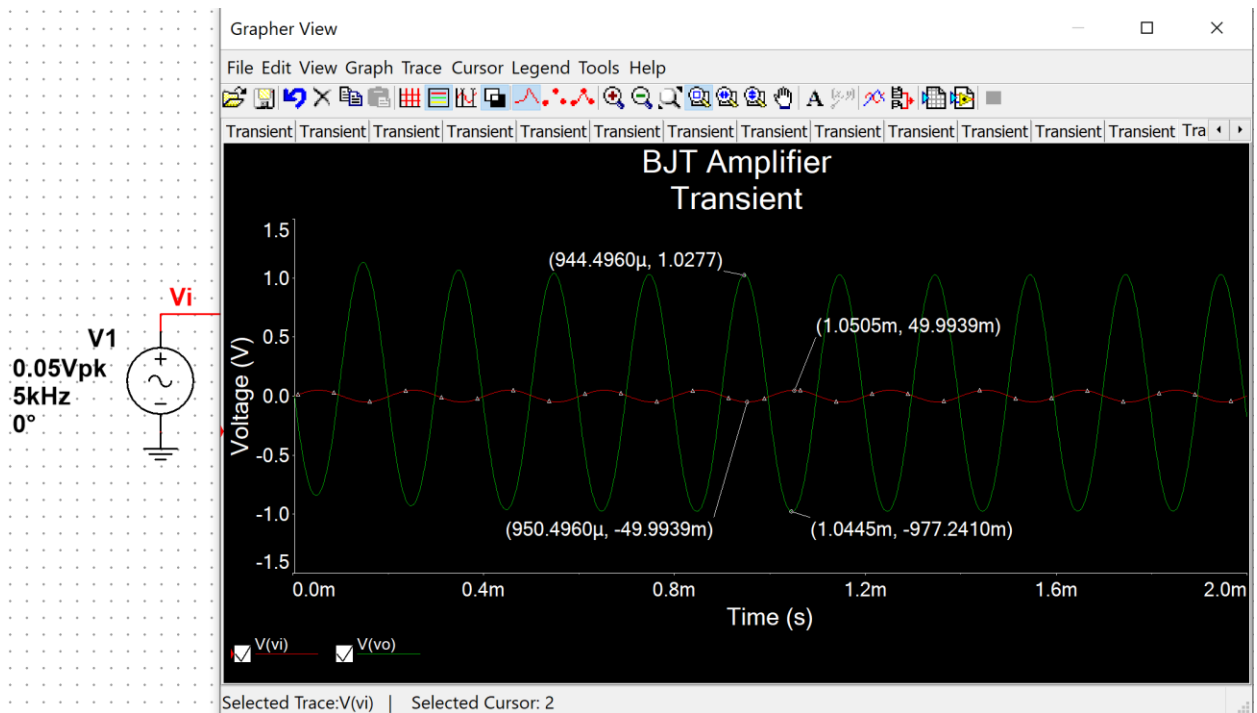


Figure 3: Time-domain waveform

$$A_v = \frac{1.03 - (-0.977)}{0.05 - (-0.05)} = 20.07 \approx 20$$

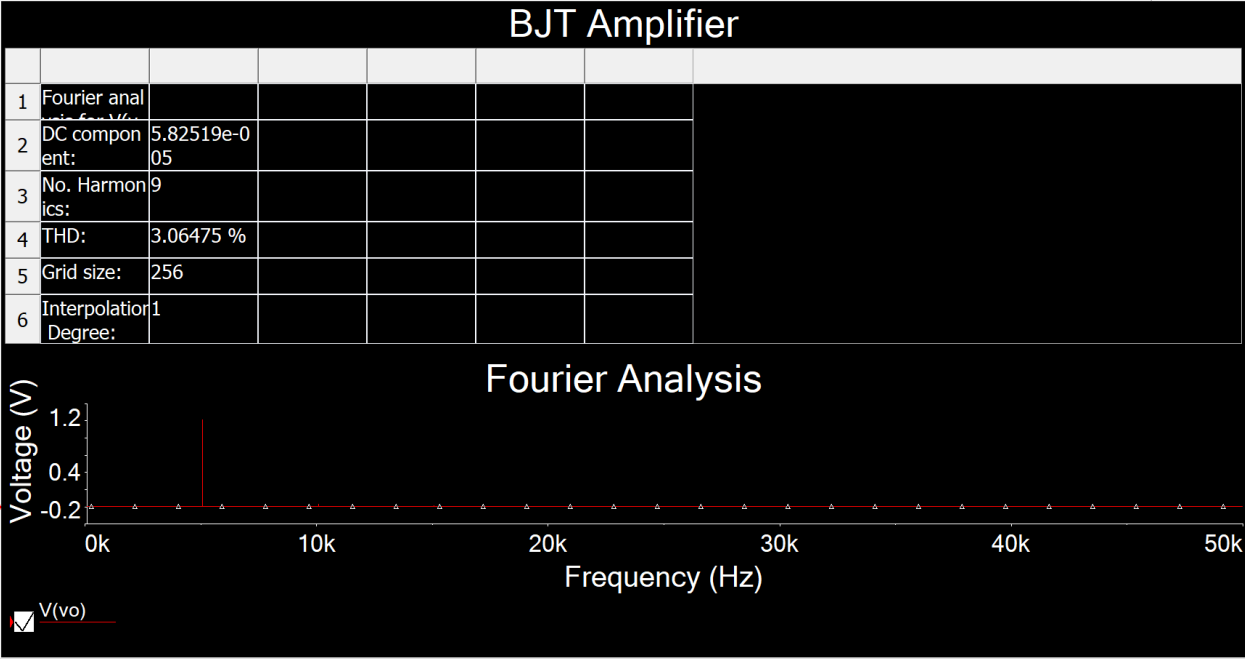


Figure 4: THD

THD = 3.06% which is less than 5%

Measurement

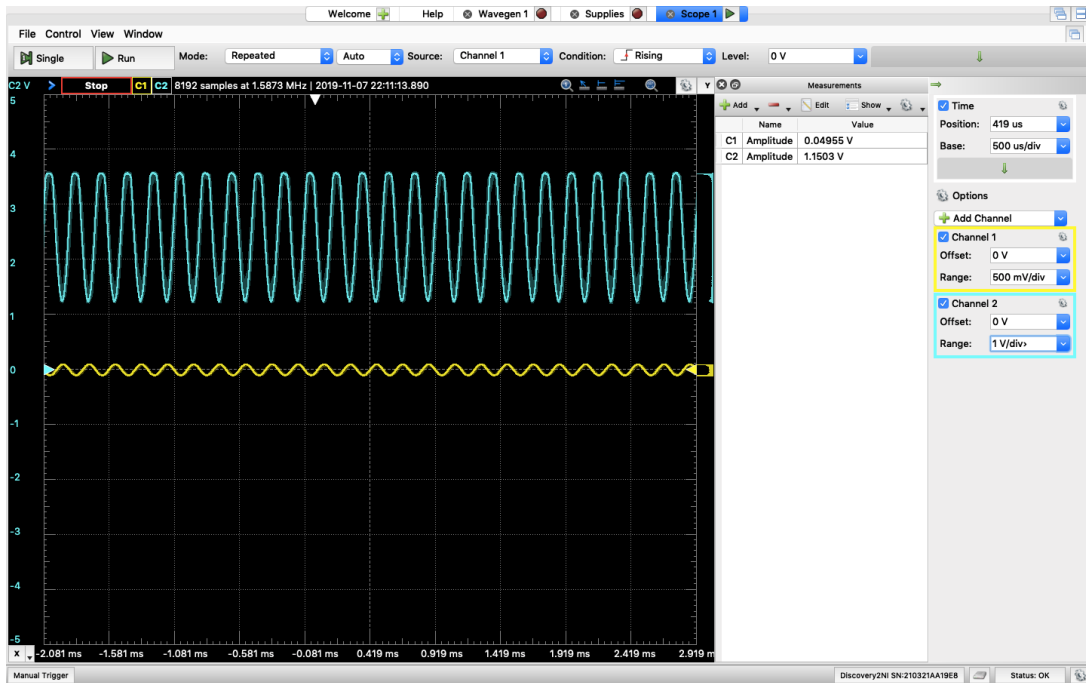


Figure 5: Stage 1 Gain

(I change R_G from 15Ω to 3.33Ω since 15Ω didn't give me gain of 20)

$$A_v = \frac{1.1503}{0.04955} = 23.21$$

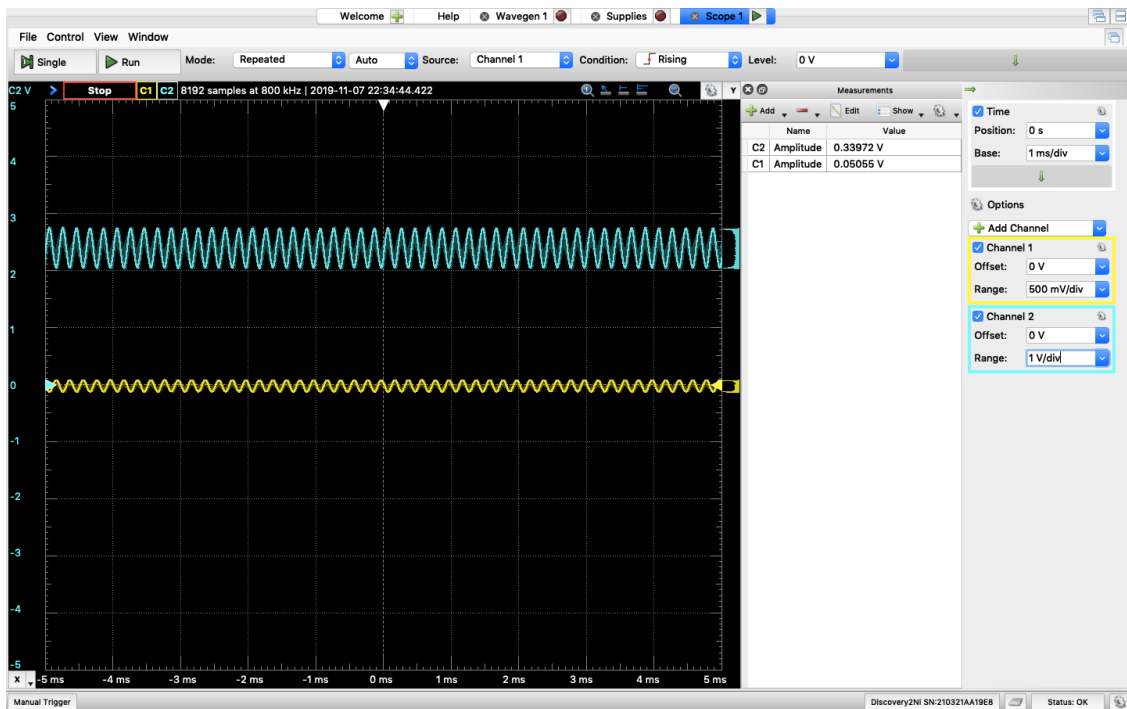


Figure 6: Stage 2 Gain

$$A_V = \frac{0.33972}{0.05055} = 6.72$$

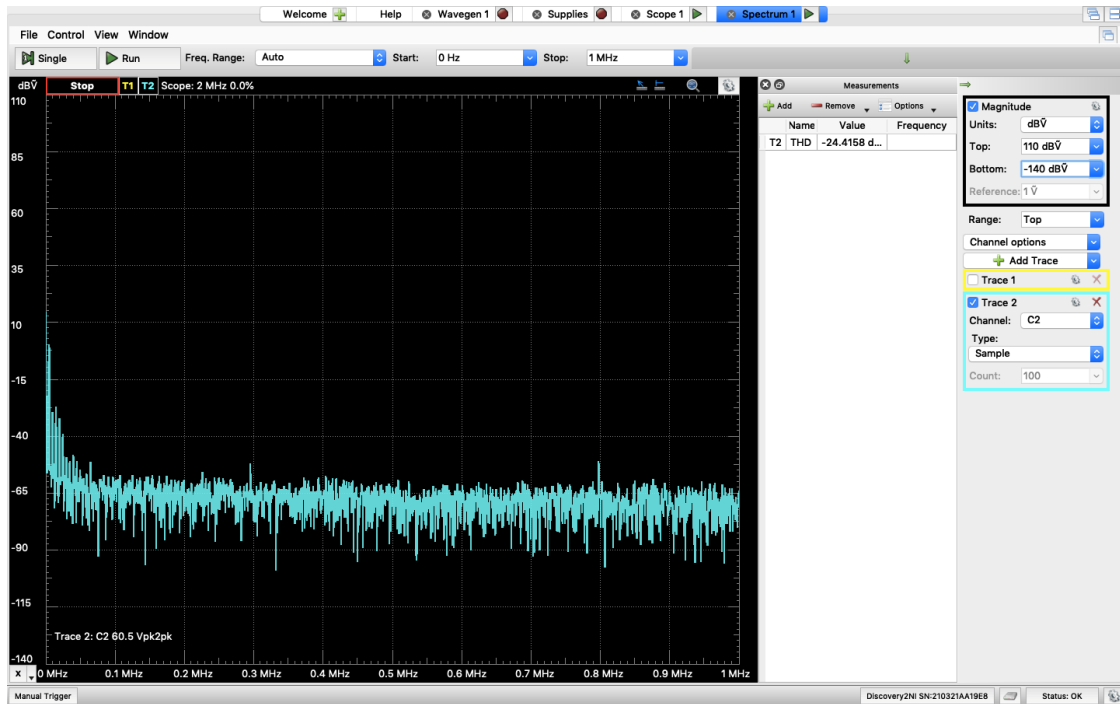


Figure 7: THD at Stage 1

$$\text{THD} = -24.4158\text{dB} = 0.06015 = 6\%$$

Table

	Calculation	Simulation
V_{RE}	1.3V	1.34V
V_{RC}	2.3V	2.27V
I_{C1}	4.2mA	4.44mA
I_{C2}	48mA	44.4mA

Comment

The measurement part is not correct for several reasons. First, the Analog Discovery 2 can only handle up to 250mW. To make stage 2 have gain of 20, the circuit needs to be modified to reduce the power consumption at stage 1. Second, the breadboard, resistors, transistors, and capacitors in the real world are not ideal. So that why not everything work as simulation.